

Inductor




$L \rightarrow$ depends on configuration
 \rightarrow depends on medium

$$\phi_{\text{magnetic}} = (B)(\text{Area})N$$


$$\phi \propto I$$

$$\boxed{\phi = LI}$$

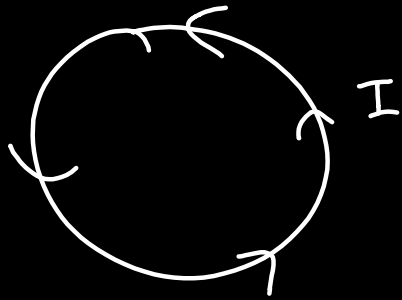

μ_0 \longrightarrow $\mu_r \mu_0$
 Vacuum medium.

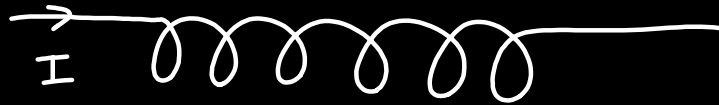$\mu_r \rightarrow$ relative permeability



$$\boxed{\Phi = LI}$$

Faraday & Lenz Law.

If flux changes


induced $\mathcal{E}_{mf} \Rightarrow$

$$\left| \frac{d\Phi}{dt} \right|$$

it oppose the change

$$\mathcal{E}_{mf} = - \frac{d\Phi}{dt}$$

$$\boxed{|\mathcal{E}_{mf}| = L \frac{dI}{dt}} \quad \begin{matrix} \star \\ \star \end{matrix}$$

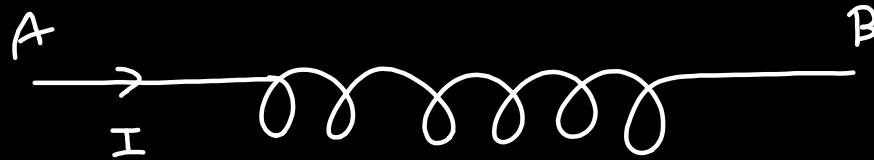


If I constant, ϕ constant, $\mathcal{E}_{mf} = 0$ induced, $V_A = V_B$

If I variable, ϕ change, \mathcal{E}_{mf} induce Hoga, $\mathcal{E}_{mf} = L \left(\frac{dI}{dt} \right)$

$$V_A - V_B = L \frac{dI}{dt}$$


Circuit Elements

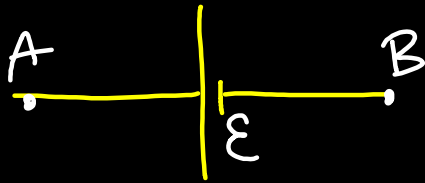


$$V_A - V_B = \mathcal{E}$$



$$V_A - V_B = IR$$

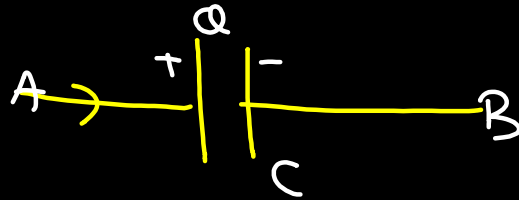

$$V_A - V_B = Q/C$$

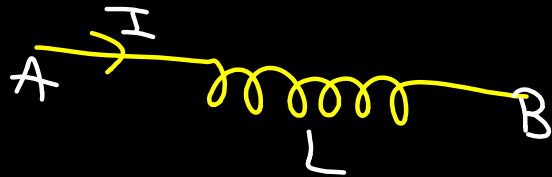

$$V_A - V_B = L \frac{dI}{dt}$$



$$V_A - V_B = L \frac{dI}{dt}$$

① I constant $\left(\frac{dI}{dt} = 0 \right)$

$$V_A - V_B = 0$$

$$V_A = V_B$$

② I increasing $\left(\frac{dI}{dt} = +ve \right)$

$$V_A - V_B = +ve$$

$$V_A > V_B$$


③ I decreasing $\left(\frac{dI}{dt} = -ve \right)$

$$V_A - V_B = -ve$$

$$V_A < V_B$$

Q Find $V_A - V_B = ??$

I is $10A$ & increasing at rate $5A/sec$

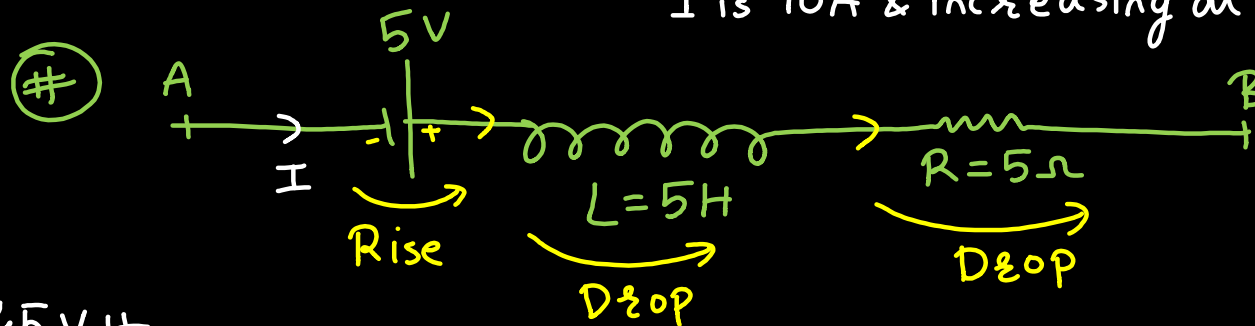

a) -45 Volt

b) 50


c) 20

d) 70

$$V_A + 5 - L \frac{dI}{dt} - IR = V_B$$

$$V_A - V_B = L \frac{dI}{dt} + IR - 5$$
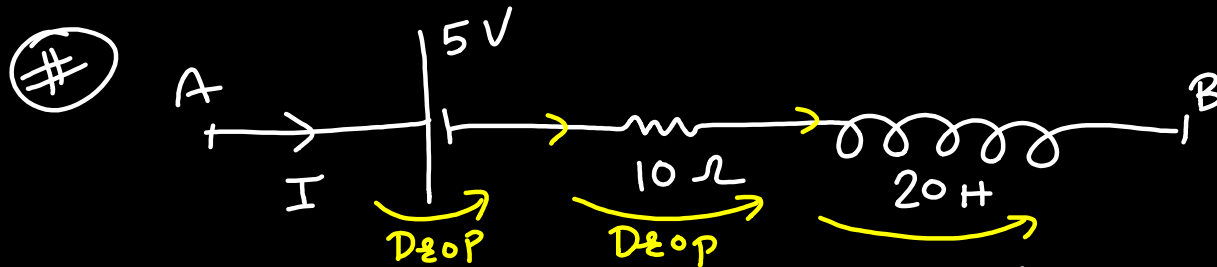
$$= (5)(+5) + 10(5) - 5 = \underline{70 \text{ Volt}}$$




$I = 10A$ & is decreasing at rate $1A/sec$

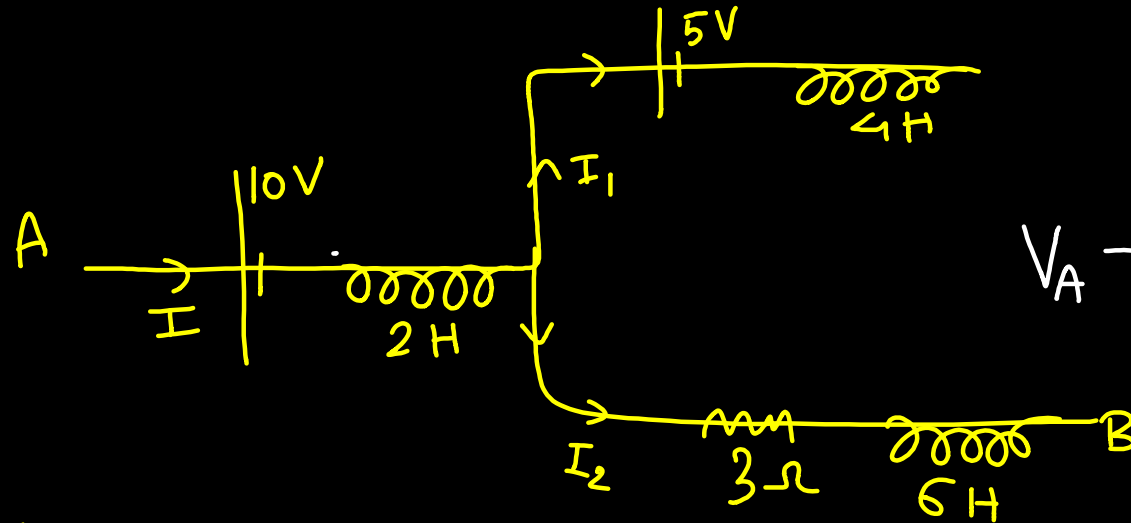- a) 85
- b) 35
- c) 125
- d) 110.

$$V_A - 5 - IR - L \frac{dI}{dt} = V_B$$

$$\begin{aligned} V_A - V_B &= 5 + IR + L \frac{dI}{dt} \\ &= 5 + 10(10) + 20(-1) \\ &= 105 - 20 \\ &= 85 \end{aligned}$$



Find $V_A - V_B = ?$

$$V_A - 10 - L \frac{dI}{dt} - I_2(3) - 6 \frac{dI_2}{dt} = V_B$$

$$I = 5A, \quad I_1 = 2A$$

I is increasing at rate $4A/s$

I_1 is " " " $6A/s$

$$\begin{aligned} V_A - V_B &= 10 + L \frac{dI}{dt} + I_2(3) + 6 \frac{dI_2}{dt} \\ &= 10 + 2(4) + (3)(3) + 6(-2) \\ &= \boxed{15} \end{aligned}$$

$$I = I_1 + I_2$$

$$5 = 2 + I_2$$

$$\boxed{3 = I_2}$$


$$\frac{dI}{dt} = 4 \text{ A/s}$$

$$I = I_1 + I_2$$

$$\frac{dI}{dt} = \frac{dI_1}{dt} + \frac{dI_2}{dt}$$

$$4 = 6 + \frac{dI_2}{dt}$$

$$\boxed{-2 = \frac{dI_2}{dt}}$$

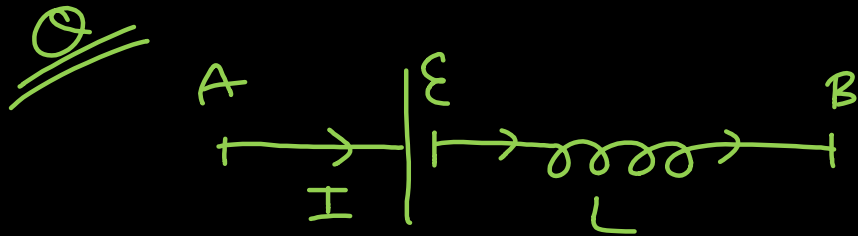

$$V_A - \varepsilon - L \frac{dI}{dt} = V_B$$

$$V_A - V_B = ?$$


$$V_A - V_B = \varepsilon + L \frac{dI}{dt}$$



$$V_A - L \frac{dI}{dt} = V_B$$

$$V_A - V_B = L \frac{dI}{dt}$$


L-R circuits (growth of current)

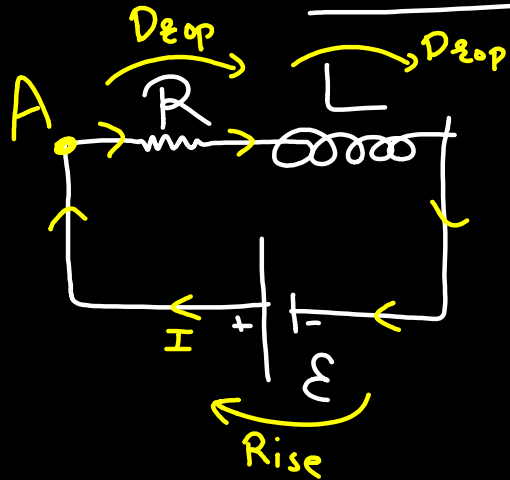

Apply Kirchhoff's Law / KVL in Loop

$$V_A - IR - L \frac{dI}{dt} + \varepsilon = V_A$$


$$\varepsilon = IR + L \frac{dI}{dt}$$

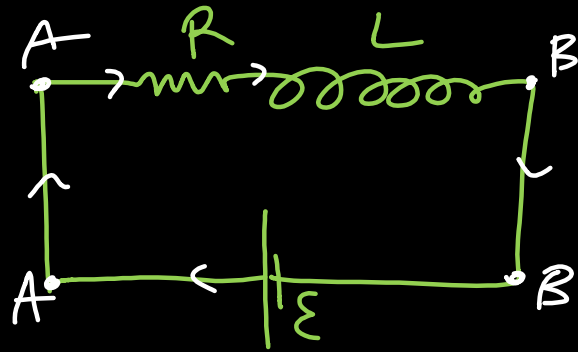


$$V_A - V_B = \mathcal{E}$$


$$V_A - V_B = IR + L \frac{dI}{dt}$$

$$\mathcal{E} = IR + L \frac{dI}{dt}$$

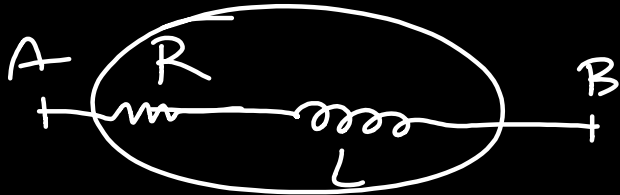

$$IR + L \frac{dI}{dt}$$

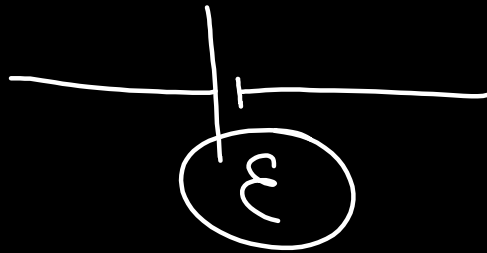

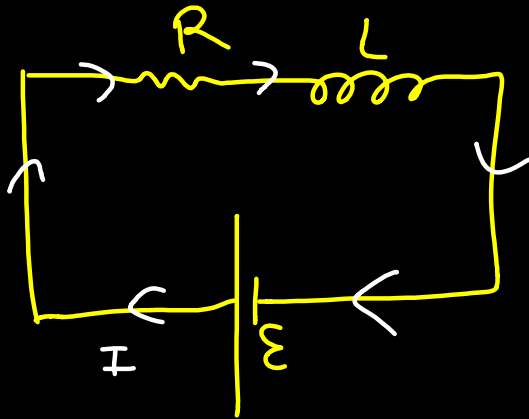

$$\varepsilon = IR + L \frac{dI}{dt}$$

$$\varepsilon - IR = L \frac{dI}{dt}$$

$$dt = \frac{L dI}{\varepsilon - IR}$$

$$\frac{dt}{L} = \frac{dI}{\varepsilon - IR}$$

Basic

$$\int \frac{1}{x} dx = \log_e x$$

$$\int \frac{1}{ax+b} dx = \frac{\log_e(ax+b)}{a}$$

$$\int \frac{dx}{6-7x} = \frac{\log_e(6-7x)}{-7}$$

$$\int \frac{dt}{L} = \int \frac{dI}{\epsilon - IR}$$

$$\frac{t}{L} = \frac{\log_e(\epsilon - IR)}{-R}$$

$$\left[\frac{-R}{L} t \right]_0^t = \left[\log_e(\epsilon - IR) \right]_0^I$$

$$\Rightarrow \frac{-R}{L} t = \log_e(\epsilon - IR) - \log_e(\epsilon)$$

$$\frac{-tR}{L} = \log_e \left(\frac{\epsilon - IR}{\epsilon} \right)$$

take anti log

$$e^{\frac{-tR}{L}} = \frac{\epsilon - IR}{\epsilon}$$

$$\epsilon e^{-tR/L} = \epsilon - IR$$

$$IR = \epsilon - \epsilon e^{-tR/L}$$

$$I = \frac{\mathcal{E}}{R} \left(1 - e^{-tR/L} \right)$$

$\tau \Rightarrow$ time constant

$$I = I_{\text{steady}} \left(1 - e^{-t/\tau} \right)$$

$$\tau = \frac{L}{R}$$

τ unit of time
= seconds.

$$I_{\text{steady}} = \mathcal{E}/R$$

unit of $\frac{L}{R} \rightarrow$ seconds

Very Special Case / Making it Easy

$$I = I_{\text{steady}} (1 - e^{-t/\tau})$$

$t = 0$ $e^0 = 1$

$$I = I_{\text{steady}} (1 - 1)$$

$$I = 0$$

$t = \infty$

$$I = I_{\text{steady}} (1 - 0)$$

$$= I_{\text{steady}}$$

$$I = \frac{\mathcal{E}}{R}$$


$e^{-\infty} = 0$

$\frac{1}{e^{\infty}} = \frac{1}{2.7^{\infty}} = \frac{1}{\infty} = 0$


#

$t=0$  behaves as Open Circuit

 \Rightarrow 

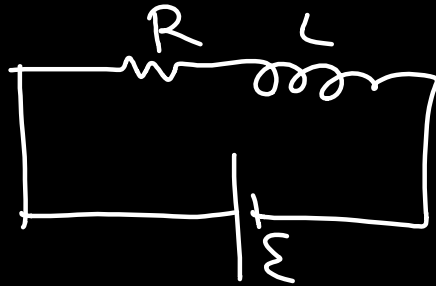

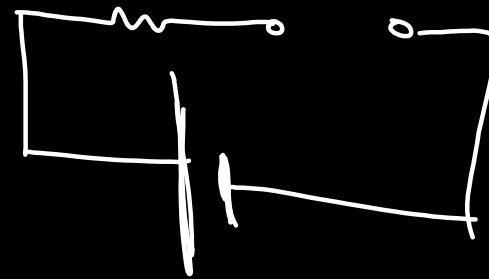


$t=0 \Rightarrow$




$I=0$

$t = \infty$  behaves as Short Circuit

 \Rightarrow 
at $t = \infty$

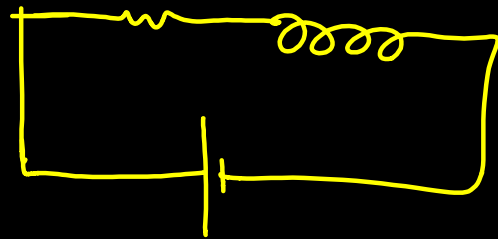


$t = \infty \Rightarrow$

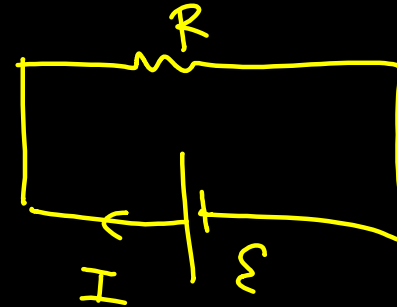


$$I = \frac{\mathcal{E}}{R}$$

Q Find current in Circuit in each Branch at
 ① $t=0$ & ② $t=\infty$.


Q 1

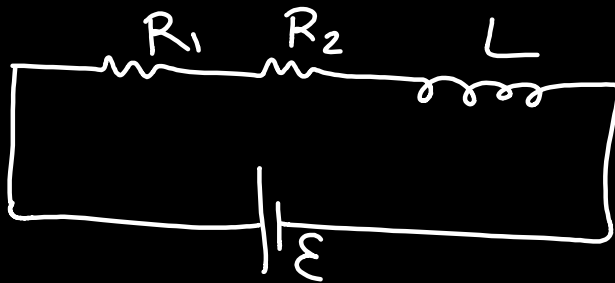

$t=0$


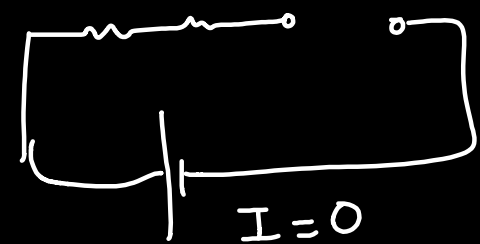


$t=\infty$

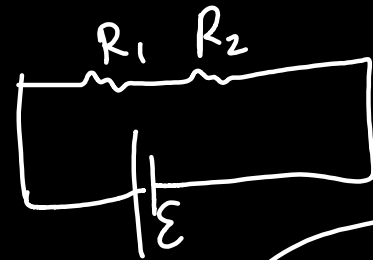


$$I = \frac{\mathcal{E}}{R_1 + R_2}$$

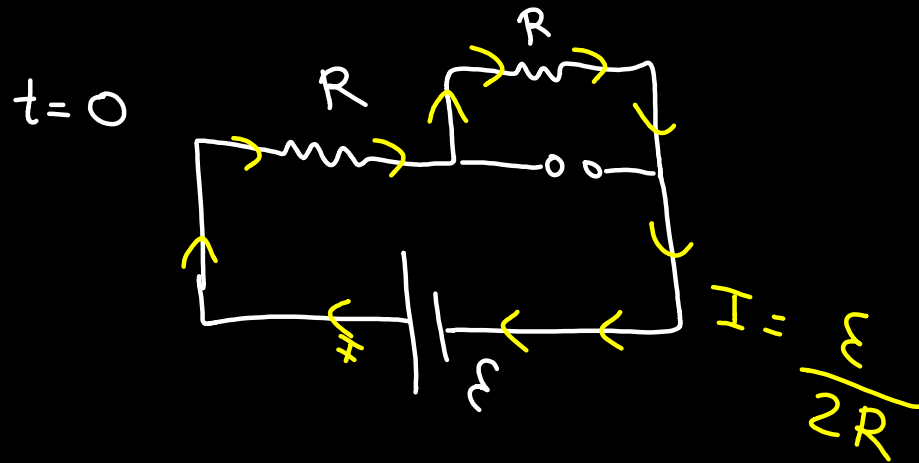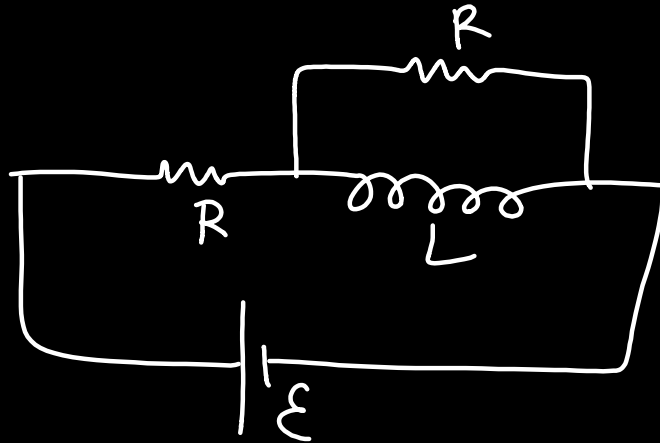
At $t=0$ & $t=\infty$ Find total Current from battery??



$t=\infty$

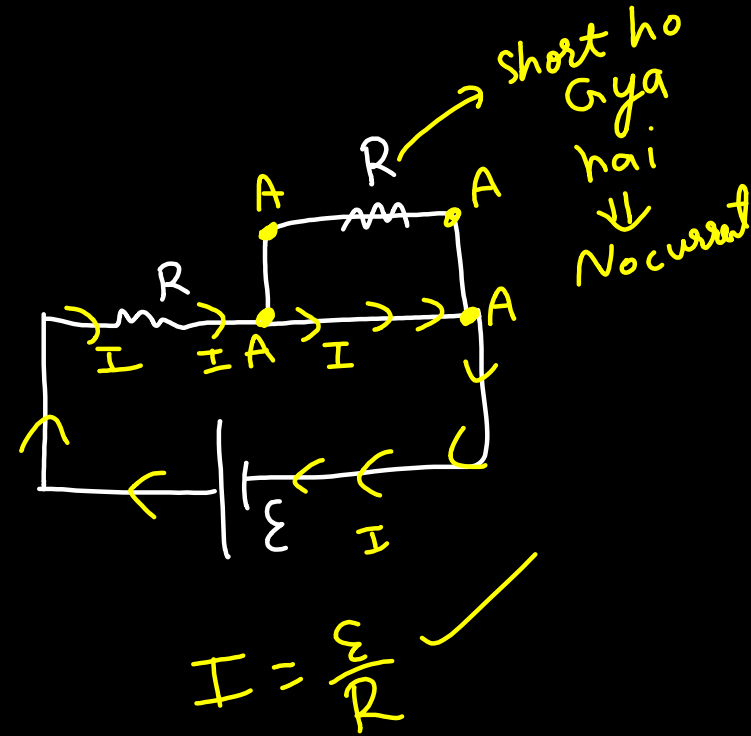

Energy Stored in Inductor

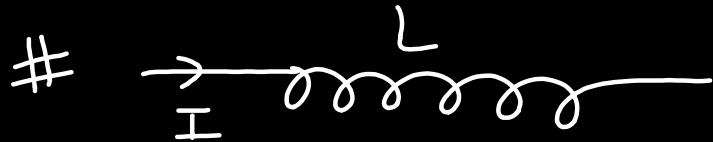


$I = I_0 (1 - e^{-t/\tau})$

$$\text{Energy stored inside inductor} = \frac{1}{2} L I^2$$

energy stored in L R circuit


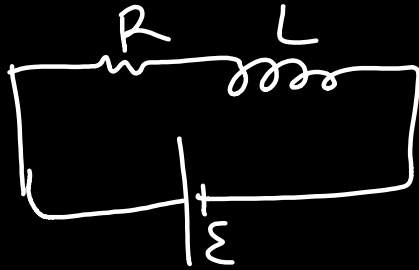
$$\frac{1}{2} L [I_0 (1 - e^{-t/\tau})]^2$$



$$I_0 = \frac{\varepsilon}{R}$$

Steady
State
Current

initial energy = 0

$$\text{maximum energy stored} = \frac{1}{2} L I_0^2$$

function of time

$$\text{Energy stored} = \frac{1}{2} L \left[I_0 (1 - e^{-t/\tau}) \right]^2$$

Power \longrightarrow Rate of Energy Stored in L


$$E_{\text{energy}} = \frac{1}{2} L I^2$$

$$\frac{d(E_{\text{energy}})}{dt} = \frac{1}{2} L \left(2 I \frac{dI}{dt} \right)$$

$$\text{Power or rate of energy} = \left(L \frac{dI}{dt} \right) I$$

$$\begin{aligned} \text{Power} &= V I \\ &= (E_{\text{mf}}) I \\ &= \left(L \frac{dI}{dt} \right) I \end{aligned}$$

#

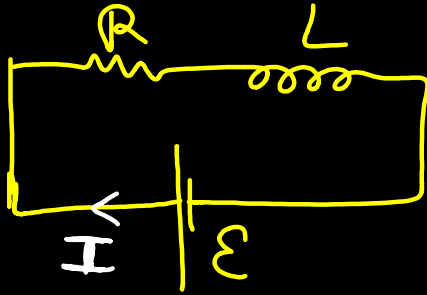


$$I = I_0 (1 - e^{-t/\tau})$$

$$I_0 = \frac{\varepsilon}{R}$$

Steady
State
current

$$\tau = \frac{L}{R}$$

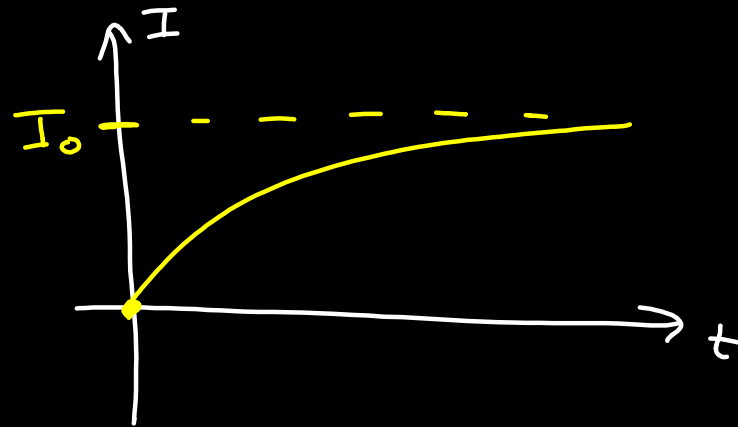

τ = Time Constant \rightarrow time when 63% of Steady State current is achieved.

$$t=0 \quad \checkmark$$

$$t=\infty \quad \checkmark$$

I at $t=\tau$

$$I = I_0(1 - e^{-t/\tau})$$

$$= I_0(1 - e^{-\tau/\tau})$$

$$= I_0(1 - e^{-1})$$

$$= I_0(1 - \frac{1}{e})$$

$$= I_0(1 - \frac{1}{2.7})$$

$$= I_0(1 - 0.37) = 0.63 I_0$$

$$e = 2.7$$

I at $t = (\ln 2) \tau$

Prop $e^{\ln(x)} = x$

$$e^{-\ln 2} = e^{\ln(2)^{-1}} = e^{\ln(\frac{1}{2})} = \frac{1}{2}$$

$$I = I_0(1 - e^{-t/\tau})$$

$$= I_0(1 - e^{-\ln(2) \tau / \tau})$$

$$= I_0(1 - e^{-\ln 2}) = I_0(1 - \frac{1}{2})$$

$$= I_0(\frac{1}{2})$$

$$\text{Power (rate of energy)} = \left(L \frac{dI}{dt} \right) I$$

$$I = I_0 \left(1 - e^{-t/\tau} \right)$$

$$\begin{aligned} \frac{dI}{dt} &= I_0 \left(0 - e^{-t/\tau} \times -\frac{1}{\tau} \right) \\ &= \frac{I_0}{\tau} e^{-t/\tau} \end{aligned}$$


$$\begin{aligned} \text{Power} &= L \left[\frac{I_0}{\tau} e^{-t/\tau} \right] \left(I_0 (1 - e^{-t/\tau}) \right) \\ &= \frac{L I_0 I_0}{\tau} e^{-t/\tau} (1 - e^{-t/\tau}) \\ &= \frac{L I_0^2}{\tau} e^{-t/\tau} (1 - e^{-t/\tau}) \end{aligned}$$

Basic

e^x
 \downarrow differentiation
 e^x

e^{-5x}
 \downarrow diff
 $(e^{-5x})(-5)$

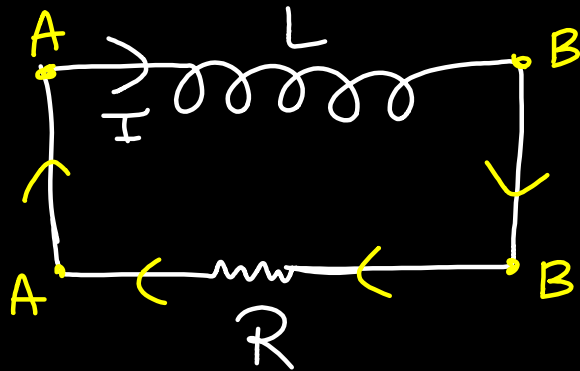Decay of Current (initial current = I_0) (I decreasing)



$$-L \frac{dI}{dt} = IR$$

$$\frac{dI}{dt} \text{ -ve.}$$

$$V_A - L \frac{dI}{dt} - IR = V_A$$

$$\boxed{-L \frac{dI}{dt} = IR}$$

$$I = -\frac{L}{R} \frac{dI}{dt}$$

$$-\frac{R}{L} dt = \frac{dI}{I}$$

$$-\frac{R}{L} \int dt = \int \frac{dI}{I}$$

$$\left[-\frac{Rt}{L} \right]_0^t = \left[\log_e I \right]_{I_0}^I$$

$$-\frac{R}{L} t = \log_e I_f - \log_e I_0$$


$$-\frac{R}{L} t = \log_e \left(\frac{I_f}{I_0} \right)$$

\Rightarrow anti log

$$e^{-\frac{R}{L} t} = \frac{I_f}{I_0}$$

$$I_f = I_0 e^{-tR/L}$$
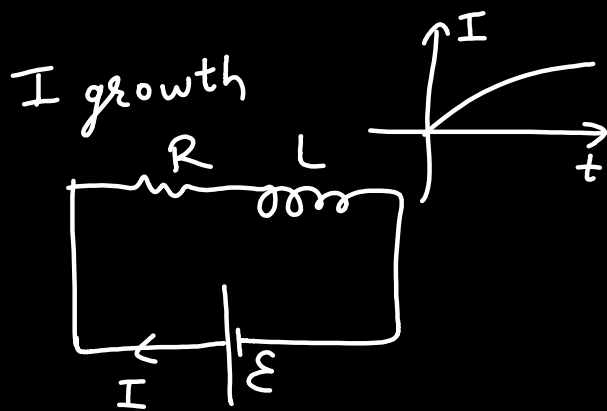
$$\boxed{I_f = I_0 e^{-t/\tau}} \quad \tau = L/R$$




$$I = I_0 (1 - e^{-t/\tau})$$

Starting $I = 0$

∞ $I = I_0$


I decay

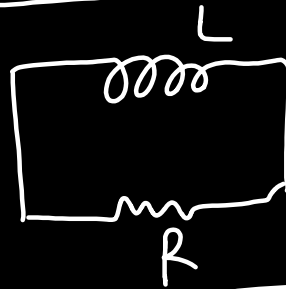

$$I = I_0 e^{-t/\tau}$$

$t = 0$ $I = I_0$

∞ $I = 0$

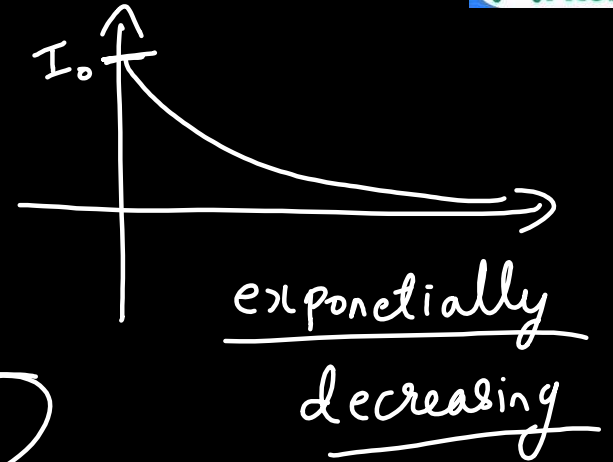

Starting energy = $\frac{1}{2} L I_0^2$

finally lost by Resistor.

Inductor + Motional Emf + SHM + Circuit Solving + NLM


Basics of SHM

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

double diff of $x \propto -(x)$

$$T_{\text{ime}} = \frac{2\pi}{\omega}$$

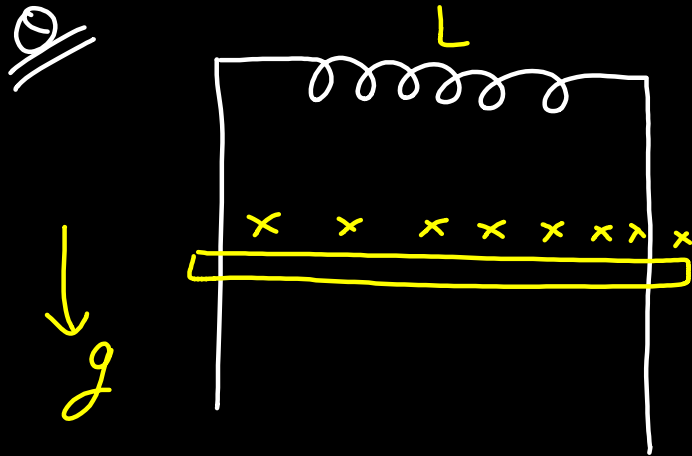& $x = A \sin(\omega t)$ if $x=0$ from starting.




conducting Rod
movable Rod
mass = m
length = l



Initial current = 0
Rod released from rest
magnetic field = B
resistance of loop is negligible.

Find

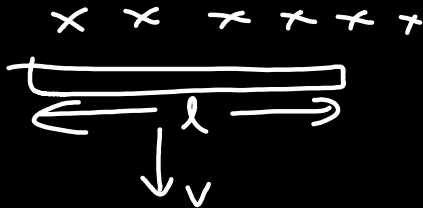- ① Draw FBD of rod
- ② vel as function of time




$$\mathcal{E}_{\text{mf}} = Blv$$

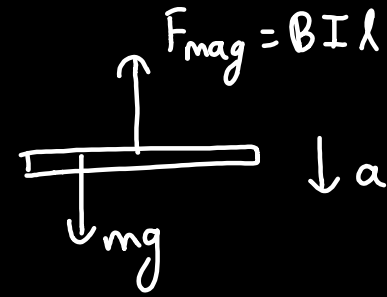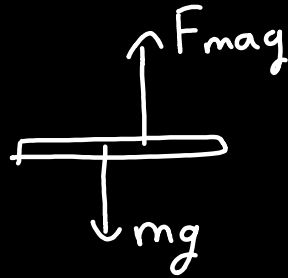

$$F_{\text{net}} = ma$$

$$mg - BIl = ma$$

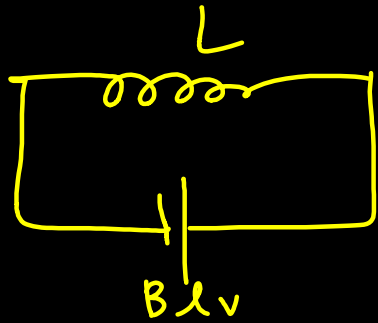

$$L \frac{dI}{dt} = Blv$$

$$\boxed{\frac{dI}{dt} = \frac{Blv}{L}} \quad (2)$$

$$\boxed{mg - BIl = ma} \quad (2)$$

$$mg - ma = BIl$$

diff

$$0 - m \frac{da}{dt} = Bl \frac{dI}{dt}$$

$$\boxed{-\frac{m}{Bl} \frac{da}{dt} = \frac{dI}{dt}}$$

$$\frac{dI}{dt} = \frac{Blv}{L} = -\frac{m}{Bl} \frac{da}{dt}$$

$$a = \frac{dv}{dt}$$

$$-\frac{B^2 l^2}{mL} v = \frac{da}{dt}$$

$$\frac{da}{dt} = \frac{d^2 v}{dt^2}$$

$$\frac{d^2 v}{dt^2} = -\left(\frac{B^2 l^2}{mL}\right) v \Rightarrow \underline{\underline{\text{Differential equation}}}$$

SHM

$$\frac{d^2x}{dt^2} = -\omega^2 x$$

$$x = A \sin(\omega t)$$

$$\text{If } t=0 \text{ or } x=0$$

$$\frac{d^2v}{dt^2} = -\left(\frac{B^2 l^2}{mL}\right) v$$

$$\omega^2 = \frac{B^2 l^2}{mL}$$

$$\omega = \frac{Bl}{\sqrt{mL}}$$

$$v = A \sin(\omega t)$$

If displ required

$$\int_0^t v dt = x \Rightarrow \int_0^t A \sin(\omega t) = \frac{A[-\cos(\omega t)]}{\omega} \Big|_0^t$$

$$\underline{\underline{\text{Displ} = \frac{A}{\omega} [1 - \cos \omega t]}}$$

$$v = A \sin(\omega t)$$

How to find A

$$t = 0 \quad \text{acc} = g$$

$$a = \frac{dv}{dt} = A \cos(\omega t) \times \omega$$

$$\text{acc} = A\omega \cos(\omega t)$$

$$t = 0$$

$$A\omega = g$$


Combination of Inductors :

(without considering mutual inductance)

Resis
Induct


Capacitor
Spring

① Series

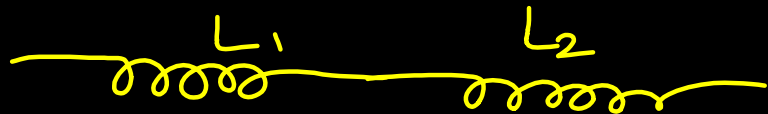

$$\Rightarrow L_{eq} = L_1 + L_2$$


② Parallel

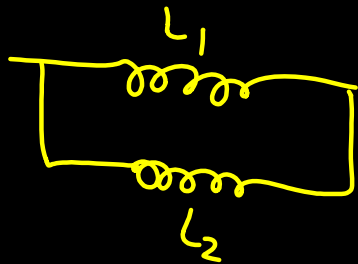


$$\Rightarrow \frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2}$$

If Mutual inductance considered

Both Same

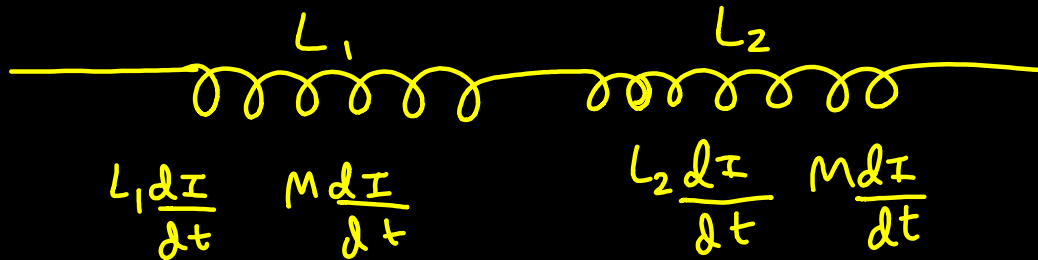

$$L_{eq} = L_1 + L_2 + 2M$$

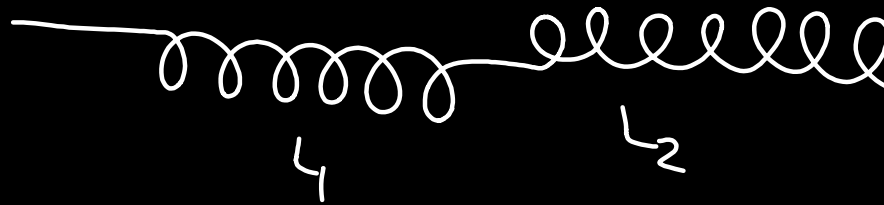


$$L_{eq} = L_1 + L_2 - 2M$$


$$M = k \sqrt{L_1 L_2}$$

$k = 1$ for ideal coupling

$$M = \sqrt{L_1 L_2}$$

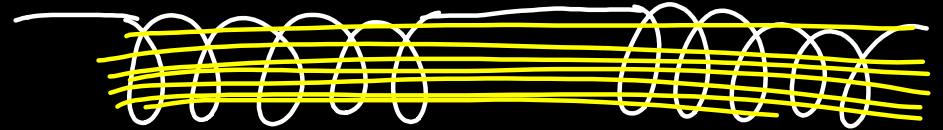


L-C oscillation

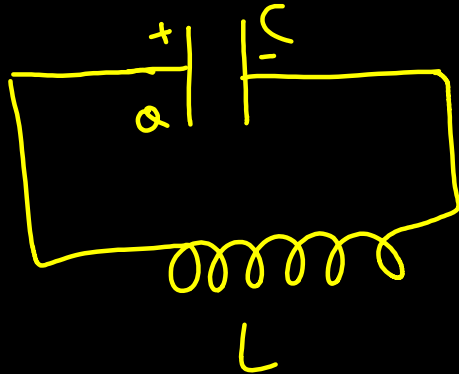

oscillation matches with SHM

SHM Basics

$T = \text{time period}$

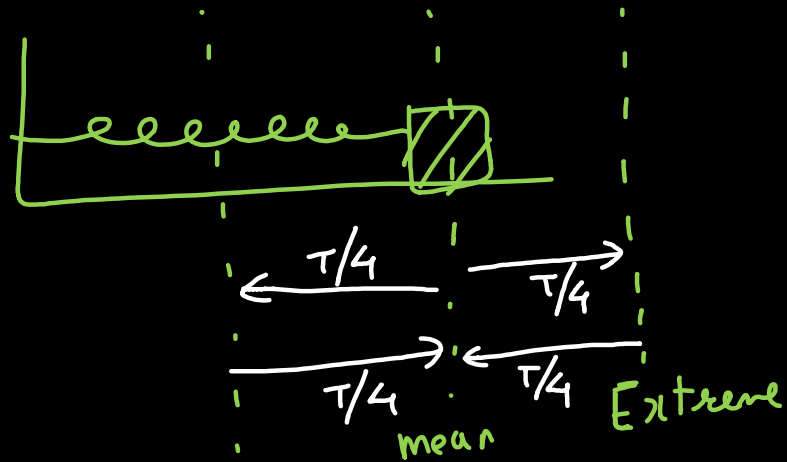

$ displ \Rightarrow$	max	○	maximum
$ speed \Rightarrow$	○	Maximum	○

Standard Equations

$$\# \frac{d^2x}{dt^2} = -\omega^2 x$$

$$\frac{d^2x}{dt^2} \propto -x$$

$$\# T = \frac{2\pi}{\omega}$$

$$\# \quad x = A \sin(\omega t) \quad t=0 \text{ or } x=0$$


$$\# \quad x = A \cos(\omega t) \quad t=0 \text{ or } x=\text{maximum}$$

Energy

$$\# \quad TE = PE + KE$$

$$\# \quad TE = \text{constant}$$

at mean $PE = 0$ here

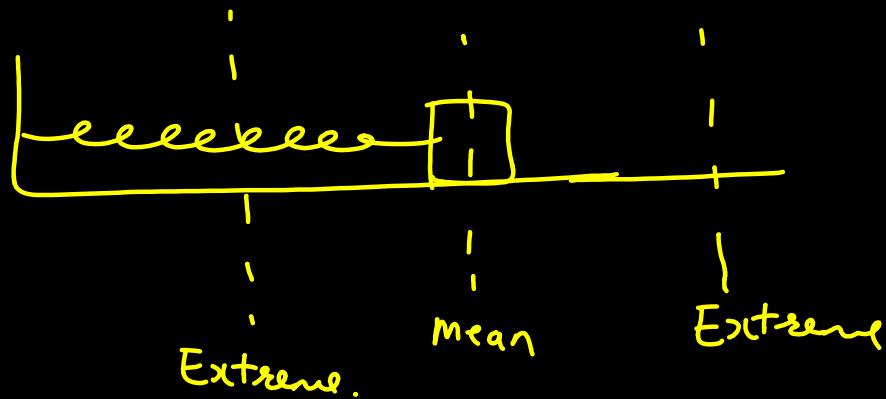

	Extreme.	mean	Extreme
$PE \Rightarrow$	maximum	0	maximum
$KE \Rightarrow$	0	maximum	0

$$PE = \frac{1}{2} kx^2$$


$$KE = \frac{1}{2} mv^2$$

$$TE = PE + KE$$

$$= PE_{\max} + 0$$

$$= 0 + KE_{\max}$$

LC oscillation

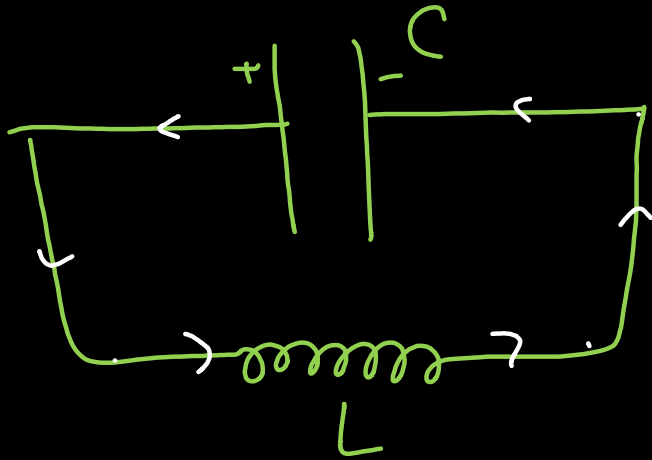

Suppose
initially
charge on capacitor = Q_0
current = 0

$$\left| \frac{Q}{C} \right| = \left| L \frac{dI}{dt} \right|$$

$$\frac{1}{LC} Q = \frac{dI}{dt}$$

$$\frac{1}{LC} Q = -\frac{d^2 Q}{dt^2}$$

$$I = \frac{dQ}{dt}$$

But Q is decreasing
 $dQ < 0$

$$I = -\frac{dQ}{dt}$$

$$\frac{dI}{dt} = -\frac{d^2 Q}{dt^2}$$

$$\frac{d^2 Q}{dt^2} = -\frac{1}{LC} Q$$

double diff of $Q \propto -Q$

SHM

Q is performing SHM

$$\frac{d^2 x}{dt^2} = -\omega^2 x$$

$$\Rightarrow \omega^2 = \frac{1}{LC}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$T = \frac{2\pi}{\omega} = 2\pi\sqrt{LC}$$

$$f = \frac{1}{T} = \frac{1}{2\pi\sqrt{LC}}$$

✱
✱
✱.

$$Q = Q_0 \sin(\omega t) \quad \text{if } t=0 \quad Q=0$$

$$Q = Q_0 \cos(\omega t) \quad \text{if } t=0 \quad Q = Q_0 \text{ max}$$

if initially Capacitor charged

$$Q = Q_0 \cos(\omega t)$$

$$\frac{dQ}{dt} = -Q_0 \sin(\omega t) \times \omega$$

$$I = -Q_0 \omega \sin(\omega t)$$


$$E \text{ of capacitor} = \frac{Q^2}{2C}$$

$$E_{\text{capacitor}} = \frac{Q_0^2}{2C} \cos^2 \omega t$$

$$E \text{ of inductor} = \frac{1}{2} L I^2$$

$$E_{\text{inductor}} = \frac{L Q_0^2 \omega^2}{2} \sin^2(\omega t)$$

Focus on Energy

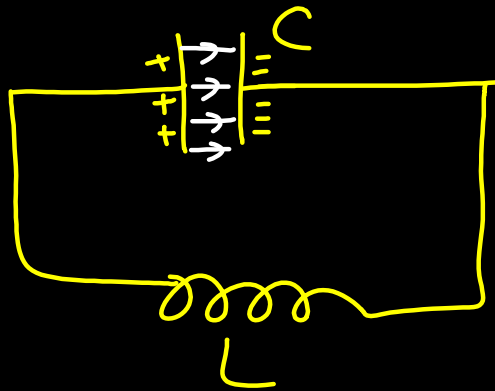


$t = 0$ $Q = Q_0$ $I = 0$

$$TE = E_{\text{capacitor}} + E_{\text{inductor}}$$


$$TE = \frac{Q_0^2}{2C} + 0$$

$t = T/4$

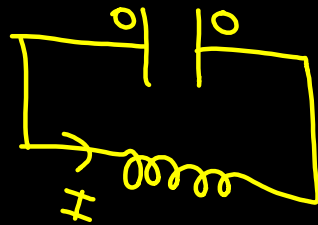

$$Q = 0 \quad I = I_{\text{max}} = Q_0 \omega$$

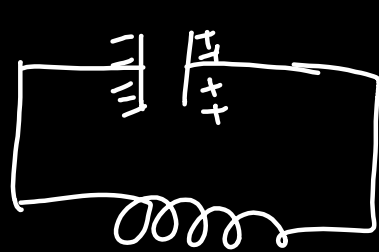
$$\begin{aligned} TE &= E_{\text{capacitor}} + E_{\text{inductor}} \\ &= 0 + \frac{1}{2} L (I_{\text{max}})^2 \end{aligned}$$



$$t = T/2$$


$$Q = Q_0 \quad I = 0$$

max.

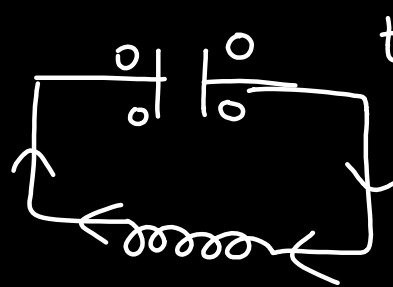

$$t = 3T/4$$

$$Q = 0 \quad I = \text{max}$$

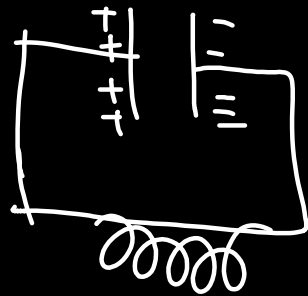

$$t = T$$

$$Q = Q_0 \quad I = 0$$

max

at any general time


$$Q = Q_0 \cos \omega t$$

$$I = Q_0 \omega \sin(\omega t)$$

$$E_{\text{capacitor}} = \frac{Q_0^2}{2C} \cos^2 \omega t$$

$$E_{\text{inductor}} = \frac{1}{2} L I_0^2 \sin^2 \omega t$$

Q //

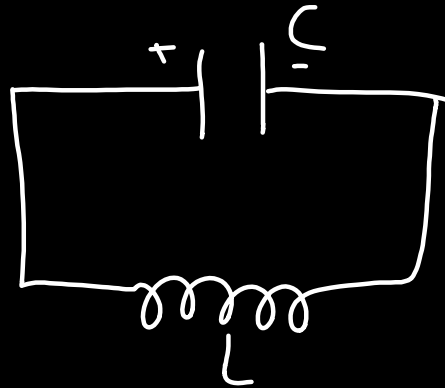

$$C = 100 \mu F$$

$$L = 40 \text{ mH}$$

$$\text{initial } Q_0 = 100 \mu (\text{coulomb})$$

Find ① angular freq of oscillation.

② time when energy is equally stored in electric & magnetic form

③ time when all energy is in magnetic form.

$$\textcircled{1} \quad \omega = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{40 \times 10^{-3} \times 100 \times 10^{-6}}} = \frac{1}{\sqrt{4 \times 10^{-6}}} = \frac{1}{2 \times 10^{-3}} = \frac{1000}{2} = 500 \text{ rad/sec.}$$

$$\textcircled{2} \quad E_{\text{capacitor}} = \frac{Q^2}{2C}$$

$$E_{\text{inductor}} = \frac{1}{2} L I^2$$

$$Q = Q_0 \cos(\omega t)$$

$$I = Q_0 \omega \sin(\omega t)$$

$$E_{\text{capacitor}} = \frac{Q_0^2}{2C} \cos^2$$

$$E_{\text{ind}} = \frac{1}{2} L Q_0^2 \omega^2 \sin^2 = \frac{1}{2} \cancel{L} Q_0^2 \frac{1}{\cancel{L} C} \sin^2 = \frac{Q_0^2}{2C} \sin^2$$

$$E_{\text{cap}} = E_{\text{ind}}$$

$$\cos = \sin$$

$$45^\circ \text{ or } \pi/4$$

$$\omega t = \frac{\pi}{4}$$

$$t = \frac{\pi}{4\omega}$$

$$\textcircled{2} \quad t = \frac{\pi}{4(500)} = \frac{\pi}{2000} \text{ sec}$$

$$\textcircled{3} \quad t = \frac{T}{4} = \left(\frac{2\pi}{\omega} \right) \frac{1}{4} = \frac{\pi}{2\omega} = \frac{\pi}{2(500)} = \frac{\pi}{1000} \text{ sec.}$$

In above Question
Find (4) max I in circuit


(5) TE of circuit

$$\begin{aligned}
 (4) \quad I_{\max} &= Q_0 \omega \\
 &= (100 \mu) 500 \\
 &= 5 \times 10^4 \times 10^{-6} \\
 &= \underline{0.05 \text{ A}}
 \end{aligned}$$

$$\begin{aligned}
 TE &= \frac{Q^2}{2C} + \frac{1}{2} L I^2 \\
 &= \frac{Q_{\max}^2}{2C} + 0 \\
 &= 0 + \frac{1}{2} L I_{\max}^2
 \end{aligned}$$

$$\begin{aligned} \textcircled{5} \quad TE &= \frac{Q_{\max}^2}{2C} = \frac{(100\mu)^2}{2(100\mu)} = \frac{100\mu}{2} = 50\mu \\ &= \underline{5 \times 10^{-5} \text{ Joule}} \end{aligned}$$


Q freq of oscillation of circuit

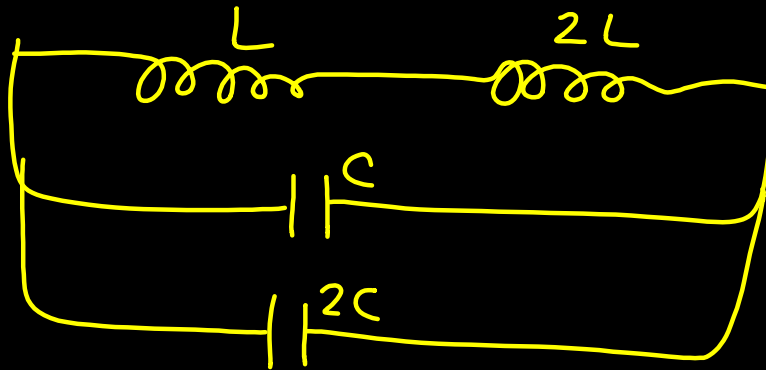

series
 $L = L_1 + L_2$

$$L_{eq} = 3L$$

parallel
 $C_{eq} = C_1 + C_2$
 $= 3C$

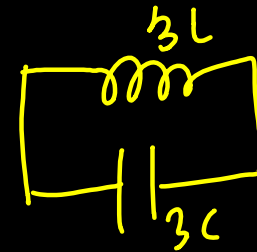

$$f = \frac{1}{2\pi \sqrt{(3L)(3C)}}$$

$$f = \frac{1}{6\pi \sqrt{LC}} \checkmark$$


Q

a) $Q/2$

b) $Q_0/\sqrt{2}$

c) $Q_0/\sqrt{3}$

d) $\frac{\sqrt{3}}{2} Q_0$

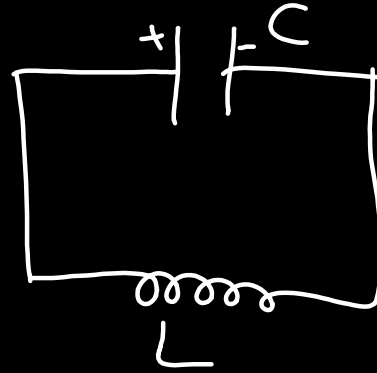

$$Q = Q_0 \cos(\omega t)$$

$$= Q_0 \frac{1}{\sqrt{2}}$$


initial charge on capacitor = Q_0

What will be the charge on capacitor when $E_{\text{electrical}}$ is equal to E_{magnetic} ?

$$E_{\text{cap}} = E_{\text{ind}}$$

$$\cos^2 = \sin^2 \quad 45^\circ$$

$$\theta = \omega t = \pi/4$$

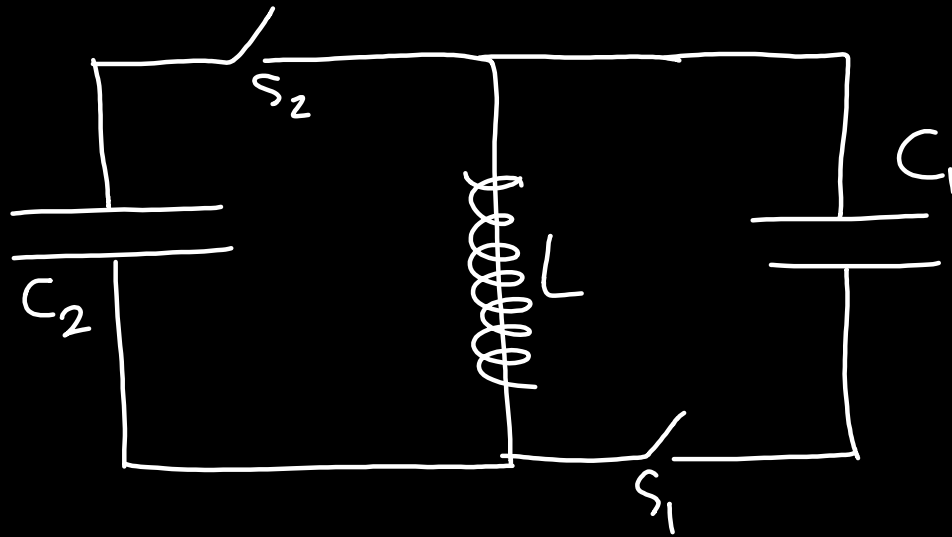

$$C_1 = 900 \mu\text{F}$$

$$C_2 = 100 \mu\text{F}$$

$$L = 10\text{H}$$

Initially C_1 was charged with 100 Volt battery & C_2 was uncharged.

Now S_1 is closed & S_2 is open for sometime t_1 And after that S_1 is open & S_2 is closed for time t_2 . Finally ΔV across C_2 was 300 Volt
Find minimum value of t_1 & t_2

Hint

$$t=0 \quad C_1 \text{ energy} \longrightarrow \frac{1}{2} C_1 V_1^2 = \frac{1}{2} (900 \mu)(100)^2 = \frac{9}{2} \text{ J}$$

$$\text{finally } C_2 \text{ energy} \longrightarrow \frac{1}{2} C_2 V_2^2 = \frac{1}{2} (100 \mu)(300)^2 = \frac{9}{2} \text{ J}$$

$$\text{minimum } t_1 \longrightarrow \frac{T_1}{4} = \frac{2\pi \sqrt{LC_1}}{4} = \frac{\pi}{2} \sqrt{(10)(900 \mu)} = \frac{3}{20} \text{ sec}$$




$$\text{minimum } t_2 \longrightarrow \frac{T_2}{4} = \frac{2\pi \sqrt{LC_2}}{4} = \frac{2\pi}{4} \sqrt{(10)(100 \mu)} = \frac{1}{20} \text{ sec}$$

$$\pi = \sqrt{10}$$

Find the current flowing in the battery at

(i) $t = 0$

(ii) $t = \infty$

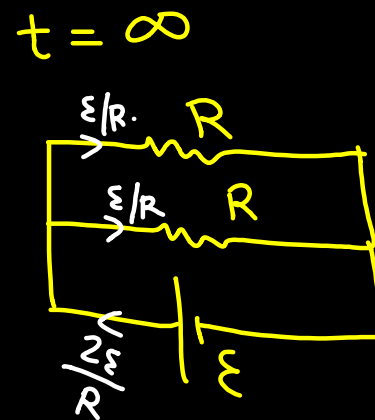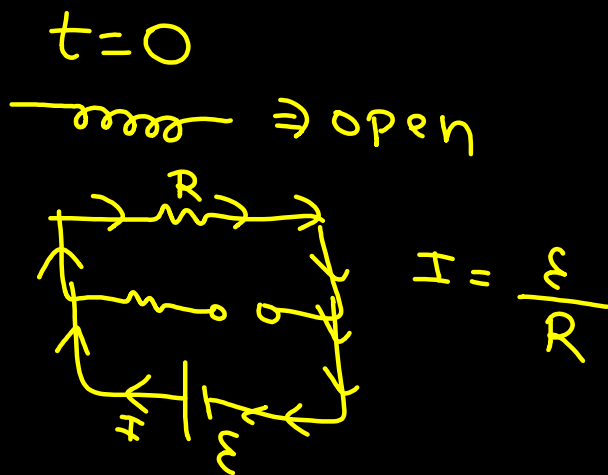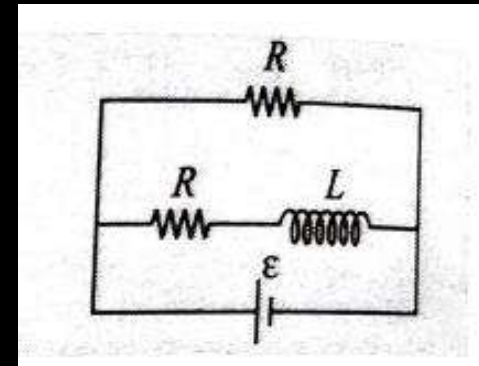

$=$


$I = \frac{\epsilon}{R/2}$

$I = \frac{2\epsilon}{R}$

An inductor coil stores 64 J of magnetic field energy and dissipates energy at the rate of 640 W when a current of 8A is passed through it. If this coil is joined across an ideal battery, find the time constant of the circuit in seconds.

- a. 0.4 b. 0.8 c. 0.125 ~~d. 0.2~~

See

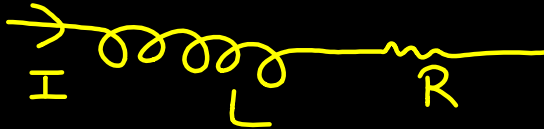Inductor Coil \Rightarrow  $I = 8A$

$$\left(\frac{1}{2} L I^2 \right) = 64$$

Power loss

$$I^2 R = 640$$

$$\tau = \frac{L}{R}$$

$$\frac{1}{2} L I^2 = 64$$

$$I = 8$$

$$\frac{1}{2} L (8)^2 = 64$$

$$L = 2$$

$$I^2 R = 640$$

$$(8)^2 R = 640$$

$$R = 10$$

$$\tau = \frac{L}{R}$$

$$= \frac{2}{10}$$

$$\tau = \underline{\underline{0.2 \text{ sec}}}$$

At $t = \tau$

At one time constant, find the

(i) current through the resistor $I = ?$

$$I^2 R = ?$$


(ii) rate at which energy is dissipated across the resistor

(iii) rate at which energy is stored in the inductor

$$\left(L \frac{dI}{dt} \right) I$$

(iv) power is delivered by the battery.

$$P = (\mathcal{E}) I$$

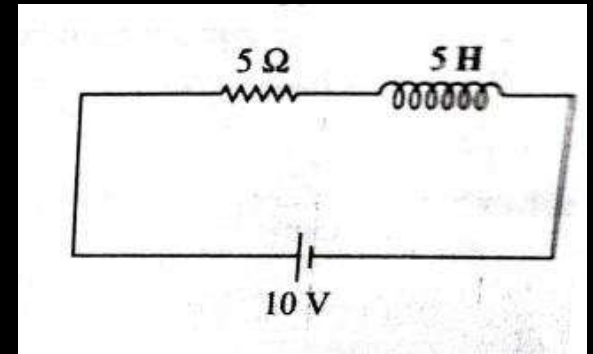

$$I_0 = \frac{\mathcal{E}}{R} = \frac{10}{5} = 2$$

$$\tau = \frac{L}{R} = \frac{5}{5} = 1$$

$$I = I_0(1 - e^{-t/\tau})$$

$$I = 2(1 - e^{-t})$$

① at $t = 1 \text{ sec}$

$$I = 2(1 - e^{-1})$$

$$= 2(1 - \frac{1}{e})$$

$$= 2(1 - \frac{1}{2.7})$$

$$= 2(0.63)$$


$$I = 1.26 \text{ A}$$

② $I^2 R$
 $(1.26)^2 (5)$

$$\underline{7.938 \text{ Watt}}$$

④ $P = \varepsilon I$
 $= (10)(1.26)$

$$P = 12.6$$

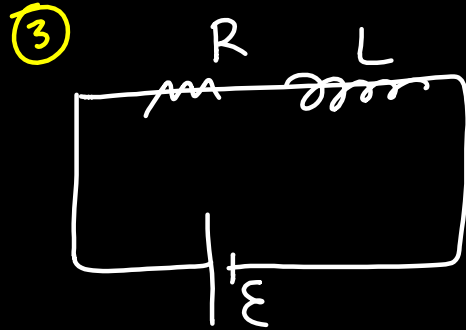

$$\text{Power given by Battery} = \text{Power lost from } R + \text{Power stored in } L$$

$$12.6 = 7.938 + \text{Power stored in } L$$

$$\underline{\underline{4.662 = \text{Power of Inductor}}}$$

or

$$\textcircled{3} \text{ Power of } L = L \left(\frac{dI}{dt} \right) I = L \left[2e^{-t} \right] \left[2(1-e^{-t}) \right]$$

$$\boxed{I = 2(1 - e^{-t})}$$

$$\frac{dI}{dt} = 2(0 - e^{-t}(-1))$$

$$L = 5$$

$$t = 1$$

$$\boxed{\frac{dI}{dt} = 2e^{-t}}$$

$$= 5 \left[2e^{-1} \right] 2(1 - e^{-1})$$

$$= \frac{20}{e} \left(1 - \frac{1}{e} \right)$$

$$= 20 \frac{(0.63)}{2.7}$$

$$= \underline{\underline{4.662}}$$


Jee
2021

An inductor of 10 mH is connected to a 20 V battery through a resistor of 10 k Ω and a switch. After a long time, when maximum current is set up in the circuit, the current is switched off. The current in the circuit after 1 μ s is $\frac{x}{100}$ mA. Then, x is equal to (Take, $e^{-1} = 0.37$)

$$L = 10 \text{ mH}$$

$$\mathcal{E}_{\text{mf}} = 20 \text{ V}$$


$$R = 10,000 \Omega$$

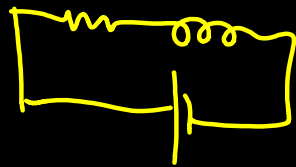

$$I_0 \checkmark$$

$$I_0 = \frac{20}{10000}$$

$$I_0 = 2 \text{ mA}$$

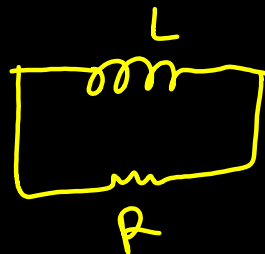

decay after 1 μ s find I

$$I = I_0 e^{-t/\tau}$$

$$I = (2 e^{-t/\tau}) \text{ mA}$$

$$\tau = \frac{L}{R} = \frac{10 \text{ m}}{10 \text{ k}} = 10^{-6}$$

At $t = 1 \mu\text{s}$

$$I = 2 e^{-\frac{1 \mu\text{s}}{1 \mu\text{s}}}$$


$$= 2 e^{-1}$$


$$= 2 \frac{1}{e} = \frac{2}{2.7} = 0.74 \text{ mA} = \frac{74}{100} \text{ mA}$$

$$\boxed{74 = x}$$

A transmitting station releases waves of wavelength 960 m. A capacitor of $2.56 \mu\text{F}$ is used in the resonant circuit. The self-inductance of coil necessary for resonance is $\times 10^{-8} \text{ H}$.

Dec 2021

Station 
 EM waves
 $\lambda = 960 \text{ m}$
 $f = \frac{c}{\lambda}$

coil 
 $C = 2.56 \mu$
 $L = ?$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Resonance
 \downarrow
 frequency match
 Karan

$$\frac{c}{\lambda} = \frac{1}{2\pi \sqrt{LC}}$$

$$\frac{3 \times 10^8}{960} = \frac{1}{2\pi \sqrt{L (2.56) \times 10^{-6}}}$$

$$L(2.56 \times 10^{-6}) = \frac{1}{4\pi^2} \frac{960 \times 960}{3 \times 10^8 \times 3 \times 10^8}$$

$$L = \frac{960 \times 960}{4 \times 3 \times 3 \times \pi^2 \times 10^8 \times 10^8 \times 2.56 \times 10^{-6}}$$

$$= \frac{96^2 \times 96^2 \times 10^2}{4 \times 9 \times 9 \times 7 \times 2.56} \times 10^{-8} = \underline{\underline{10 \times 10^{-8}}}$$