



Current Electricity

Electric Current

$$I_{av} \text{ (average current)} = \frac{\Delta q}{\Delta t}$$

$$I \text{ (instantaneous current)} = \lim_{\Delta t \rightarrow 0} \frac{\Delta q}{\Delta t} = \frac{dq}{dt}$$

SI unit : Ampere

Electric Current in a Conductor

$$I = nqAv_d$$


where I = current, n = number of charge carriers per unit volume, A = area of cross section, v_d = drift velocity.

$$\vec{v}_d = -\frac{e\vec{E}}{m}\tau$$

where e = charge of electron, m = mass of electron, \vec{E} = electric field, τ = relaxation time.

Current Density(J) and Mobility (μ)

$$\vec{J} = \frac{ne^2}{m}\tau\vec{E}$$

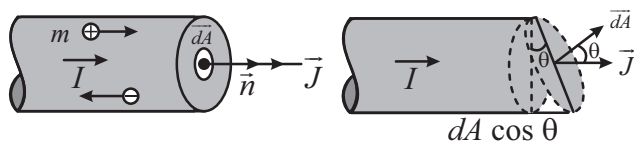

$$I = \int \vec{J} \cdot d\vec{A}$$

$$\mu = \frac{|v_d|}{E} = \frac{e\tau}{m}$$

(SI unit: m^2/Vs)

Electrical Resistance (R) and Ohm's Law

$$I = neAv_d = neA\left(\frac{eE}{m}\right)\tau$$

$$E = \frac{V}{l}$$

$$\text{So, } I = \left(\frac{ne^2\tau}{m}\right)\left(\frac{A}{l}\right) \times V = \left(\frac{A}{\rho l}\right) \times V = \frac{V}{R}$$

$$\Rightarrow V = IR$$

ρ is called resistivity (it is also called specific resistance) and

$$\rho = \frac{m}{ne^2\tau} = \frac{1}{\sigma}, \sigma \text{ is called conductivity}$$

SI Units: $R \rightarrow \text{ohm } (\Omega)$, $\rho \rightarrow \text{ohm-meter } (\Omega\text{-m})$, $\sigma \rightarrow \Omega^{-1}\text{m}^{-1}$.

Dependence of Resistance on Temperature:

$$R = R_0 (1 + \alpha (T - T_0)).$$

α = thermal coefficient of resistivity (**positive for conductors and negative for semi conductors and insulators**)

Electrical Power

$$P = VI$$

$$\text{Energy} = \int P dt$$

$$P = I^2 R = VI = \frac{V^2}{R}, \quad \text{Heat: } H = VIt = I^2 R t = \frac{V^2}{R} t$$


Kirchhoff's Laws

I. Law (Junction law or Nodal Analysis): This law is based on law of conservation of charge. It states that "The algebraic sum of the currents meeting at a junction is zero" or 'total currents entering a junction equals total current leaving the junction'.

$\Sigma I_{in} = \Sigma I_{out}$. It is also known as **KCL (Kirchhoff's current law)**.

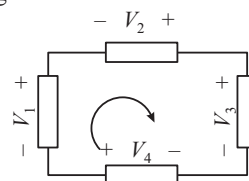II. Law (Loop analysis): The algebraic sum of all the voltages in closed circuit is zero.

$\Sigma IR + \Sigma EMF = 0$ in a closed loop. The closed loop can be traversed in any direction. While traversing a loop if higher potential point is entered, put a +ve sign in expression or if lower potential point is entered put a negative sign.




$-V_1 - V_2 + V_3 - V_4 = 0$. Boxes may contain resistor or battery or any other element (linear or non-linear).

It is also known as **KVL (Kirchhoff's voltage law)**.

Combination of Resistances


I. Resistances in Series:

$$R = R_1 + R_2 + R_3 + \dots + R_n$$

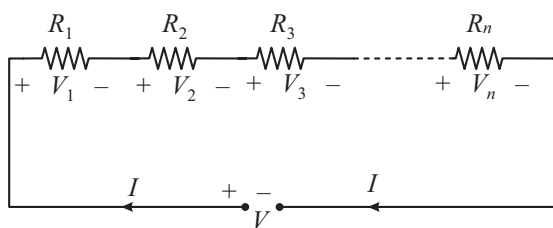


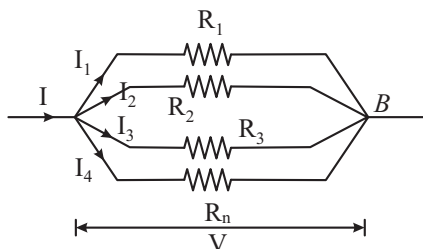II. Resistances in Parallel:

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$



Wheatstone Network

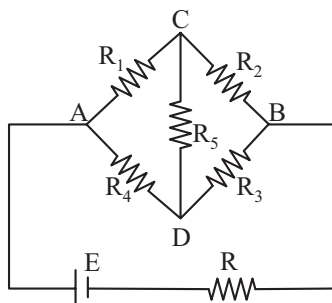


Current through the R_5 is zero (null point or balance point) if

$$\frac{R_1}{R_4} = \frac{R_2}{R_3}$$

Grouping of Cells

I. Cells in Series:

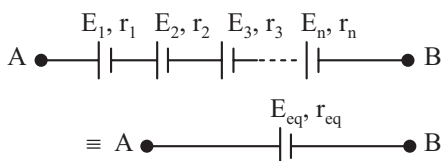


Equivalent EMF $E_{eq} = E_1 + E_2 + \dots + E_n$ [write EMF's with polarity]

Equivalent internal resistance $r_{eq} = r_1 + r_2 + r_3 + r_4 + \dots + r_n$

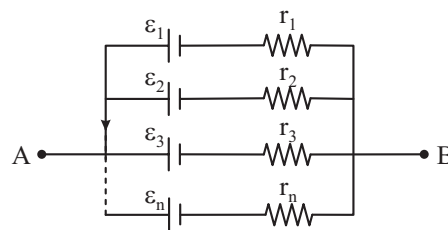II. Cells in Parallel:


$$E_{eq} = \frac{\frac{\epsilon_1}{r_1} + \frac{\epsilon_2}{r_2} + \dots + \frac{\epsilon_n}{r_n}}{\frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}} \quad [\text{Use emf with polarity}]$$

$$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2} + \dots + \frac{1}{r_n}$$




Ammeter

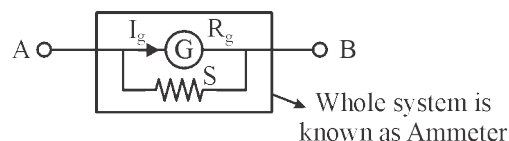A shunt (small resistance) is connected in parallel with galvanometer to convert it into ammeter. An ideal ammeter has zero resistance



Ammeter is represented as follows :

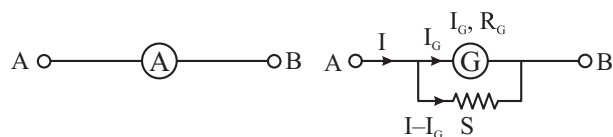


If maximum value of current to be measured by ammeter is I then $I_G \cdot R_G = (I - I_G) S$

$$S = \frac{I_G \cdot R_G}{I - I_G} \Rightarrow S = \frac{I_G \times R_G}{I} \quad (\text{if } I \gg I_G).$$

where, I = Maximum current that can be measured using the given ammeter.

Voltmeter

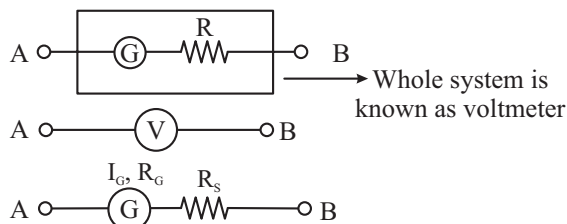A high resistance is put in series with galvanometer. It is used to measure potential difference across a resistor in a circuit.




For maximum potential difference

$$V = I_G \cdot R_S + I_G R_G$$

$$\text{If } R_G \ll R_S \Rightarrow R_S \approx \frac{V}{I_G}$$

Potentiometer

Primary circuit

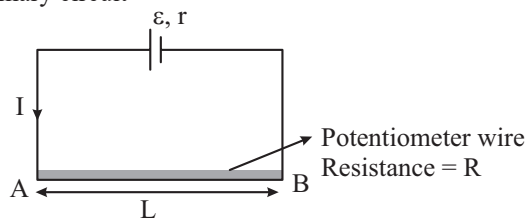

$$I = \frac{\varepsilon}{r + R}; \quad V_A - V_B = \frac{\varepsilon}{R + r} \cdot R$$

Potential gradient (x) → Potential difference per unit length of wire

$$x = \frac{V_A - V_B}{L} = \frac{\varepsilon}{R + r} \cdot \frac{R}{L}$$

Applications of potentiometer

(a) To find emf of unknown cell and compare emf of two cells.

In case I,

In figure, (1) is joint to (2) then balance length = l_1


$$\varepsilon_1 = x l_1 \quad \dots(i)$$

In case II,

In figure, (3) is joint to (2) then balance length = l_2

$$\varepsilon_2 = x l_2 \quad \dots(ii)$$

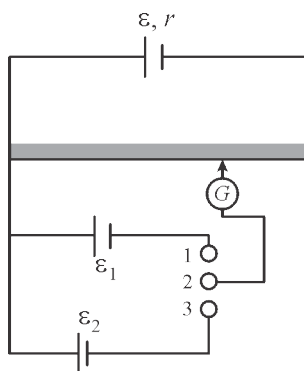
$$\frac{\varepsilon_1}{\varepsilon_2} = \frac{l_1}{l_2}$$



If any one of ε_1 or ε_2 is known the other can be found.

If x is known then both ε_1 and ε_2 can be found.

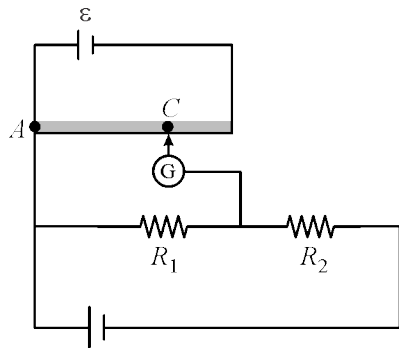(b) To find current if resistance is known



$$V_A - V_C = x l_1$$



$$I R_1 = x l_1$$

$$I = \frac{x l_1}{R_1}$$

Similarly, we can find the value of R_2 also.

Potentiometer is ideal voltmeter because it does not draw any current from circuit at the balance point.

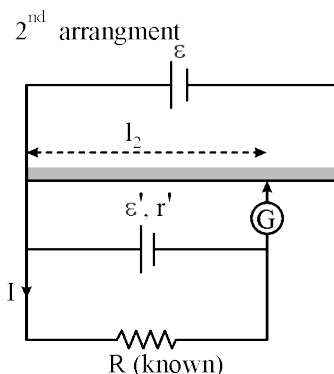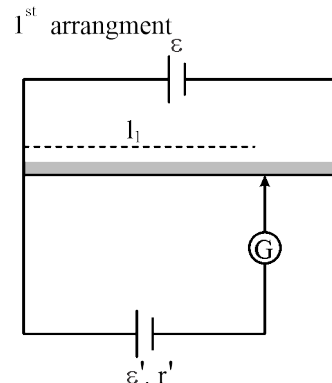(c) To find the internal resistance of cell.



$$\text{By first arrangement} \quad \varepsilon' = x l_1 \quad \dots(i)$$

$$\text{By second arrangement} \quad I R = x l_2 \quad \dots(ii)$$

$$I = \frac{x l_2}{R}, \text{ Also } I = \frac{\varepsilon'}{r' + R}$$

$$\therefore \frac{\varepsilon'}{r' + R} = \frac{x l_2}{R} \Rightarrow \frac{x l_1}{r' + R} = \frac{x l_2}{R}$$

$$r' = \left[\frac{l_1 - l_2}{l_2} \right] R$$

Metre Bridge

It is used to measure unknown resistance.


If $AB = l$ cm, then $BC = (100 - l)$ cm.

Resistance of the wire between A and B , $R \propto l$

[\because Specific resistance ρ and cross-sectional area A are same for whole of the wire]

$$\text{or } R = \sigma l \quad \dots(i)$$

where σ is resistance per cm of wire.

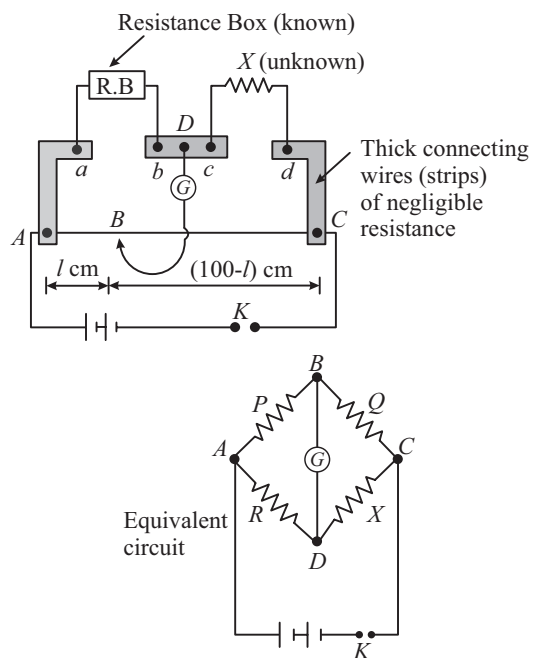

If P is the resistance of wire between A and B , then

$$P \propto l \Rightarrow P = \sigma (l)$$

Similarly, if Q is resistance of the wire between B and C , then

$$Q \propto 100 - l \Rightarrow Q = \sigma (100 - l) \quad \dots(ii)$$

Dividing (i) by (ii),

$$\frac{P}{Q} = \frac{l}{100 - l}$$

Applying the condition for balanced Wheatstone bridge, we get $RQ = PX$

$$\therefore X = R \frac{Q}{P} \quad \text{or} \quad X = \frac{100 - l}{l} R$$

Since R and l are known, therefore, the value of X can be calculated.