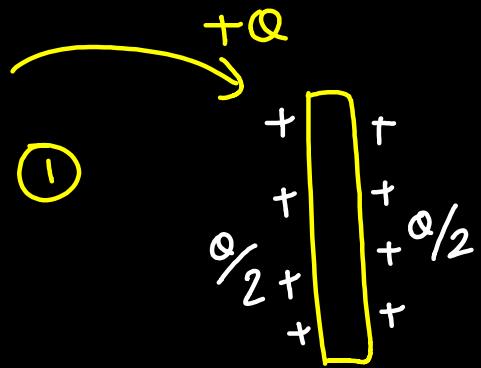


## Today's Target


- Charge Distribution in Conducting Plates
- Capacitance
- Types of Capacitors
- Capacitor as Circuit Element
- Redistribution of Charges
- Combination of Capacitors
- Kirchoff's Law & Circuit Solving
- Dielectrics
- R-C circuits

## # Conducting Plates



$E$  due to Non Conducting

②

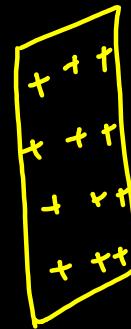

$$E = \frac{\sigma}{2\epsilon_0}$$


$$\sigma = \left( \frac{\text{charge}}{\text{area}} \right)$$

Conducting Plate

$$\begin{array}{c} + \\ + \\ + \\ \sigma \end{array} \rightarrow \frac{\sigma}{2\epsilon_0} \rightarrow \frac{\sigma}{\epsilon_0} \Rightarrow \left( \frac{\sigma}{\epsilon_0} \right)$$

Conducting
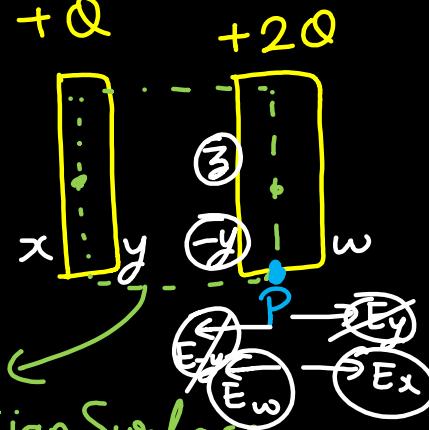
$$+ \boxed{r} + \quad E = \frac{\sigma}{\epsilon_0}$$



gaussian Surface

$$\phi_{\text{total}} = 0$$

$$Q_{\text{enclosed}} = 0$$

$$y + z = 0$$

$$z = -y$$

$$x + y = Q$$


$$z + w = 2Q$$

① gauss law

Facing Surfaces  
Equal & Opp

②  $E_{\text{net inside conductor}} = 0$


$x = w$   
Outer surface charge  
Same.

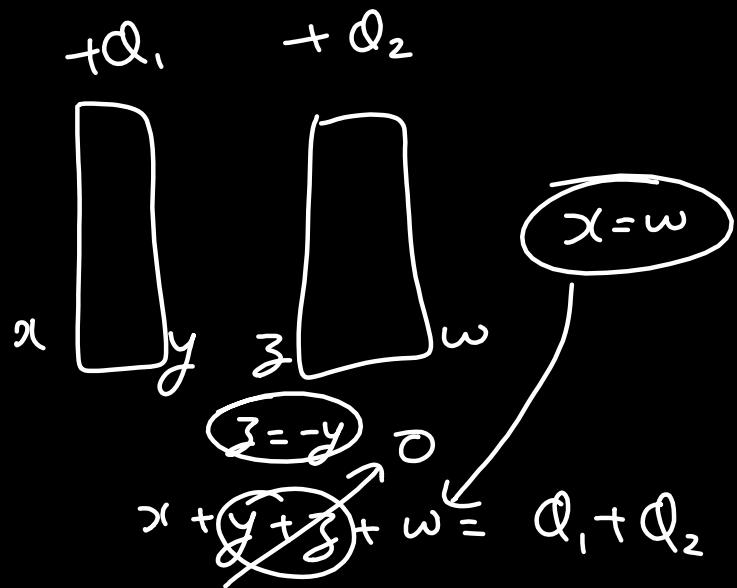

$$\text{Outer} = \frac{\text{total}}{2}$$

$$2x = Q_1 + Q_2$$


$$x = \frac{Q_1 + Q_2}{2}$$

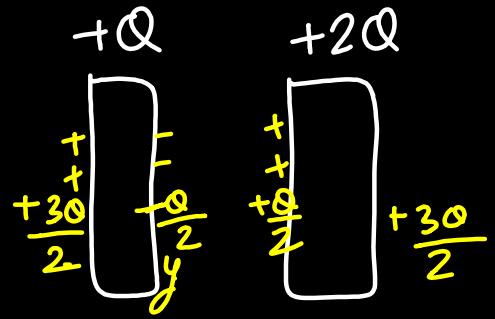

$$\text{outer} = \frac{Q + 2Q}{2} = \frac{3Q}{2}$$

$$\frac{3Q}{2} + y = Q$$


$$y = -\frac{Q}{2}$$

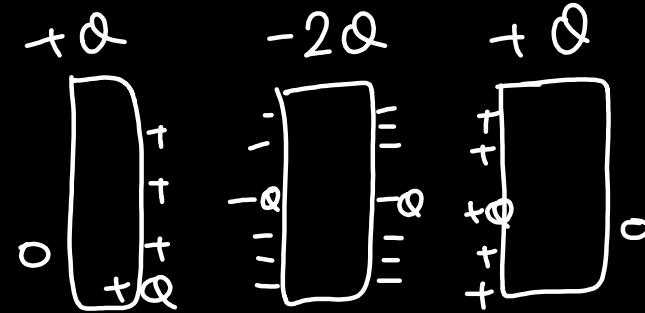

$$\text{outer} = \frac{Q - 2Q + Q}{2} = 0$$

$$\textcircled{O} \quad |\Delta V| = |E \cdot d|$$


when  $E$  is constant

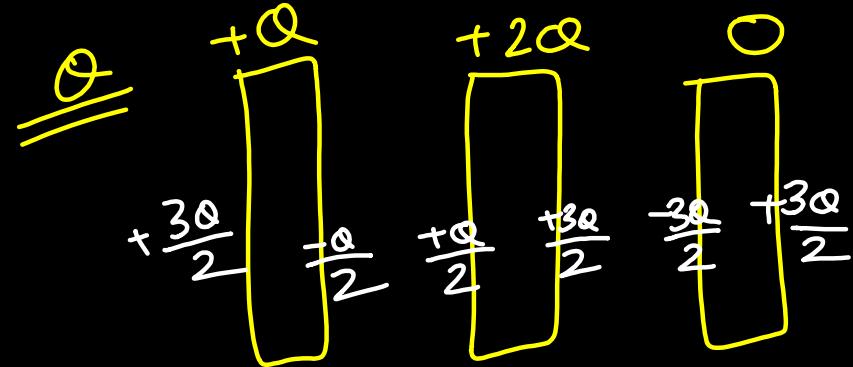

$$\textcircled{O} \quad |\Delta V| = \left| \int \vec{E} \cdot \vec{dx} \right|$$

when  $E$  is variable.


$\frac{Q}{A}$

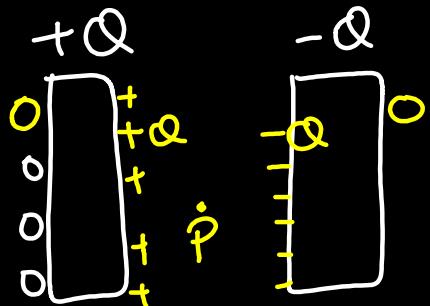

$E \text{ at } P = ?$



$$+ \rightarrow E_+ = \sigma / 2\epsilon_0$$
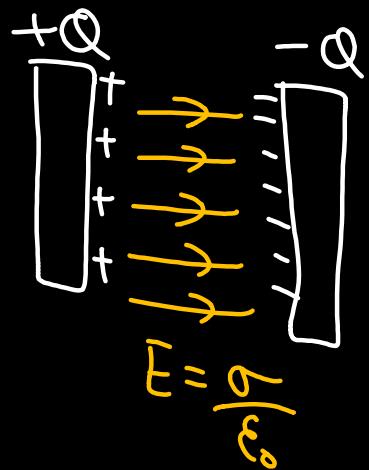
$$\rightarrow E_- = \sigma / 2\epsilon_0 \Rightarrow \sigma / \epsilon_0$$



$$\sigma = Q / A$$

when one plate is Earthed

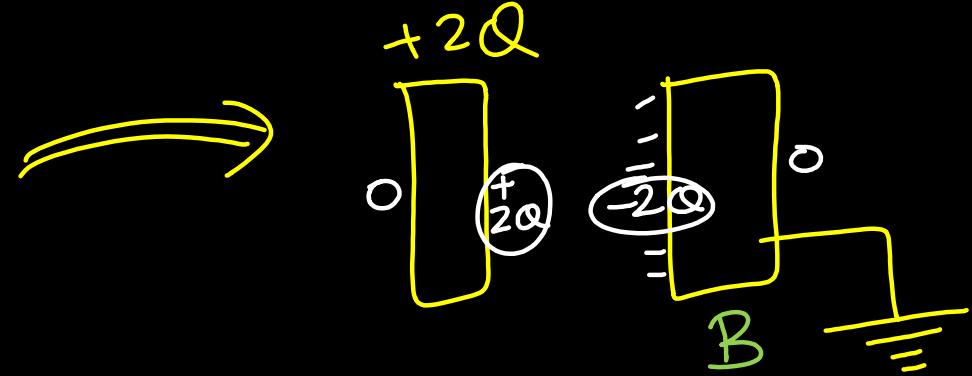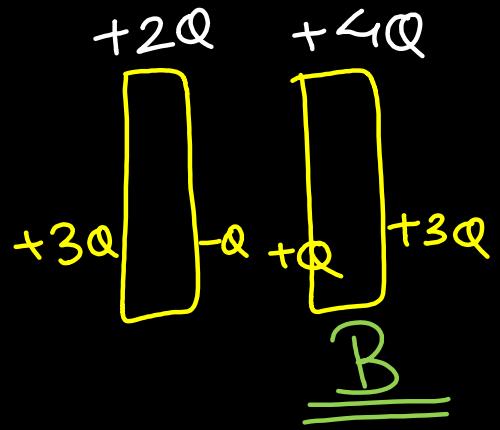

# total charge of system becomes = 0


Charge flow From Plate B to Earth  $\Rightarrow +6Q$

$+4Q$   
initial

$-2Q$   
final

B  
↓  
Earth

Two plates Earth

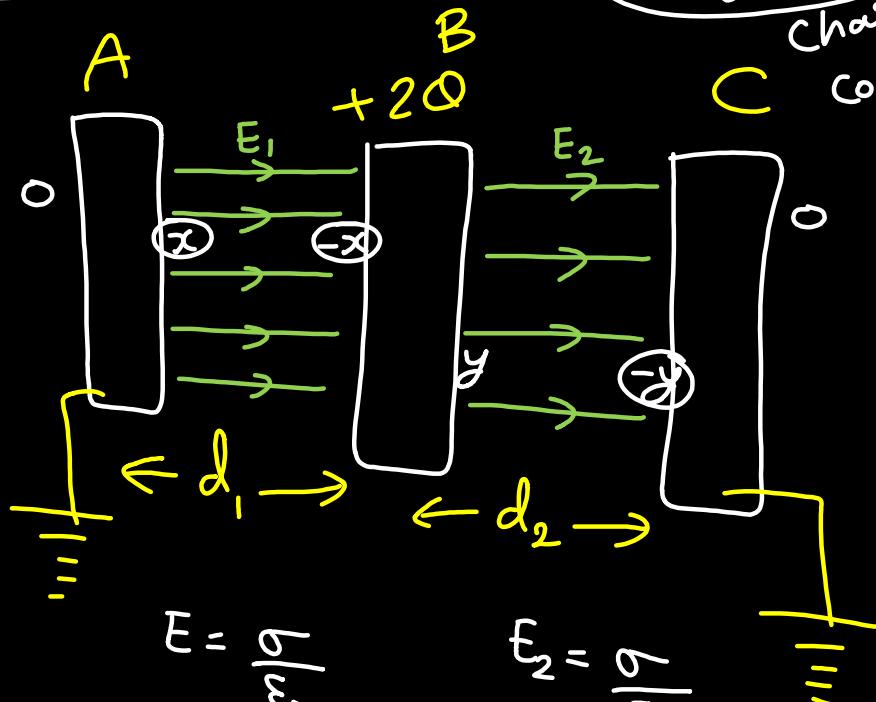

$$E = \frac{\sigma}{\epsilon_0}$$

$$E_1 = \frac{x}{A\epsilon_0}$$

$$E_2 = \frac{\sigma}{\epsilon_0}$$

$$= \frac{y}{A\epsilon_0}$$

$$-x + y = 2Q$$

charge  
conservation

$$V_A = 0$$

$$V_C = 0$$

$$V_A - V_C = 0$$

$$\Delta V_{AC} = 0$$

$$E_1 d_1 + E_2 d_2 = 0$$

$$\frac{x d_1}{A \epsilon_0} + \frac{y d_2}{A \epsilon_0} = 0$$

## CAPACITANCE

Concept of Capacitance - Capacitance of a conductor is a measure of ability of the conductor to store charge on it. When a conductor is charged then its potential rises. The increase in potential is directly proportional to the charge given to the conductor.

$$Q \propto V \Rightarrow Q = CV$$


The constant C is known as the capacitance of the conductor.

$$\text{Capacitance is a scalar quantity with dimension } C = \frac{Q}{V} = \frac{Q^2}{W} = \frac{A^2 T^2}{M^1 L^2 T^{-2}} = M^{-1} L^{-2} T^4 A^2$$

Unit :- farad, coulomb/volt

The capacity of a conductor is independent of the charge given or its potential raised. It is also independent of nature of material and thickness of the conductor.

## Capacitor

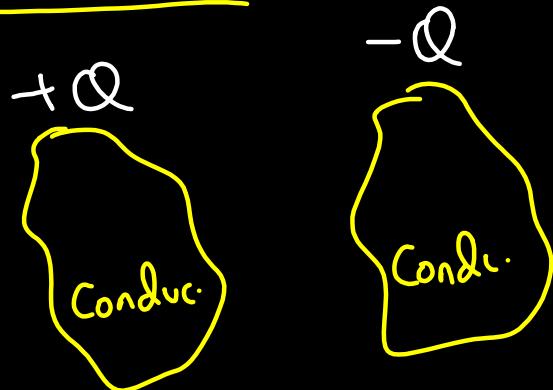


$$Q \propto \Delta V$$

$$Q = C \Delta V$$

Capacitance .

$$\begin{aligned} \text{Potential} &= \frac{PF}{\text{charge}} \\ &= \frac{M L^2 T^{-2}}{AT} \end{aligned}$$
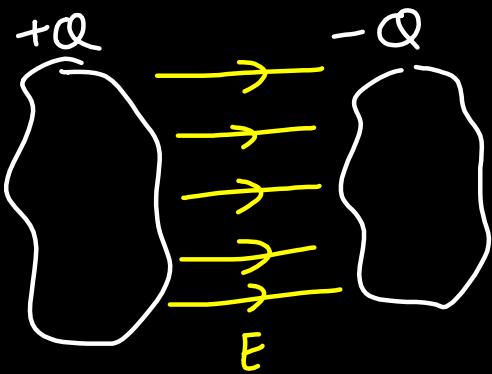
$$\begin{aligned} C &= \frac{Q}{\Delta V} & \text{unit} \\ &= \frac{[AT]}{\frac{[ML^2 T^{-2}]}{[AT]}} & = [A^2 T^4 M^{-1} L^{-2}] \end{aligned}$$




$$C = \frac{Q}{\Delta V}$$

$C$  does not depend upon  
# charge given  
#  $\Delta V$

$$\infty V = 0$$

## isolated Conductor

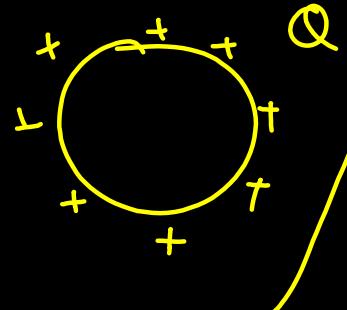

$$C = \frac{Q}{V}$$

$$C = \frac{Q}{(KQ/R)}$$

$$V = \frac{KQ}{R}$$

$$K \rightarrow \frac{1}{4\pi\epsilon_0}$$

$$C = \frac{R}{K}$$

$$C = 4\pi\epsilon_0 R$$


The Capacitance of a Spherical Conductor - When a charge  $Q$  is given to a isolated spherical conductor then its potential rises.

$$V = \frac{1}{4\pi\epsilon_0} \frac{Q}{R} \Rightarrow C = \frac{Q}{V} = \boxed{4\pi\epsilon_0 R} \star$$

If conductor is placed in a medium then  $C_{\text{medium}} = 4\pi\epsilon R = 4\pi\epsilon_0\epsilon_r R$

Capacitance depends upon :

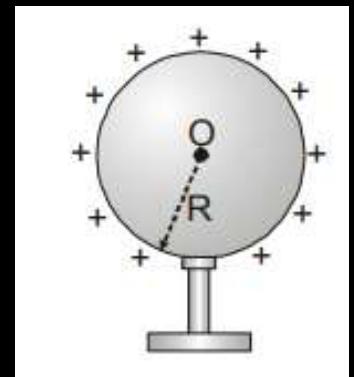- Size and Shape of Conductor ✓
- Surrounding medium ✓
- Presence of other conductors nearby ✓




- **Condenser/Capacitor** - The pair of conductor of opposite charges on which sufficient quantity of charge may be accommodated is defined as condenser.

$$\Delta V = V_+ - V_-$$


$$= V_A - V_B$$

$C = \frac{Q}{\Delta V}$

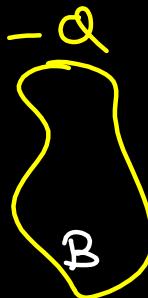

$$\Delta V = |E d|$$


$$= \left| \int \vec{E} \cdot d\vec{r} \right|$$

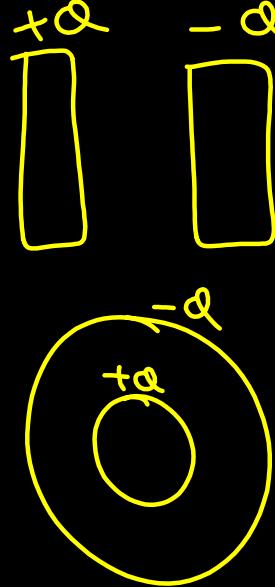

**Statement 1:** It is not possible to make a sphere of capacity 1 farad using a conducting material.

**Statement 2:** It is possible for earth as its radius is  $6.4 \times 10^6$  m. [Online May 26, 2012]

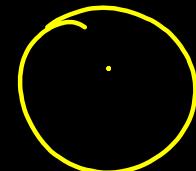- (a) Statement 1 is true, Statement 2 is true, Statement 2 is the correct explanation of Statement 1.
- (b) Statement 1 is false, Statement 2 is true.
- (c) Statement 1 is true, Statement 2 is true, Statement 2 is not the correct explanation of Statement 1.
- ~~(d)~~ Statement 1 is true, Statement 2 is false.



$$C = 4\pi\epsilon_0 R = 1 \text{ Farad}$$

$$R = 6400 \text{ km}$$

$$\epsilon_0 = 8.85 \times 10^{-12}$$


earth

$$C = 4\pi\epsilon_0 R$$

$$= 4\pi(8.85 \times 10^{-12})(6400 \times 10^3)$$

$$C = 711 \mu F$$

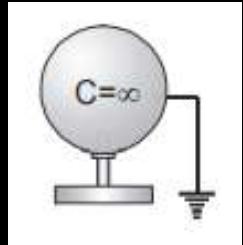- As the potential of the Earth is assumed to be zero, capacity of earth or a conductor connected to earth will be infinite  $C = \frac{q}{V} = \frac{q}{0} = \infty$
- Actual capacity of the Earth  $C = 4\pi\epsilon_0 R = \frac{1}{9\times 10^9} \times 64 \times 10^5 = 711\mu F$



## Spherical Capacitor

Outer sphere is earthed - When a charge  $Q$  is given to inner sphere it is uniformly distributed on its surface, a charge  $-Q$  is induced on inner surface of outer sphere. The charge  $+Q$  induced on outer surface of outer sphere flows to earth as it is grounded.

$$E = 0 \text{ for } r < R_1 \text{ and } E = 0 \text{ for } r > R_2$$


Potential of inner sphere  $V_1$





As outer surface is earthed so potential  $V_2 = 0$

Potential difference between spheres  $V = V_1 - V_2$

$$\text{So } C \text{ between both the spheres} = \frac{Q}{V} = 4\pi\epsilon_0 \frac{R_1 R_2}{R_2 - R_1} \text{ (in air or vacuum)}$$
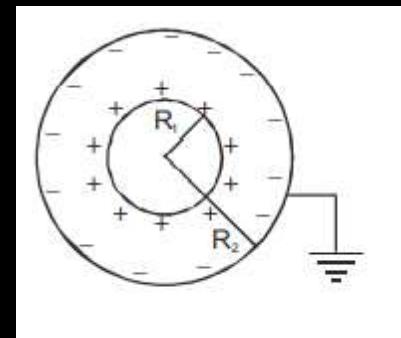
$$\text{In presence of medium between spheres } C = 4\pi\epsilon_r\epsilon_0 \frac{R_1 R_2}{R_2 - R_1}$$



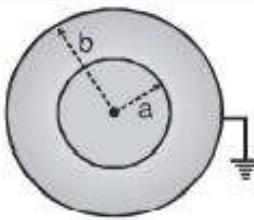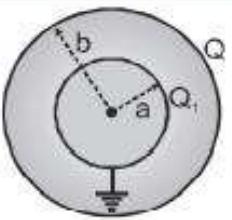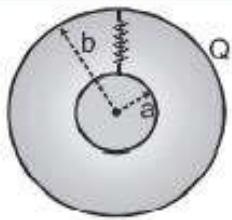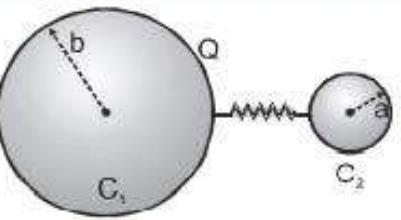Spherical capacitor outer is earthed	Inner is earthed and outer is given a charge	Connected and outer is given a charge	Connected spheres
 $C = \frac{4\pi\epsilon_0 ab}{b - a}$ $(b > a)$	 $C = \frac{4\pi\epsilon_0 b^2}{b - a}$ $(b > a)$	 $C = 4\pi\epsilon_0 b$	 $C = C_1 + C_2$ $C = 4\pi\epsilon_0(a+b)$

Capacitance of an isolated conducting sphere of radius  $R_1$  becomes  $n$  times when it is enclosed by a concentric conducting sphere of radius  $R_2$  connected to earth. The ratio of

their radii  $\left(\frac{R_2}{R_1}\right)$  is:

- (A)  $\frac{n}{n-1}$
- (B)  $\frac{2n}{2n+1}$
- (C)  $\frac{n+1}{n}$
- (D)  $\frac{2n+1}{n}$

JEE MAINS 2022

$$\frac{R_2}{R_1} = \frac{n}{n-1}$$


$$C_1 = \frac{4\pi\epsilon_0 R_1}{1}$$

$$C' = n C_1$$

$$\frac{4\pi\epsilon_0(R_2 R_1)}{(R_2 - R_1)} = n \left( \frac{4\pi\epsilon_0 R_1}{1} \right)$$

$$\begin{aligned} R_2 &= nR_2 - nR_1 \\ nR_1 &= R_2(n-1) \end{aligned}$$

$$\frac{R_2}{R_2 - R_1} = n$$

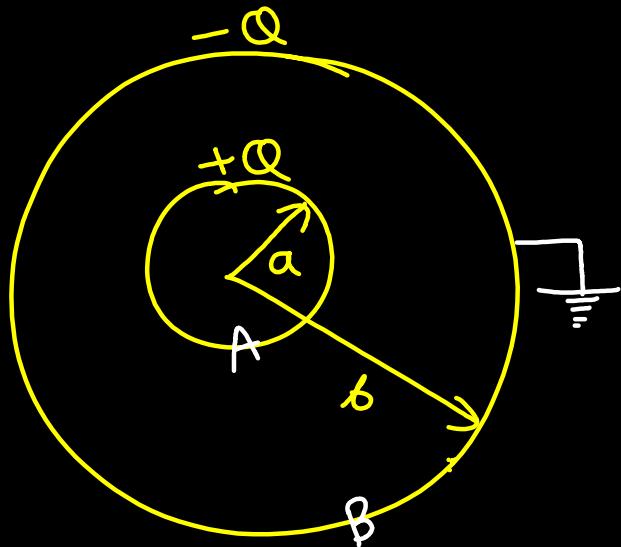


$$C = \frac{Q}{\Delta V}$$

$$C = \frac{Q}{kQ \left( \frac{1}{a} - \frac{1}{b} \right)}$$

$$C = \frac{1}{k} \frac{(ab)}{(b-a)}$$

$$V_A = \frac{kQ}{a} + \frac{k(-Q)}{b} = kQ \left( \frac{1}{a} - \frac{1}{b} \right)$$
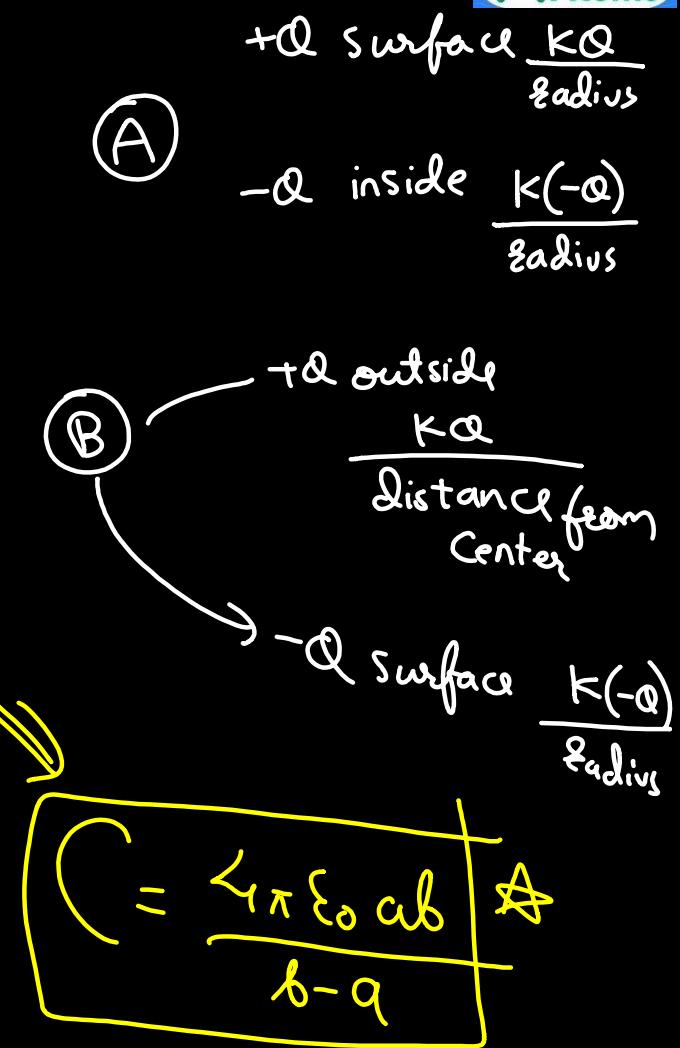
$$V_B = \frac{kQ}{b} + \frac{k(-Q)}{b} = 0$$



## Cylindrical Capacitor

When a charge  $Q$  is given to inner cylinder it is uniformly distributed on its surface.


A charge  $-Q$  is induced on inner surface of outer cylinder. The charge  $+Q$  induced on outer surface of outer cylinder flows to earth as it is grounded


$$\text{Electrical field between cylinders } E = \frac{\lambda}{2\pi\epsilon_0 r} = \frac{Q/\ell}{2\pi\epsilon_0 r}$$

Potential difference between both cylindrical surfaces

$$V = \int_{R_1}^{R_2} \frac{Q}{2\pi\epsilon_0 r \ell} dr = \frac{Q}{2\pi\epsilon_0 \ell} \ln \left( \frac{R_2}{R_1} \right). \quad \text{Capacitance } C = \frac{Q}{V} = \frac{2\pi\epsilon_0 \ell}{\log_e(R_2/R_1)}$$
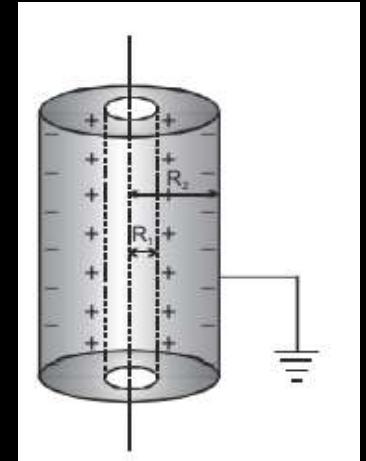
$$\text{In presence of medium } C = \frac{2\pi\epsilon_0 \epsilon_r \ell}{\log_e(R_2/R_1)}$$



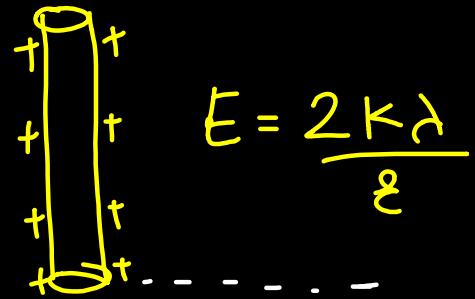

$$E = \frac{2k\lambda}{\epsilon}$$

$$\lambda = \frac{Q}{\text{length}}$$


$$\lambda(\text{length}) Q$$

$$\Delta V = \left| \int \vec{E} \cdot d\vec{r} \right| = \int \frac{2k\lambda}{\epsilon} dr$$

$$= 2k\lambda \log \epsilon \Big]_{\epsilon_1}^{\epsilon_2}$$

$$= 2k\lambda \log \epsilon_2 - \log \epsilon_1$$
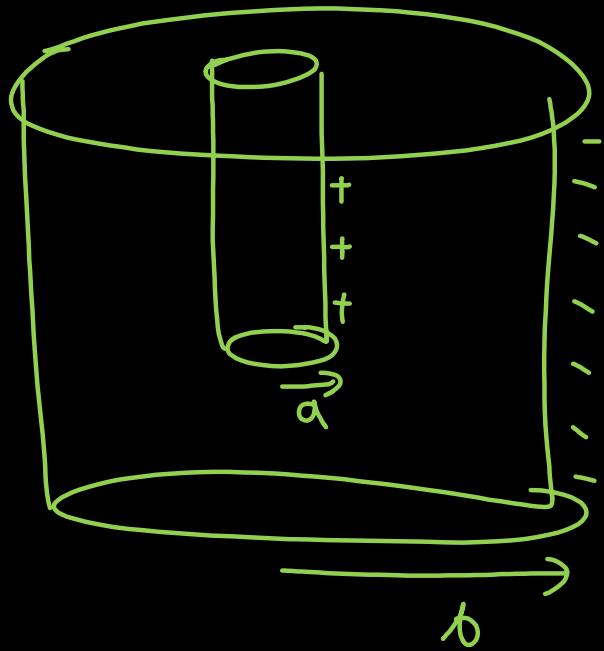
$$\Delta V = \boxed{2k\lambda \ln \left( \frac{\epsilon_2}{\epsilon_1} \right)}$$



$$Q = \lambda l$$

$$\Delta V = 2k \lambda \ln\left(\frac{b}{a}\right)$$

$$C = \frac{Q}{\Delta V} = \frac{\lambda l}{2k \times \ln\left(\frac{b}{a}\right)}$$

$$= \frac{4\pi \epsilon_0 l}{2 \ln\left(\frac{b}{a}\right)}$$

$C = \frac{2\pi \epsilon_0 l}{\ln(b/a)}$

## DIFFERENT TYPES OF CAPACITORS

### Parallel Plate Capacitor

**(i) Capacitance** - It consists of two metallic plates M and N each of area A at separation d. Plate M is positively charged and plate N is earthed. If  $\epsilon_r$  is the dielectric constant of the material medium and E is the field at a point P that exists between the two plates, then

**I step** : Finding electric field

$$E = E_+ + E_- = \frac{\sigma}{2\epsilon} + \frac{\sigma}{2\epsilon} = \frac{\sigma}{\epsilon} = \frac{\sigma}{\epsilon_0 \epsilon_r} [\epsilon = \epsilon_0 \epsilon_r]$$


**II step** : Finding potential difference

$$V = Ed = \frac{\sigma}{\epsilon_0 \epsilon_r} d = \frac{qd}{A\epsilon_0 \epsilon_r} \left( \because E = \frac{V}{d} \text{ and } \sigma = \frac{q}{A} \right)$$

**III step** : Finding capacitance  $C = \frac{q}{V} = \frac{\epsilon_r \epsilon_0 A}{d}$

If medium between the plates is air or vacuum, then  $\epsilon_r = 1 \Rightarrow C_0 = \frac{\epsilon_0 A}{d}$

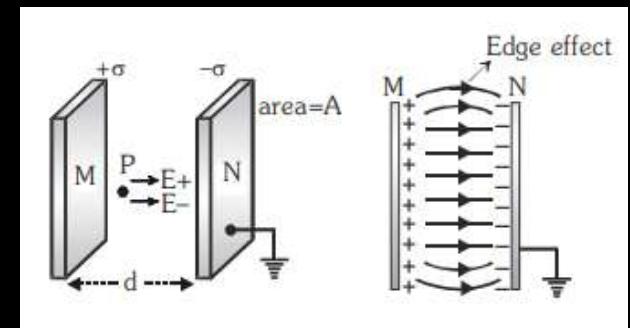so  $C = \epsilon_r C_0 = K C_0$  (where  $\epsilon_r = K$  = dielectric constant)



(ii) Force between the plates - The two plates of capacitor attract each other because they are oppositely charged.

$$\text{Electric field due to positive plate } E = \frac{\sigma}{2\epsilon_0} = \frac{Q}{2\epsilon_0 A}$$

$$\text{Force on negative charge-}Q \text{ is } F = -QE = -\frac{Q^2}{2\epsilon_0 A}$$

$$\text{Magnitude of force } F = \frac{Q^2}{2\epsilon_0 A} = \frac{1}{2} \epsilon_0 A E^2$$

$$\text{Force per unit area or energy density or electrostatic pressure} = \frac{F}{A} = u = p = \frac{1}{2} f_0 F^2$$

Let  $C$  is capacitance of a conductor. On being connected to a battery. It charges to a potential  $V$  from zero potential. If  $q$  is charge on the conductor at that time then  $q = CV$ . Let battery supplies small amount of charge  $dq$  to the conductor at constant potential  $V$ . Then small amount of work done by the battery against the force exerted by existing charge is


$$dW = Vdq = \frac{q}{C} dq \Rightarrow W = \int_0^Q \frac{q}{C} dq = \frac{1}{C} \left[ \frac{q^2}{2} \right]_0^Q \Rightarrow W = \frac{Q^2}{2C}$$


where  $Q$  is the final charge acquired by the conductor. This work done is stored as potential energy, so

$$U = \frac{Q^2}{2C} = \frac{1}{2} \frac{(CV)^2}{C} = \frac{1}{2} CV^2 = \frac{1}{2} \left( \frac{Q}{V} \right) V^2 = \frac{1}{2} QV$$


$$\therefore U = \frac{Q^2}{2C} = \frac{1}{2} CV^2 = \frac{1}{2} QV$$

- If one of the plates of parallel plate capacitor slides relatively than C decrease (As overlapping area decreases).
- If both the plates of parallel plate capacitor are touched each other resultant charge and potential became zero.
- Electric field between the plates of a capacitor is shown in figure. Non-uniformity of electric field at the boundaries of the plates is negligible if the distance between the plates is very small as compared to the length of the plates.

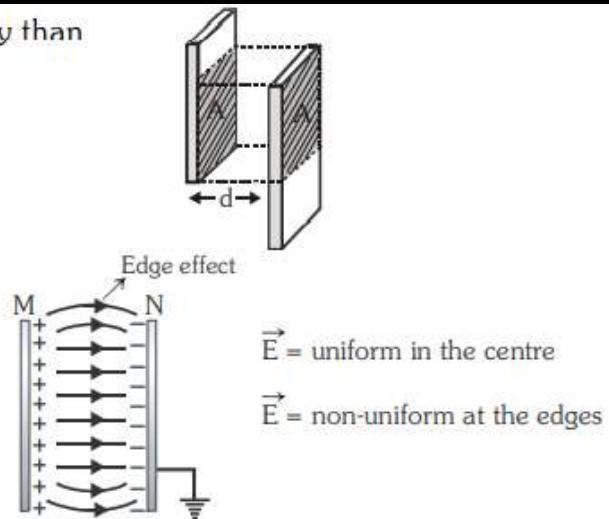

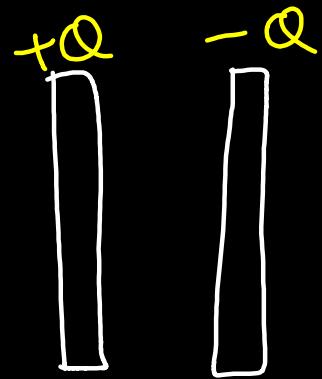
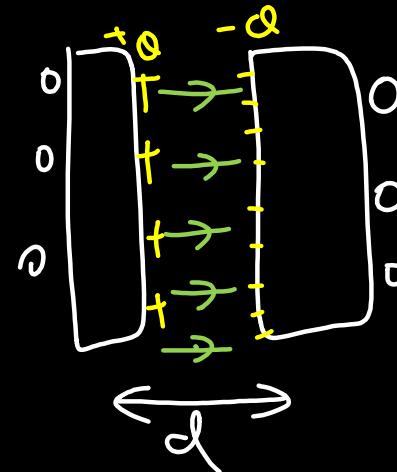
$$\sigma = \frac{\text{charge}}{\text{area}}$$




$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0}$$

$$\Delta V = E d = \frac{\sigma d}{\epsilon_0} = \frac{Q d}{A \epsilon_0}$$



$$C = \frac{Q}{\Delta V} = \frac{Q}{d / A \epsilon_0}$$

$$C = \frac{A \epsilon_0}{d}$$

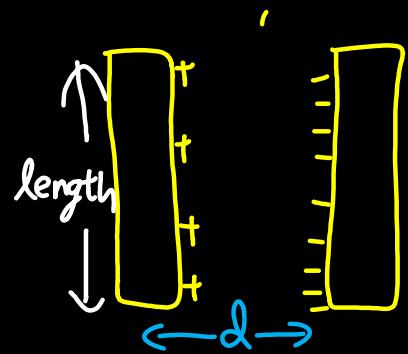
$$C = \frac{Q}{\Delta V} = \frac{A \epsilon_0}{d}$$



Area of plates = (length) (width)

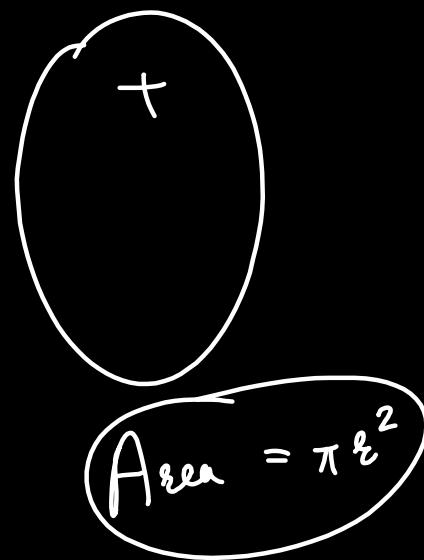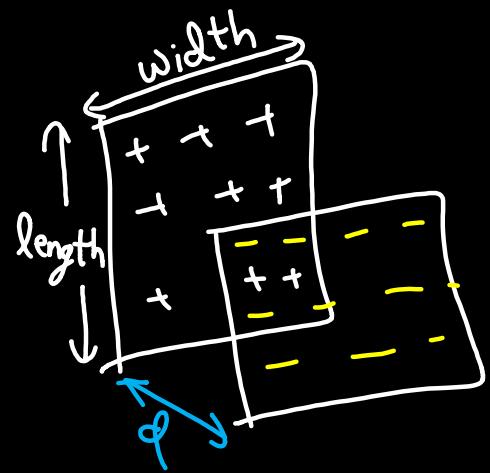

## Energy of Capacitor

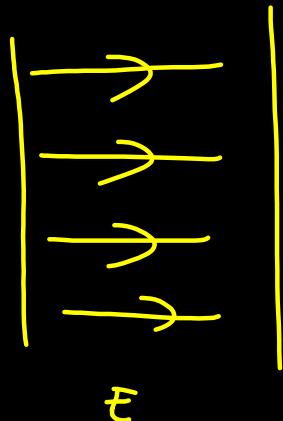

$$\text{energy density} = \frac{\text{energy}}{\text{Vol}} = \frac{1}{2} \epsilon_0 E^2$$

$$\text{Vol} = Ad$$

$$\text{energy} = \frac{1}{2} \underline{\epsilon_0} \underline{E^2} \underline{Ad}$$

$$C = \frac{Q}{\Delta V}$$

$$\frac{A \epsilon_0}{d} = C$$


$$A \epsilon_0 = \underline{\underline{Cd}}$$

$$\text{energy} = \frac{1}{2} \underline{\underline{E^2}} \underline{\underline{d^2}} C$$

$$\Delta V = Ed$$

$$U = \frac{1}{2} C (\Delta V)^2 = \frac{Q^2}{2C} = \frac{1}{2} Q \Delta V$$

## Force b/w Plates

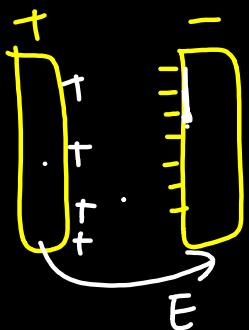

$$\left( + \atop + \atop + \right) \xrightarrow{\sigma} \frac{\sigma}{2\epsilon_0}$$

$$\text{force} = (\text{charge})(\text{field})$$

$$= (Q \text{ of plate 2}) \left( \begin{array}{l} \text{field due to} \\ \text{1 over 2} \end{array} \right)$$

$$F = Q \frac{\sigma}{2\epsilon_0} = \frac{Q^2}{2A\epsilon_0} = \frac{\sigma^2 A}{2\epsilon_0}$$

$$\frac{\text{Force}}{\text{area}} = \text{Pressure} = \frac{\sigma^2}{2\epsilon_0}$$

If Medium is Changed

Vaccum

$\epsilon_0$


medium

$\epsilon_0 \epsilon_r$

$\rightarrow$  relative  
permittivity

$$k_{H_2O} = 81$$

$$k_{\text{metal}} = \infty$$

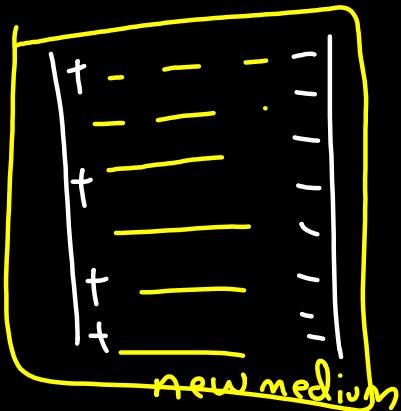


$\partial \epsilon$

$\epsilon_0 k$

$\rightarrow$  dielectric  
constant

$$C = \frac{A \epsilon_0}{d}$$
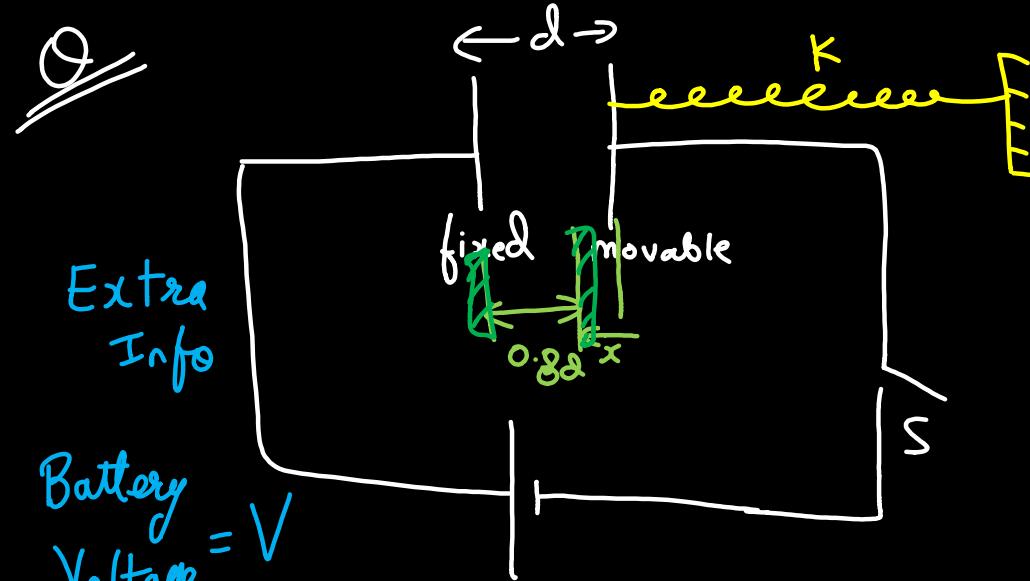
$$C'_{\text{new}} = \frac{A \epsilon_0 \epsilon_r}{d} = \frac{A \epsilon_0 k}{d} = k C_{\text{vacuum}}$$



$$C = \frac{Q}{V}$$

$$Q = C V \\ = \left( \frac{A \epsilon_0}{0.8d} \right) V$$

$$\sigma = \frac{Q}{A}$$

$\left| \begin{array}{l} F_{\text{electro}} \\ \rightarrow k_x \end{array} \right.$


initially uncharged & natural  
 $S$  close

Then distance b/w plates  
 in new equilibrium is  $(0.8d)$

$$x = 0.2d$$

$$k(0.2d) = F$$
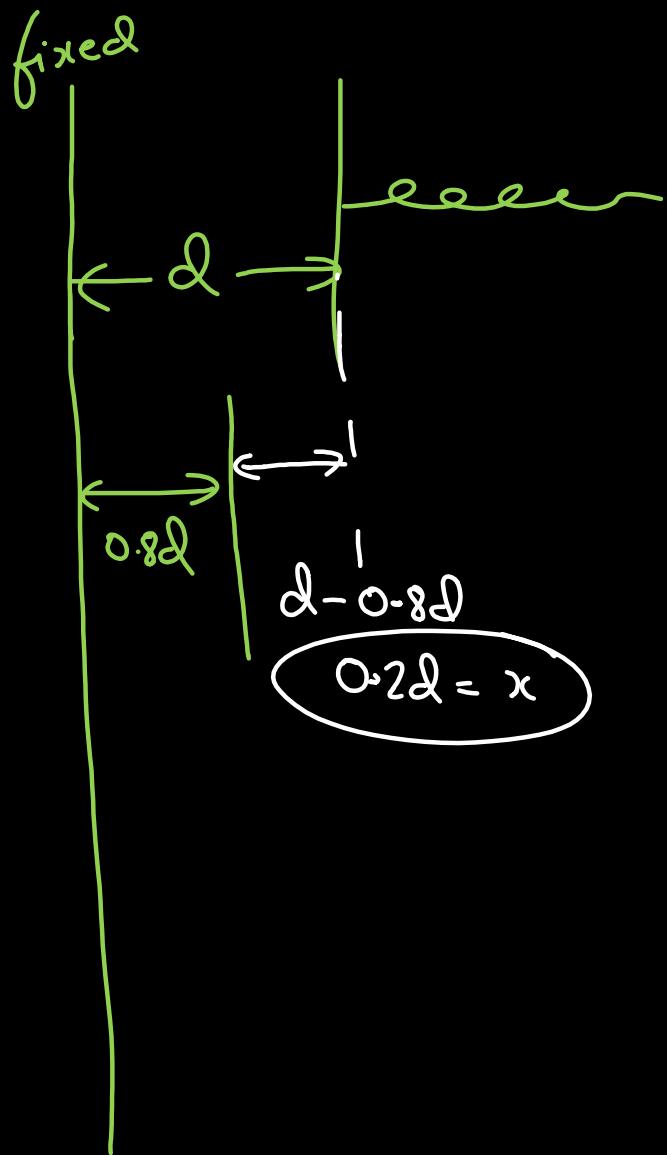
$$k(0.2d) = \frac{\sigma^2 A}{2 \epsilon_0}$$



A parallel plate capacitor with plates of area  $1 \text{ m}^2$  each, are at a separation of  $0.1 \text{ m}$ . If the electric field between the plates is  $100 \text{ N/C}$ , the magnitude of charge on each plate is :

$$(\text{Take } \epsilon_0 = \underline{8.85 \times 10^{-12} \frac{\text{C}^2}{\text{N} \cdot \text{m}^2}}) \quad [\underline{12 \text{ Jan. 2019 III}}]$$

- (a)  $7.85 \times 10^{-10} \text{ C}$
- (b)  $6.85 \times 10^{-10} \text{ C}$
- ~~(c)  $8.85 \times 10^{-10} \text{ C}$~~
- (d)  $9.85 \times 10^{-10} \text{ C}$

$$A = 1 \text{ m}^2$$

$$d = 0.1 \text{ m}$$

$$E = 100$$

$$Q = ?$$

$$E = \frac{Q}{\epsilon_0}$$

$$\epsilon = \frac{Q}{A \epsilon_0}$$

$$Q = E A \epsilon_0$$

$$= 100 \times 1 \times 8.85 \times 10^{-12}$$

A parallel plate capacitor is made of two circular plates separated by a distance 5 mm and with a dielectric of dielectric constant 2.2 between them. When the electric field in the dielectric is  $3 \times 10^4$  V/m the charge density of the positive plate will be close to: [2014]


- (a)  $6 \times 10^{-7}$  C/m<sup>2</sup>
- (b)  $3 \times 10^{-7}$  C/m<sup>2</sup>
- (c)  $3 \times 10^4$  C/m<sup>2</sup>
- (d)  $6 \times 10^4$  C/m<sup>2</sup>



$$A = \pi r^2$$

$$d = 5\text{mm}$$

$$\underline{k = 2.2}$$

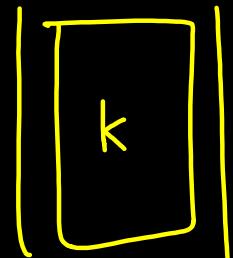

$$E = 3 \times 10^4$$

$$\sigma = ?$$





$$E = \frac{\sigma}{\epsilon_0}$$

vacuum

$$E_{\text{med}} = \frac{\sigma}{\epsilon_0 \epsilon_r} = \frac{\sigma}{\epsilon_0 k}$$


$$\sigma = (E_{\text{med}}) \epsilon_0 k = \underline{3 \times 10^4 \times 8.85 \times 10^{-12} \times 2.2}$$

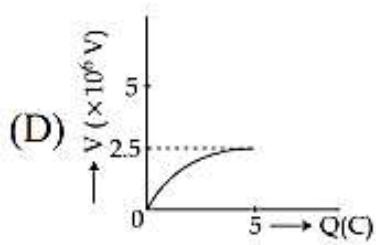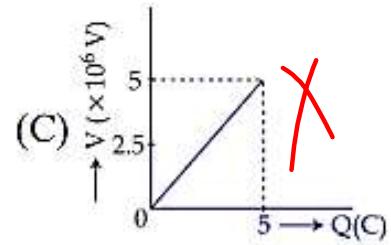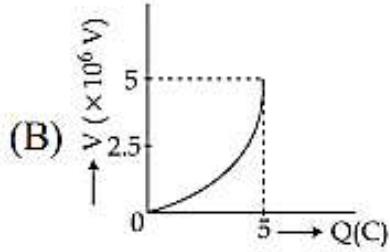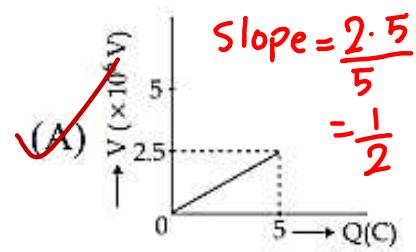A condenser of  $2 \mu\text{F}$  capacitance is charged steadily from 0 to 5C. Which of the following graph represents correctly the variation of potential difference (V) across it's plates with respect to the charge (Q) on the condenser?



$$C = 2 \mu\text{F}$$

$$Q = 0 \text{ to } 5\text{C}$$

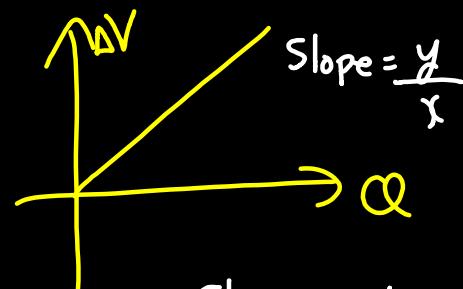

$$\text{Slope} = \frac{1}{C} = \frac{1}{2}$$

$$Q = C \Delta V$$

$$Q \propto \Delta V$$


$$\frac{1}{C} = \frac{\Delta V}{Q}$$

JEE MAINS 2022
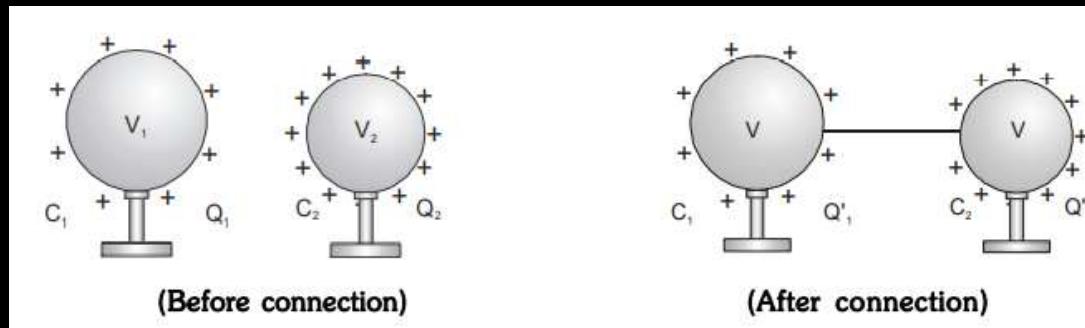
## Redistribution of charges and loss of energy

When two charged conductors are connected by a conducting wire then charge flows from a conductor at higher potential to that at lower potential. This flow of charge stops when the potential of two conductors became equal.

Let the amounts of charges after the conductors are connected are  $Q_1'$  and  $Q_2'$  respectively and potential is  $V$  then



Common potential - According to law of Conservation of charge

$$Q_{\text{before connection}} = Q_{\text{after connection}} \Rightarrow C_1 V_1 + C_2 V_2 = C_1 V + C_2 V$$

Common potential after connection

$$V = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

### Charges after connection

$$Q_1' = C_1 V = C_1 \left( \frac{Q_1 + Q_2}{C_1 + C_2} \right) = \left( \frac{C_1}{C_1 + C_2} \right) Q \quad (Q : \text{Total charge on system})$$

$$Q_2' = C_2 V = C_2 \left( \frac{Q_1 + Q_2}{C_1 + C_2} \right) - \left( \frac{C_1}{C_1 + C_2} \right) Q$$


Ratio of the charges after redistribution  $\frac{Q_1'}{Q_2'} = \frac{C_1 V}{C_2 V} = \frac{R_1}{R_2}$  (in case of spherical conductors)

**Loss of energy in redistribution** – When charge flows through the conducting wire then **energy is lost mainly on account of Joule effect**, electrical energy is converted into heat energy, so change in energy of this system,

$$\Delta U = U_f - U_i \Rightarrow \left( \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 \right) - \left( \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) \Rightarrow \Delta U = -\frac{1}{2} \left( \frac{C_1 C_2}{C_1 + C_2} \right) (V_1 - V_2)^2$$

Here negative sign indicates that energy of the system decrease in the process

## Capacitor as a Circuit Element

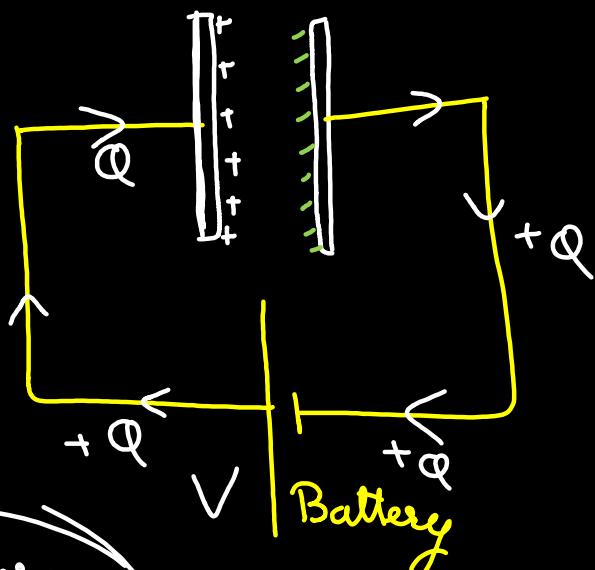

charge on  
Capacitor

$$Q = C \Delta V$$

$$\begin{aligned} \text{WD by battery} &= (Q) (\Delta V) \\ &= (CV) (V) \\ &= CV^2 \end{aligned}$$

50% energy is  
lost in heat

energy stored in  $C = \frac{1}{2} CV^2$



Battery

$$\begin{array}{c} + \\ | \\ \text{low} \\ | \\ - \\ \text{high} \end{array}$$


$\text{Emf} = \mathcal{E}$   
or  
 $\text{Potential diff} = V$

$$W_{\text{external}} = \Delta U + \text{heat loss}$$
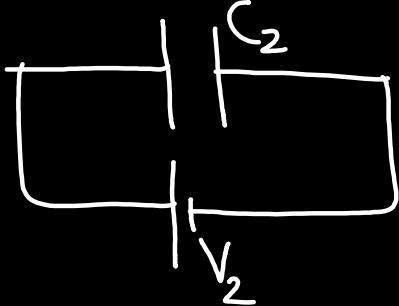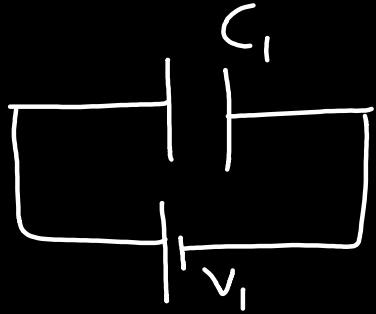
## Redistribution of Charges between Capacitors



Batteries removed

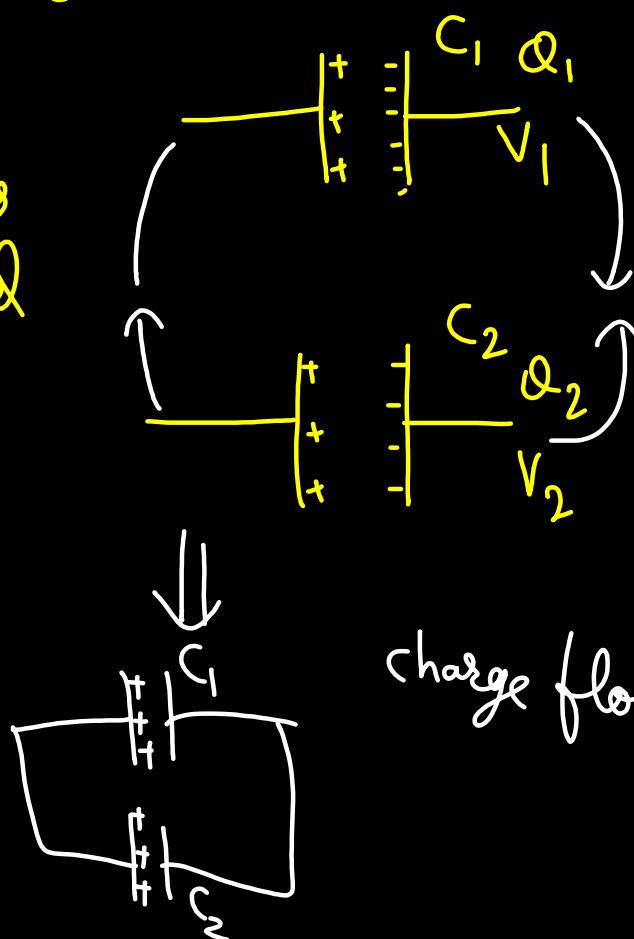

# charge conservation

#  $V_{\text{final}}$  same

charge flow high  $V$  to low  $V$

Jab Tak  $V_{\text{final}}$  same of both.

$$C = \frac{Q}{\Delta V}$$

$$Q = C \Delta V$$

$$\frac{Q}{C} = \Delta V$$

$$Q = C \Delta V$$

$$Q = CV$$


$$C_1 \quad V_1$$

$$Q_1 = C_1 V_1$$

$$C_2 \quad V_2$$

$$Q_2 = C_2 V_2$$

$\Rightarrow$

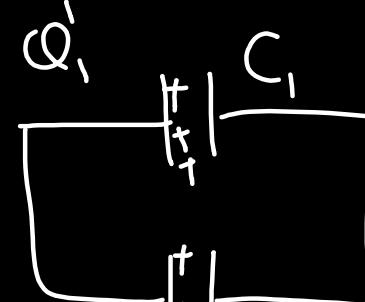

$$V_f$$

$$Q'_1 = C_1 V_f$$

$$Q'_2 = C_2 V_f$$

$$Q'_1 + Q'_2 = Q_1 + Q_2$$

$$U_{\text{initial}} = \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2$$

$$C_1 V_f + C_2 V_f = C_1 V_1 + C_2 V_2$$

$$U_{\text{final}} = \frac{1}{2} C_1 V_f^2 + \frac{1}{2} C_2 V_f^2$$


$$\text{heat loss} = |\Delta U| = U_{\text{ini}} - U_{\text{final}} =$$

$$\frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

A capacitor  $C$  is fully charged with voltage  $V_0$ . After disconnecting the voltage source, it is connected in parallel with another uncharged capacitor of capacitance  $\frac{C}{2}$ . The energy loss in the process after the charge is distributed between the two capacitors is : [Sep. 04, 2020 (II)]

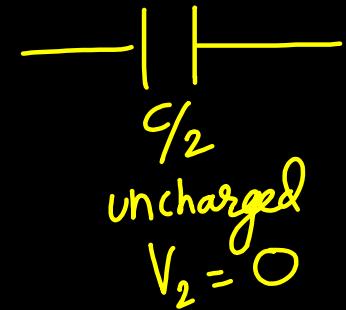- (a)  $\frac{1}{2}CV_0^2$
- (b)  $\frac{1}{3}CV_0^2$
- (c)  $\frac{1}{4}CV_0^2$
- (d)  $\frac{1}{6}CV_0^2$



$$\frac{1}{2} \times \frac{C \times \frac{C}{2}}{C + \frac{C}{2}} \times V_0^2 = \frac{1}{2} \times \frac{C \times \frac{C}{2}}{C + \frac{C}{2}} (V_0 - 0)^2$$

$$\frac{1}{6} CV_0^2$$

## Derivation

charge Conservation

$$Q'_1 + Q'_2 = Q_1 + Q_2$$

$$C_1 V_f + C_2 V_f = C_1 V_1 + C_2 V_2$$

$$V_f = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2}$$

$$Q'_1 = C_1 V_f \quad Q'_2 = C_2 V_f$$

$$U_{\text{ini}} - U_{\text{final}} = \text{heat}$$


$$\left( \frac{1}{2} C_1 V_1^2 + \frac{1}{2} C_2 V_2^2 \right) - \left( \frac{1}{2} C_1 V_f^2 + \frac{1}{2} C_2 V_f^2 \right)$$

$$\frac{1}{2} (C_1 + C_2) V_f^2$$


$$\frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 .$$

In the figure shown, after the switch 'S' is turned from position 'A' to position 'B', the energy dissipated in the circuit in terms of capacitance 'C' and total charge 'Q' is:

[12 Jan. 2019 I]

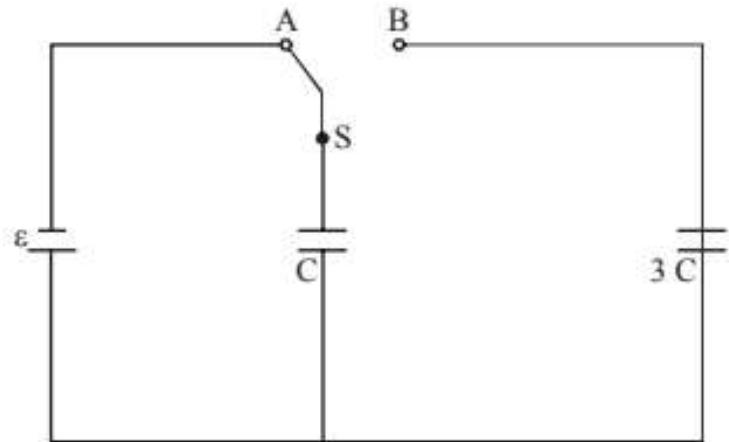

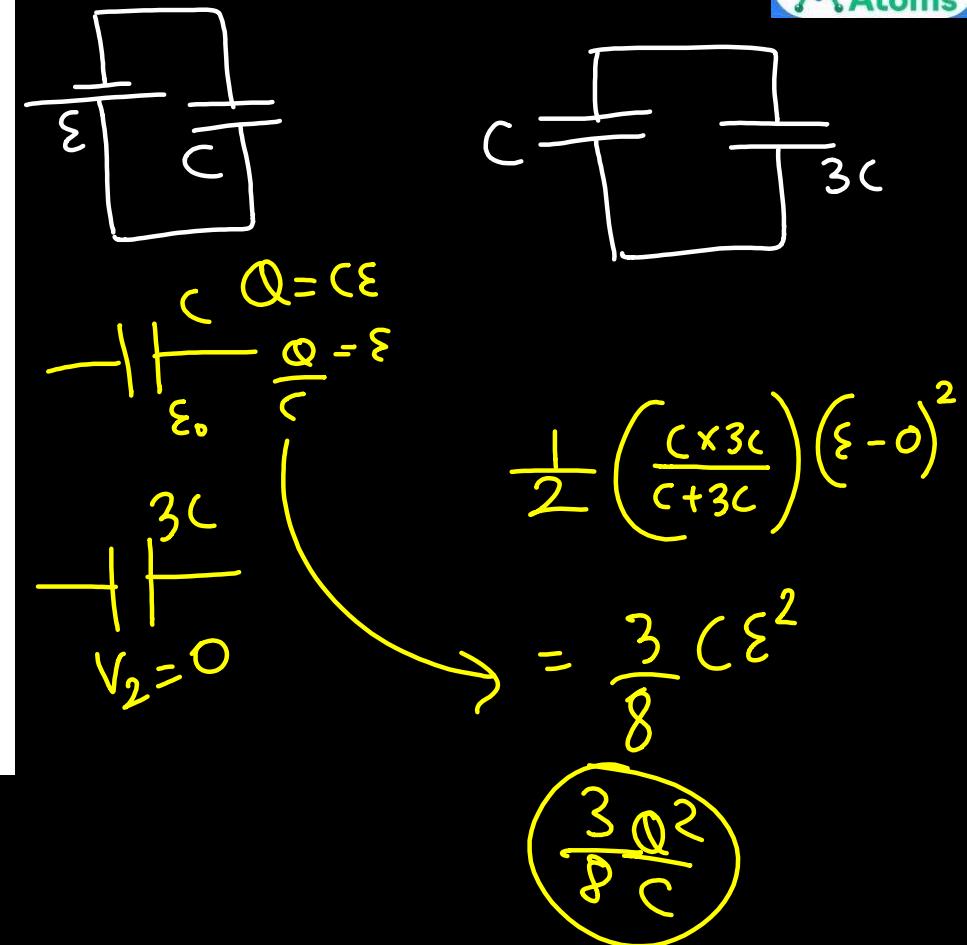- (a)  $\frac{1}{8} \frac{Q^2}{C}$    ~~(b)~~  $\frac{3}{8} \frac{Q^2}{C}$    (c)  $\frac{5}{8} \frac{Q^2}{C}$    (d)  $\frac{3}{4} \frac{Q^2}{C}$



$$\begin{aligned} & \text{Initial State: } \frac{\epsilon}{C} \\ & \text{Final State: } \frac{\epsilon}{3C} \\ & \text{Intermediate State: } \frac{\epsilon}{C} + \frac{\epsilon}{3C} = \frac{4\epsilon}{3C} \quad Q = CE \\ & \text{Energy Dissipated: } \frac{1}{2} \left( \frac{C}{C+3C} \right) (\epsilon - 0)^2 \\ & = \frac{3}{8} CE^2 \\ & = \frac{3}{8} \frac{Q^2}{C} \end{aligned}$$



A  $5 \mu\text{F}$  capacitor is charged fully by a  $220 \text{ V}$  supply. It is then disconnected from the supply and is connected in series to another uncharged  $2.5 \mu\text{F}$  capacitor. If the energy

change during the charge redistribution is  $\frac{X}{100} \text{ J}$  then value

of  $X$  to the nearest integer is \_\_\_\_\_.


[NA Sep. 02, 2020 (I)]

$$X \approx 4$$

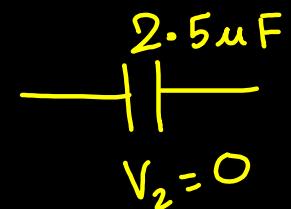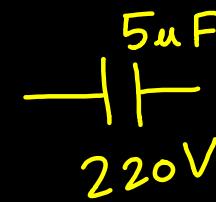


$$\begin{aligned}\Delta U &= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2 \\ &= \frac{1}{2} \left( \frac{5 \times 2.5 \mu\text{F}}{5 + 2.5 \mu\text{F}} \right) (220 - 0)^2\end{aligned}$$

A source of potential difference  $V$  is connected to the combination of two identical capacitors as shown in the figure. When key 'K' is closed, the total energy stored across the combination is  $E_1$ . Now key 'K' is opened and dielectric of dielectric constant 5 is introduced between the plates of the capacitors. The total energy stored across the combination is now  $E_2$ . The ratio  $E_1/E_2$  will be :

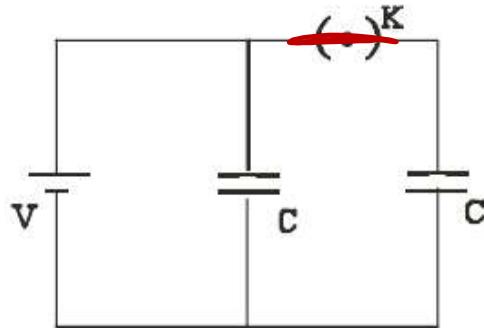


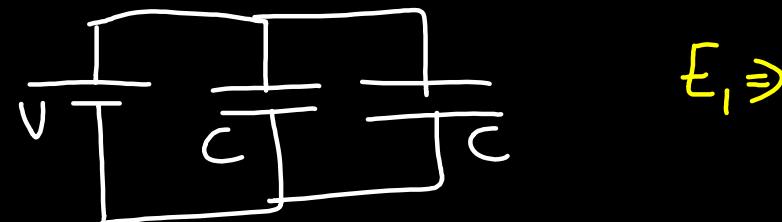- (A)  $\frac{1}{10}$
- (B)  $\frac{2}{5}$
- (C)  $\frac{5}{13}$
- (D)  $\frac{5}{26}$




$$E_1 \Rightarrow$$


Finally

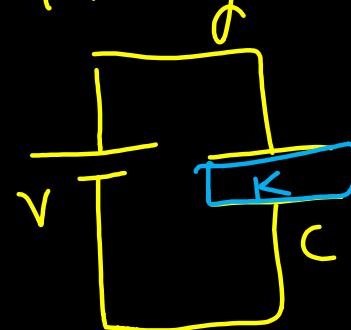

$$E_2 =$$

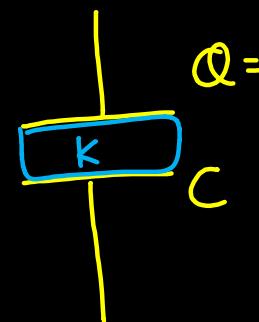

$$\frac{E_1}{E_2} = ?$$

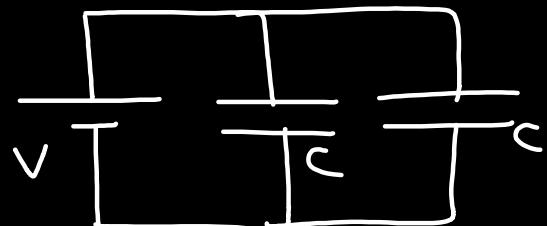

$$E_1 = \frac{1}{2}CV^2 + \frac{1}{2}CV^2$$


$$E_1 = \underline{\underline{CV^2}}$$

$$\underline{\underline{\text{charge on } C = CV}} \quad \underline{\underline{CV}}$$

final

$$C' = \frac{A\epsilon_0 K}{d}$$


$$= KC$$

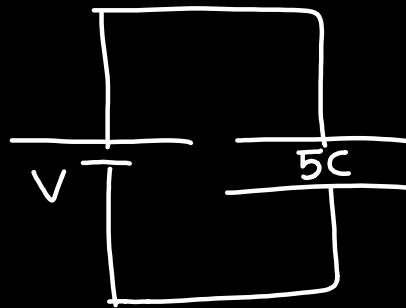

$$E_2 = \frac{1}{2}(5C)V^2 + \frac{CV^2}{10}$$

$$= \frac{26}{10}CV^2$$

$$E_2 = \frac{13}{5}CV^2$$

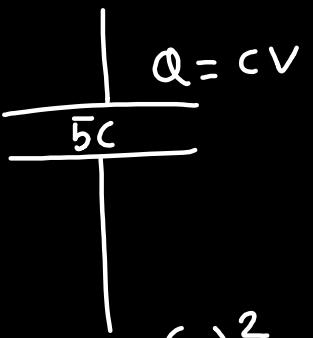


$$Q = CV$$

$$U = \frac{(Q)^2}{2C'}$$

$$= \frac{(CV)^2}{25C}$$


$$= \frac{CV^2}{10}$$

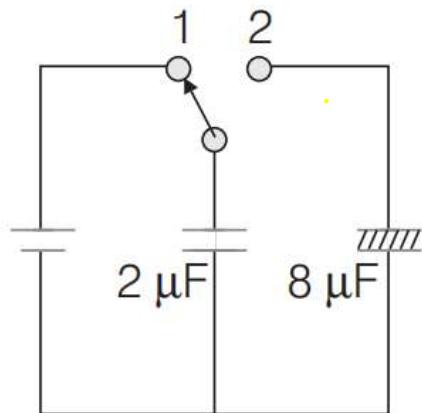A  $2\mu F$  capacitor is charged as shown in the figure. The percentage of its stored energy dissipated after the switch  $S$  is turned to position 2 is \_\_\_\_\_ (2011)



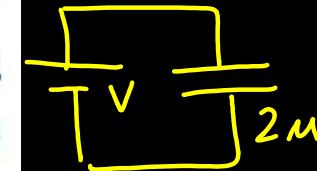- (a) 0%
- (b) 20%
- (c) 75%
- ~~(d) 80%~~



$$\text{lost} = \frac{\text{loss}}{\text{initial}} \times 100$$




$$\begin{aligned} U_i &= \frac{1}{2} C V^2 \\ &= \frac{1}{2} 2\mu F V^2 \\ &= V^2 \end{aligned}$$

$$\Delta U = \frac{1}{2} \frac{8 \times 8}{8 + 2} (V - 0)^2$$

$$\text{loss} = 0.8 V^2$$

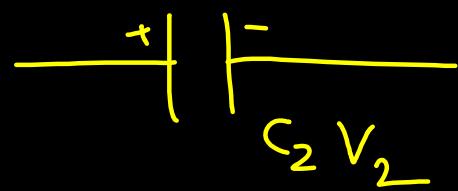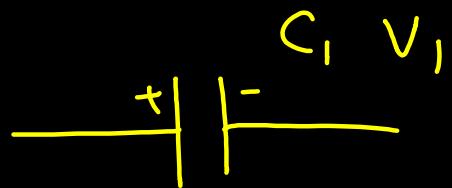

Reverse Polarity Connection

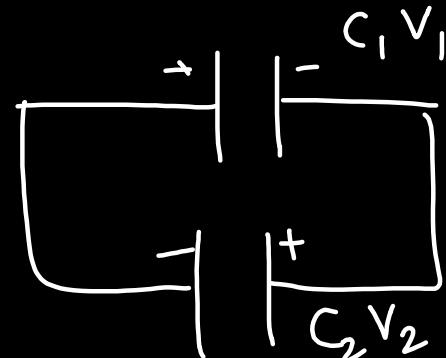


$$V_f = \frac{C_1 V_1 + C_2 (-V_2)}{C_1 + C_2}$$

$$\text{loss} = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - (-V_2))^2$$

$$= \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 + V_2)^2.$$
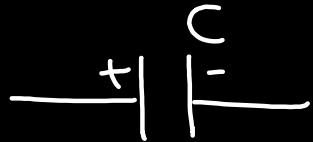
## Charged Capacitor Connected with Battery




$$Q_{\text{initial}} = CV$$

$$U_{\text{initial}} = \frac{Q^2}{2C}$$

$$= \frac{(CV)^2}{2C}$$

$$= \frac{1}{2}CV^2$$

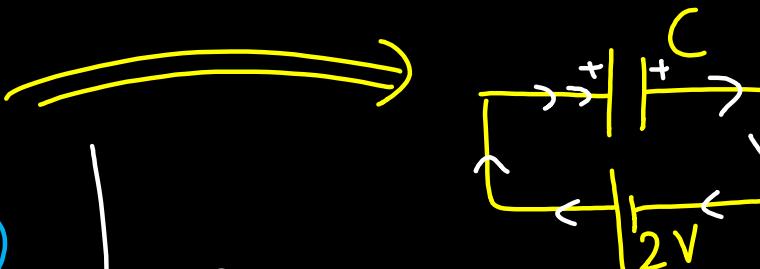

$$Q_{\text{final}} = C(\Delta V_{\text{final}})$$


$$= C 2V$$

$$\underline{\underline{Q_{\text{final}} = 2CV}}$$


$$WD \text{ by Battery} = (Q_{\text{flow}})(\Delta V) = (CV)(2V) = 2CV^2.$$

$$U_{\text{final}} = \frac{1}{2}CV_f^2 = \frac{1}{2}C(2V)^2 = \underline{\underline{2CV^2}}$$

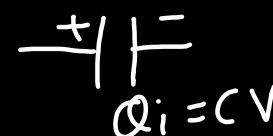find heat lost  
after connecting  
battery?



$$Q_i = CV$$

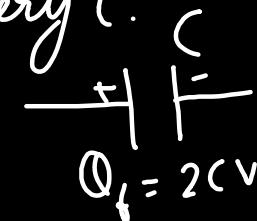

$$Q_f = 2CV$$

$$Q_{\text{flow}}$$

$$\text{from battery} = 2CV - CV$$



$$= \underline{\underline{CV}}$$

$$\Delta WD_{Batt} = \Delta U + \text{heat loss}$$

$$2CV^2 = (U_f - U_i)$$

$$2CV^2 = 2CV^2 - \frac{1}{2}CV^2 + \text{heat}$$



$$\frac{1}{2}CV^2 = \text{heat}$$

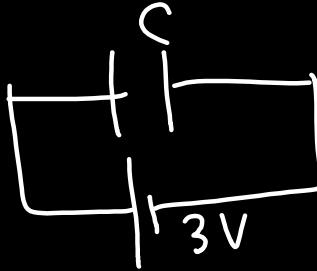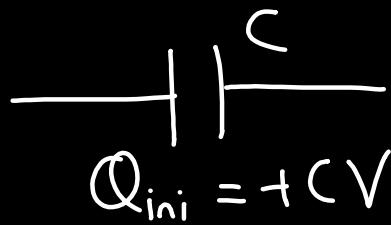

Find  
~~Q<sub>final</sub>~~ charge on  
 capacitor

$$\begin{aligned}
 Q_{final} &= C(\Delta V_{final}) \quad ② \\
 &= C 3V \\
 &= \boxed{3CV}
 \end{aligned}$$

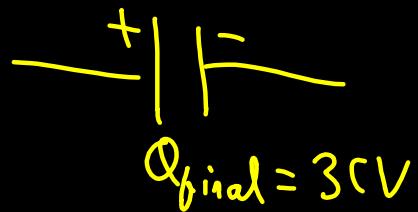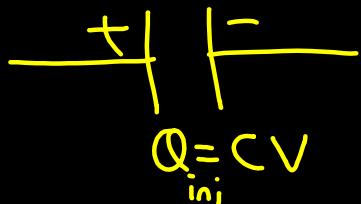
$\downarrow$   
 $3CV - CV$   
 $= \boxed{2CV}$



Two capacitors of capacitances  $C$  and  $2C$  are charged to potential differences  $V$  and  $2V$ , respectively. These are then connected in parallel in such a manner that the positive terminal of one is connected to the negative terminal of the other. The final energy of this configuration is :

[Sep. 05, 2020 (I)]

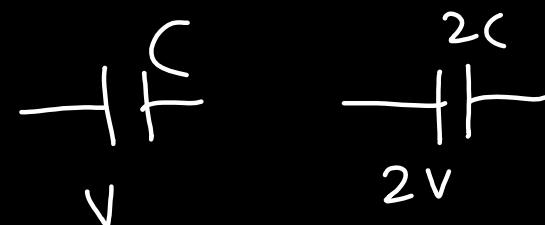- (a)  $\frac{25}{6}CV^2$
- (b)  $\frac{3}{2}CV^2$
- (c) zero
- (d)  $\frac{9}{2}CV^2$



$$|V_{\text{final}}| = \frac{CV + 2C(-2V)}{C + 2C}$$



$$\begin{aligned} U_{\text{final}} &= \frac{1}{2}C(V)^2 + \frac{1}{2}(2C)(V)^2 \\ &= \frac{3CV^2}{2} \end{aligned}$$


G.O.A.T.

11<sup>th</sup>

12<sup>th</sup> Bounce back

A parallel plate capacitor of capacitance  $C$  is connected to a battery and is charged to a potential difference  $V$ . Another capacitor of capacitance  $2C$  is similarly charged to a potential difference  $2V$ . The charging battery is now disconnected and the capacitors are connected in parallel to each other in such a way that the positive terminal of one is connected to the negative terminal of the other. The final energy of the configuration is (1995)




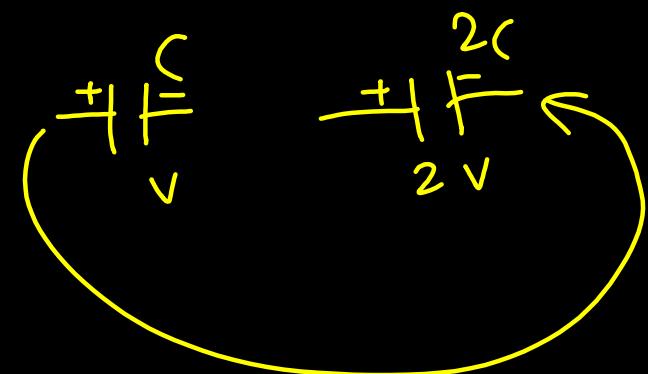
- (a) zero
- (b)  $\frac{3}{2}CV^2$
- (c)  $\frac{25}{6}CV^2$
- (d)  $\frac{9}{2}CV^2$


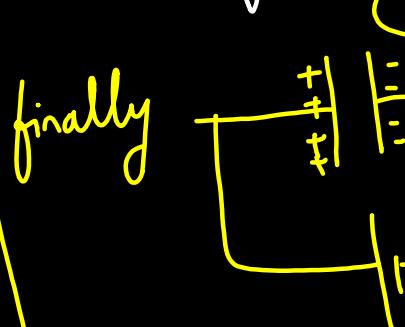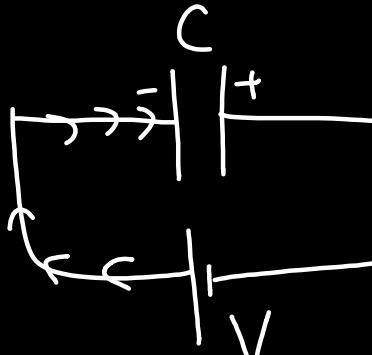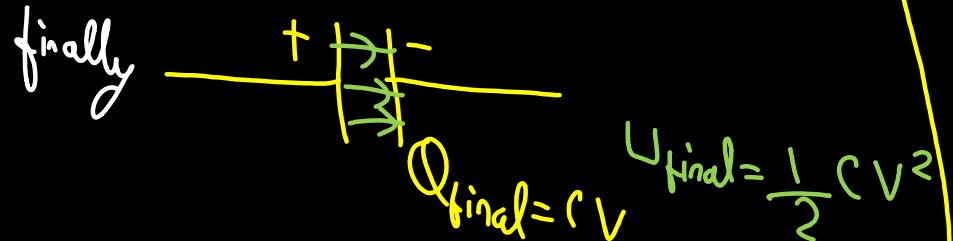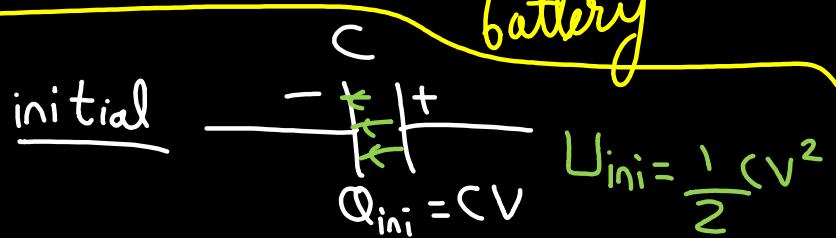
## Charged C connected with Reverse Polarity



$Q_{init} = CV$  -ve of C connected with +ve of battery



After Connection  
find heat loss ??.

$$Q_{final} = CV$$


$$Q_{flown \text{ from battery}} = +2CV$$

$$WD_{\text{Bat}} = \Delta U + \text{heat}$$


$$(2cv)(v) = U_f - U_i + \text{heat}$$

$$2cv^2 = 0$$

$$2cv^2 = \text{heat}$$

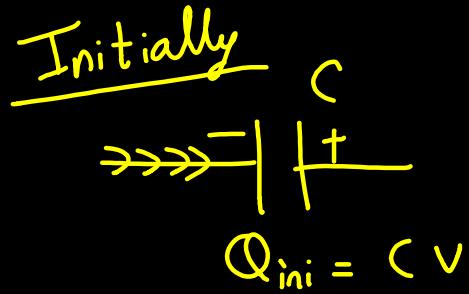

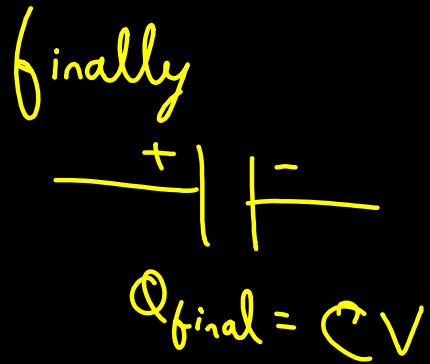
$$\begin{aligned} W_D^{\text{Bat}} &= (Q_{\text{flow}})(P.d.) \\ &= (2CV)(V) = \underline{\underline{2CV^2}} \end{aligned}$$



$$\begin{aligned} Q_{\text{flow}} &= (\text{final} - \text{initial}) \text{ with polarity} \\ &= 2CV \end{aligned}$$


## KIRCHHOFF'S LAWS

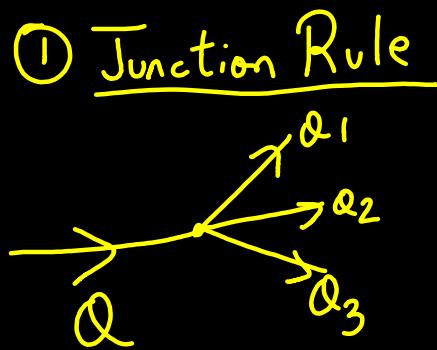- (i) Junction Rule - Sum of charges present on the plates of capacitors connected at a junction is equal to zero (If initially all the capacitors are uncharged) (while adding charges of different plates battery can be neglected as net charge on battery is zero).
- (ii) **Loop Rule** - In any closed loop the algebraic sum of potential drops across different elements is equal to zero.




$$Q = Q_1 + Q_2 + Q_3$$

(charge conservation)

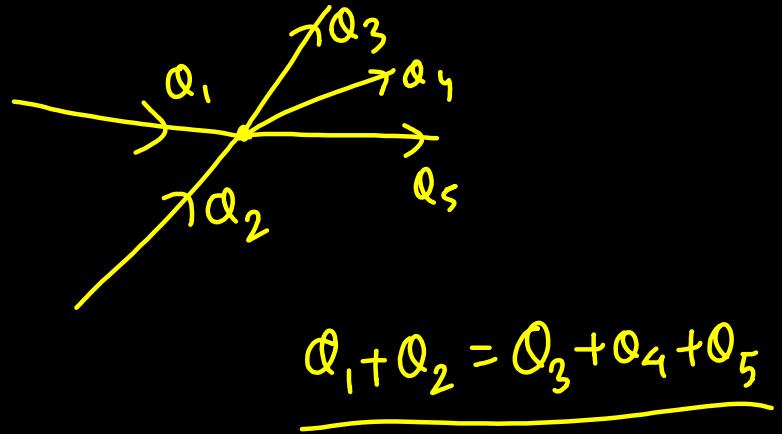


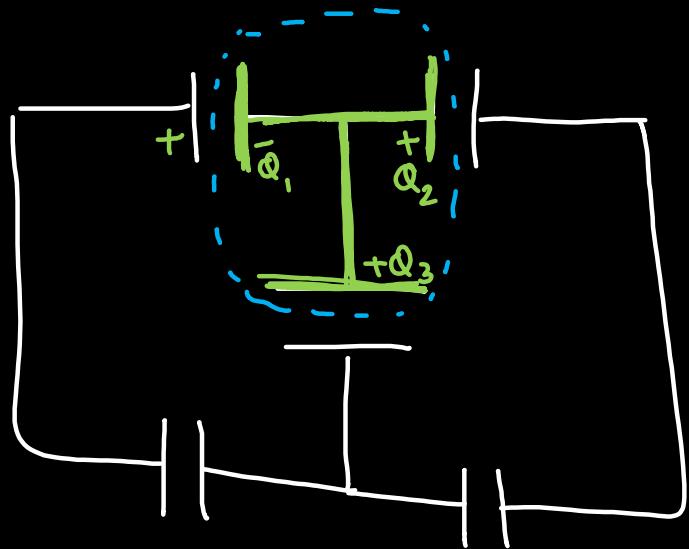Concept = island (isolated) ( initial total charge = final total charge)



# initially all  
# No charge


# finally

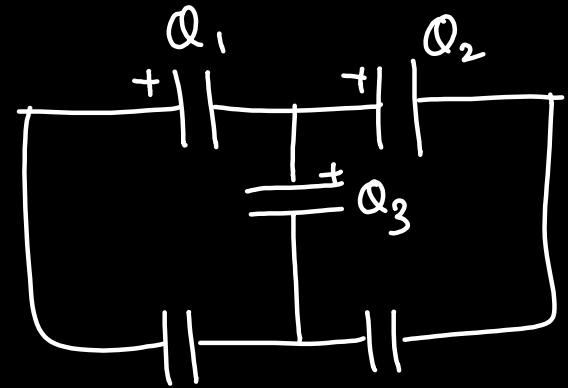

$$Q = -Q_1 + Q_2 + Q_3$$

Loop Law  
(energy conservation)


# Pointe namings

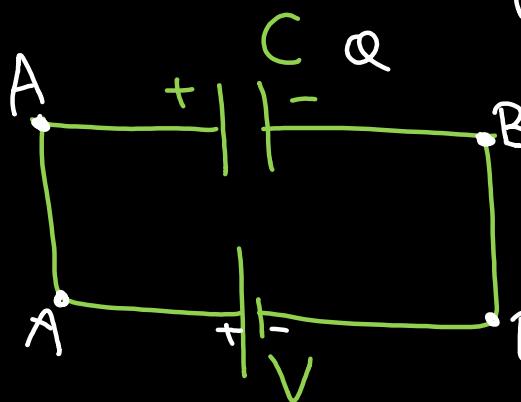


$$\Delta V = CV$$

$$V = \frac{Q}{C}$$
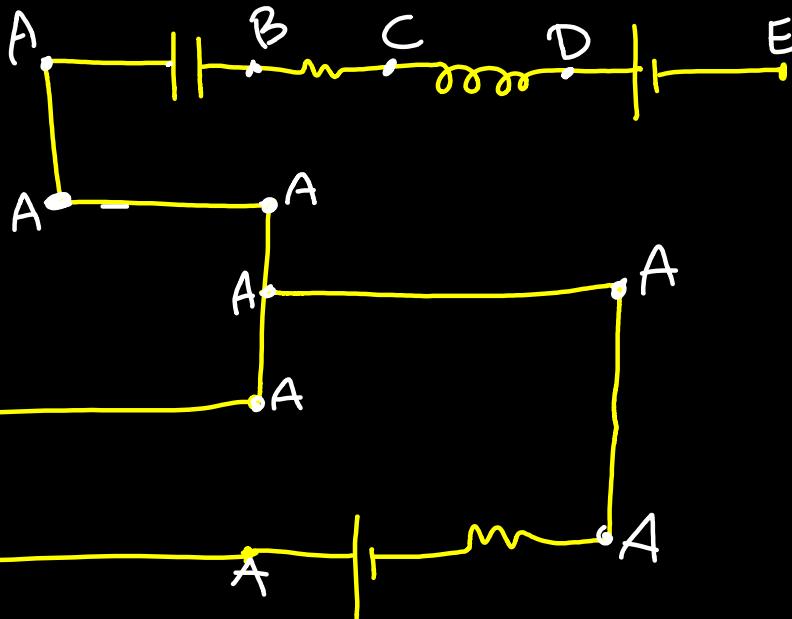
$$\Delta V_{AB} = V \quad \Delta V_{AB} = \frac{Q}{C} \Rightarrow \frac{Q}{C} = V \rightarrow eQ \text{ of loop law.}$$



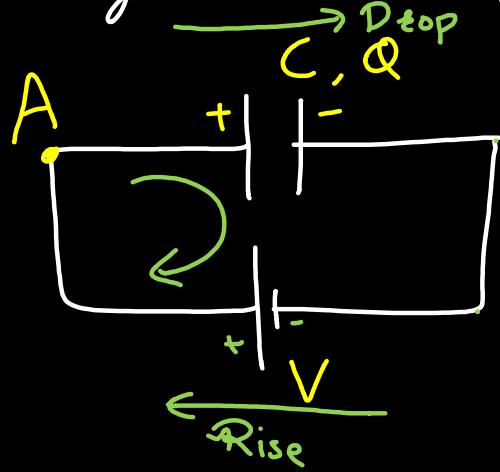→ algebraic sum of all  $\Delta V$  in loop is 0.



Rise +

$\Delta V_{\text{top}}$  -

start

$$V_A - \frac{Q}{C} + V = V_A^{\text{end}}$$

$$0 - \frac{Q}{C} + V = 0$$

$$V = \frac{Q}{C}$$

## COMBINATION OF CAPACITORS


**Series Combination** (i) When initially uncharged capacitors are connected as shown in the  
(ii) All capacitors will have same charge but different potential difference across them.

(iii) We can say that

$$V_1 = \frac{Q}{C_1} \quad V_1 = \text{potential across } C_1$$

$Q$  = charge on positive plate of  $C_1$   $C_1$  = capacitance of capacitor similarly
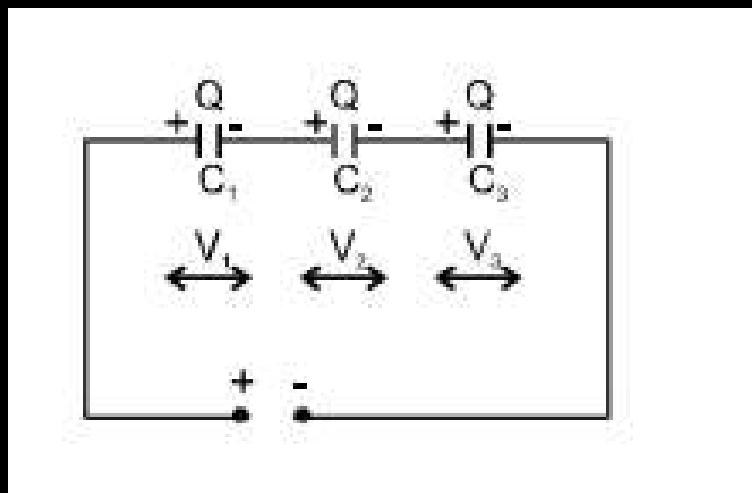
$$V_2 = \frac{Q}{C_2}, \quad V_3 = \frac{Q}{C_3} \dots \dots$$



$$(iv) V_1 : V_2 : V_3 = \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$

We can say that potential difference across capacitor is inversely proportional to its capacitance in series combination.  $V \propto \frac{1}{C}$

Note : In series combination the smallest capacitor gets maximum potential.

$$(v) \quad V_1 = \frac{\frac{1}{C_1}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V \quad V_2 = \frac{\frac{1}{C_2}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V \quad V_3 = \frac{\frac{1}{C_3}}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots} V$$

Where  $V = V_1 + V_2 + V_3$

(vi) Energy stored in the combination


$$U_{\text{combination}} = \frac{Q^2}{2C_1} + \frac{Q^2}{2C_2} + \frac{Q^2}{2C_3} \quad U_{\text{combination}} = \frac{Q^2}{2C_{eq}}$$

Energy supplied by the battery in charging the combination

$$U_{\text{battery}} = Q \times V = Q \cdot \frac{Q}{C_{eq}} = \frac{Q^2}{C_{eq}} \quad \frac{U_{\text{combination}}}{U_{\text{battery}}} = \frac{1}{2}$$


Note : Half of the energy supplied by the battery is stored in form of electrostatic energy and half of the energy is converted into heat through resistance.
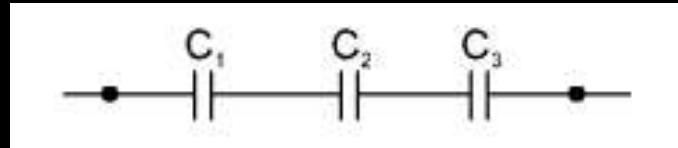
### **Formulae Derivation for series combination**



meaning of equivalent capacitor

$$C_{eq} = \frac{Q}{V}$$

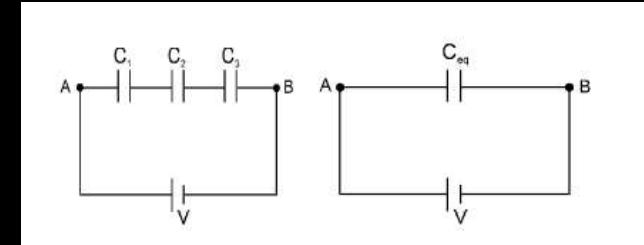

Now, Initially, the capacitor has no charge. Applying Kirchhoff's voltage law


$$\frac{-Q}{C_1} + \frac{-Q}{C_2} + \frac{-Q}{C_3} + V = 0.$$

$$V = Q \left[ \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \right]$$

$$\frac{V}{Q} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

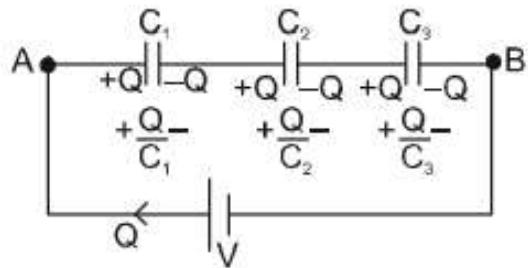in general  $\frac{1}{C_{eq}} = \sum_{n=1}^n \frac{1}{C_n}$



## **Parallel Combination**

1. When one plate of each capacitors (more than one) is connected together and the other plate of each capacitor is connected together, such combination is called parallel combination.
2. All capacitors have same potential difference but different charges.
3. We can say that :


$$Q_1 = C_1 V$$

$Q_1$  = Charge on capacitor  $C_1$

$C_1$  = Capacitance of capacitor  $C_1$

$V$  = Potential of across capacitor  $C_1$

4.  $Q_1 : Q_2 : Q_3 = C_1 : C_2 : C_3$

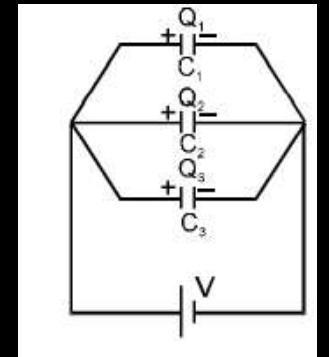

The charge on the capacitor is proportional to its capacitance  $Q \propto C$

$$5. Q_1 = \frac{C_1}{C_1+C_2+C_3} Q; Q_2 = \frac{C_2}{C_1+C_2+C_3} Q; Q_3 = \frac{C_3}{C_1+C_2+C_3} Q$$

Where  $Q = Q_1 + Q_2 + Q_3 \dots \dots$

Note : Maximum charge will flow through the capacitor of largest value.

6. Energy stored in the combination:

$$\text{V}_{\text{combination}} = \frac{1}{2} C_1 V^2 + \frac{1}{2} C_2 V^2 + \dots = \frac{1}{2} (C_1 + C_2 + C_3 \dots) V^2 = \frac{1}{2} C_{\text{eq}} V^2$$

$$U_{\text{battery}} = QV = CV^2 = \frac{U_{\text{combination}}}{U_{\text{battery}}} = \frac{1}{2}$$

Note : Half of the energy supplied by the battery is stored in form of electrostatic energy and half of the energy is converted into heat through resistance.

### Formulae Derivation for parallel combination :


$$Q = Q_1 + Q_2 + Q_3 = C_1 V + C_2 V + C_3 V$$

$$= V(C_1 + C_2 + C_3)$$

$$\frac{Q}{V} = C_1 + C_2 + C_3$$

$$C_{\text{eq}} = C_1 + C_2 + C_3$$
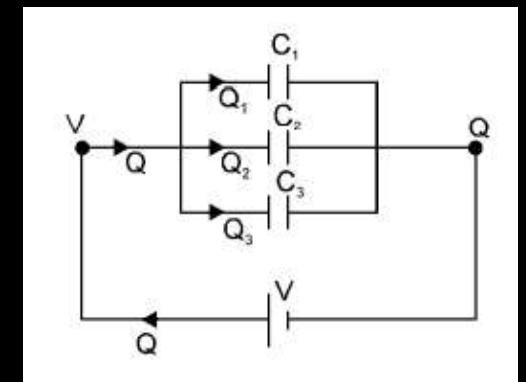
$$\text{In general } C_{\text{eq}} = \sum_{n=1}^n C_n$$



## Mixed Combination

The combination which contains mixing of series parallel combinations or other complex combinations fall in mixed category.

There are two types of mixed combinations

- (i) Simple   (ii) Complex.

### Simple Mixed Combination

Combinations which can be easily converted in series parallel combination.




### Complex Mixed Combination

The given combination can not be simplified by series or parallel combination such a combination is solved by using Kirchhoff's Law and other techniques. A special case of this combination is Wheatstone bridge.

## Wheatstone bridge

If  $\frac{C_1}{C_4} = \frac{C_3}{C_5}$  or  $C_1 C_5 = C_3 C_4$  then

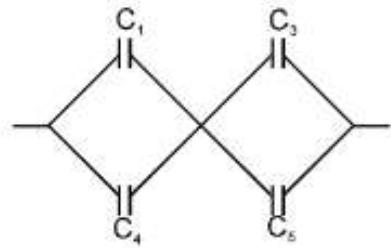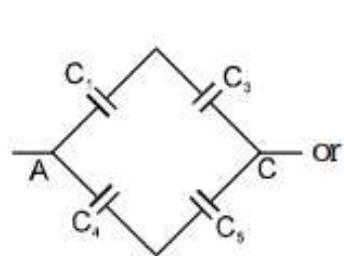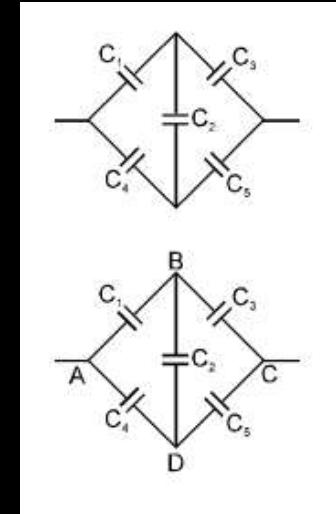- (i) Such combination is called balanced Wheatstone bridge.
- (ii) In this case  $V_B = V_D$ .
- (iii) Charge on  $C_2 = 0$
- (iv) The equivalent can be converted in to given circuits:




$$(v) \quad C_{eq} = \frac{(C_1 + C_4)(C_3 + C_5)}{C_1 + C_2 + C_3 + C_5} = \frac{C_1 C_3}{C_1 + C_3} + \frac{C_4 C_5}{C_4 + C_5}$$

(vi) If  $C_1 = C_4 = C_3 = C_5 = C$  then  $C_{eq} = C$

Other important circuit solving techniques

(Applicable in both capacitive and resistive networks) .

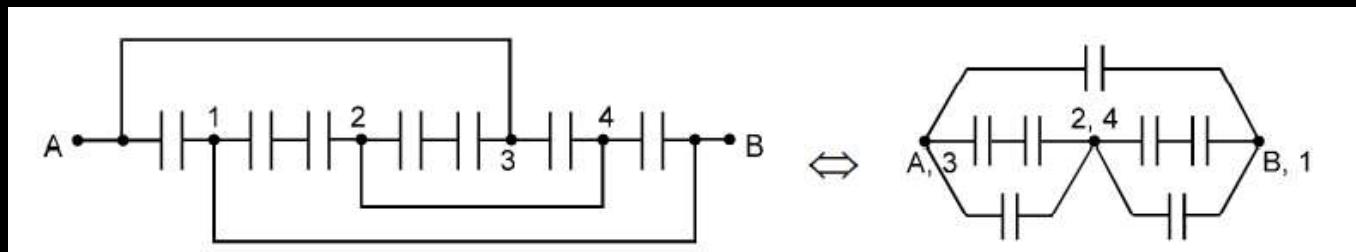**(A) Equipotential technique** – All the junction which are at equal potential ( such as junction connected by a connecting wire) can be replaced by a single junction. So redraw the circuit to get it simplified




**(B) Infinite Circuits** - Assume equivalent capacitance / resistance to be  $C_{eq}$  /  $R_{eq}$  of whole network , then add one or more branch ( repetitive) in infinite network . Calculate equivalent of this new circuit. It should again be equal to  $C_{eq}$  /  $R_{eq}$ .

Note : If all the resistance / capacitance of a circuit are made k times then equivalent will also become K-times
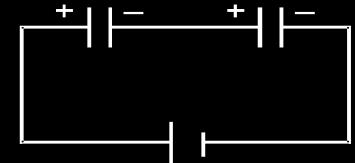
## GOLDEN POINT



- For a given voltage to store maximum energy capacitors should be connected in parallel.  
If N identical capacitors each having breakdown voltage V are joined in
  - (I ) series then the break down voltage of the combination is equal to NV
  - (ii)parallel then the breakdown voltage of the combination is equal to V.
- Two capacitors are connected in series with a battery. Now battery is removed and loose wires connected together then final charge on each capacitor is zero.



- If N identical capacitors are connected then

$$C_{\text{series}} = \frac{1}{N} \quad C_{\text{parallel}} = NC$$

In DC capacitor's offers infinite resistance in steady state, so there will be no current flows through capacitor branch

## CIRCUIT SOLVING

For the given circuit we are interested in finding charges and potential difference across,  $C_1$ ,  $C_2$  and  $C_3$

Now, In loop 1 Using KVI , we get

$$\varepsilon - \frac{q_2}{C_3} = 0 \Rightarrow q_2 = C_3 \varepsilon$$

In loop 2 Using KVL, we get

$$\frac{q_2}{C_3} - \frac{q_1}{C_1} - \frac{q_1}{C_2} = 0 \Rightarrow \frac{q_2}{C_3} = \frac{q_1}{C_1} + \frac{q_1}{C_2}$$

By solving (i) and (ii)

We get the values of  $q_1$  and  $q_2$


And with the help of  $q_1$ ,  $q_2$  we can find corresponding potential difference.

Now, we are also interested in calculating  $V_F - V_B$  In path BCDEF

By applying K.V.L. we get

$$V_F - V_B = (V_C - V_B) + (V_D - V_C) + (V_E - V_D) + (V_F - V_E) \left( -\frac{q_1}{C_1} \right) + \left( -\frac{q_1}{C_2} \right) + (0) + (0)$$

also from path BAF =  $-\varepsilon$

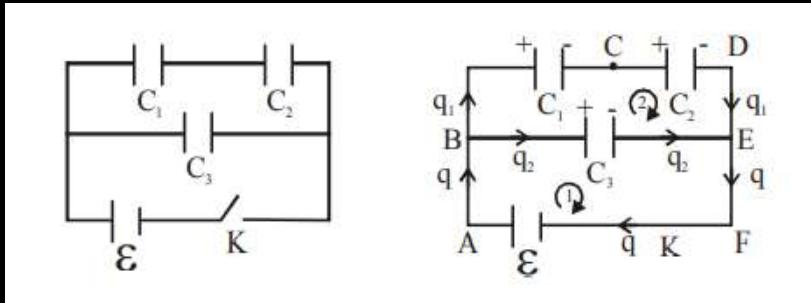

## CHARGE FLOW AND HEAT GENERATION

- (i) Whenever there is potential difference there will be flow of charge.
- (ii) Charge always have tendency to flows from high potential energy to low potential energy when released freely.
- (iii) Positive charge always flows from high potential to low potential ( if only electric force act on charge )
- (iv) Negative charge always flows from low potential to high potential (if only electric force act on charge )
- (v) The flow of charge will continue till there is potential difference between the conductors ( finally potential difference = 0)
- (vi) Formulae related with redistribution of charges.

Before connecting the conductors		
Parameter	Conductor I <sup>st</sup>	Conductor II <sup>nd</sup>
Capacitance	$C_1$	$C_2$
Charge	$Q_1$	$Q_2$
Potential	$V_1$	$V_2$

After connecting the conductors		
Parameter	I <sup>st</sup> Conductor	II <sup>nd</sup> Conductor
Capacitance	$C_1$	$C_2$
Charge	$Q'_1$	$Q'_2$
Potential	$V$	$V$


$$V = \frac{Q'_1}{C_1} = \frac{Q'_2}{C_2} \Rightarrow \frac{Q'_1}{Q'_2} = \frac{C_1}{C_2} \quad \text{But, } Q'_1 + Q'_2 = Q_1 + Q_2$$

$$\therefore V = \frac{Q_1 + Q_2}{C_1 + C_2} = \frac{C_1 V_1 + C_2 V_2}{C_1 + C_2} ; \quad \therefore Q'_1 = \frac{C_1}{C_1 + C_2} (Q_1 + Q_2) \text{ & } Q'_2 = \frac{C_2}{C_1 + C_2} (Q_1 + Q_2)$$

$$\text{Heat loss during redistribution : } \Delta H = \frac{1}{2} \frac{C_1 C_2}{C_1 + C_2} (V_1 - V_2)^2$$

The loss of energy is in the form of Joule heating in the wire.

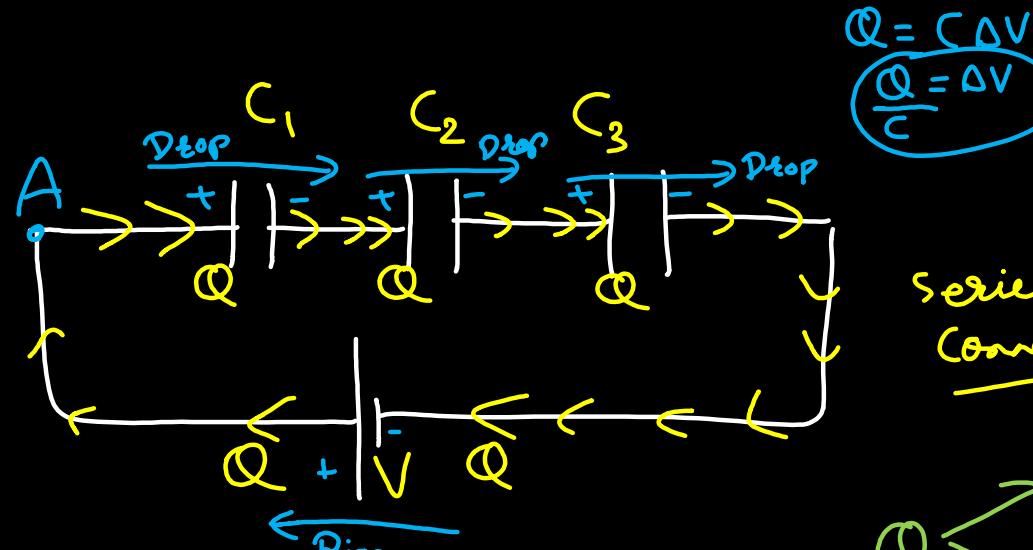**Note :** Always put  $Q_1$ ,  $Q_2$ ,  $V_1$  and  $V_2$  with sign.




$$Q = C \Delta V$$

$$\frac{Q}{C} = \Delta V$$

Series Connection

$$-\frac{Q}{C_1} - \frac{Q}{C_2} - \frac{Q}{C_3} + V = 0$$

$\Rightarrow$

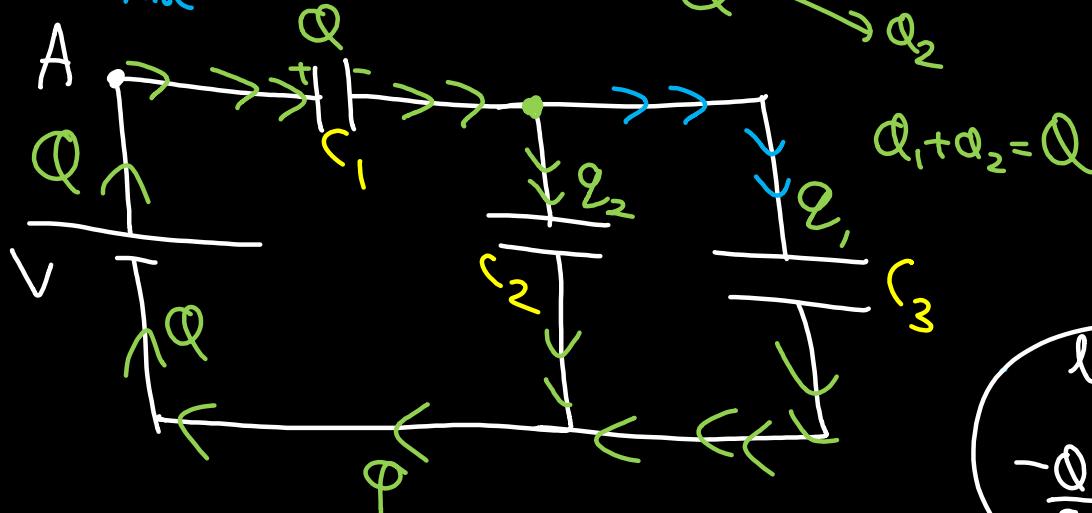

$$Q \rightarrow Q_1$$

$$Q \rightarrow Q_2$$

$$Q \rightarrow Q_3$$

$$Q \rightarrow Q-x$$

loop 2

$$-\frac{Q}{C_1} - \frac{Q_2}{C_2} + V = 0$$


loop 1

$$-\frac{Q}{C_1} - \frac{Q_3}{C_3} + V = 0$$

## Combination of Capacitors
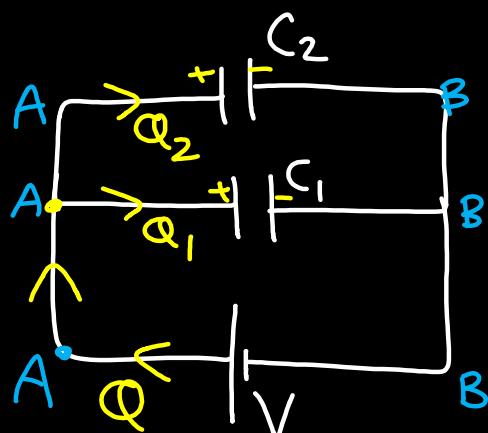
### ① Parallel Connection

→ when connected across same points, ( $\Delta V$  across is same)



$$\frac{Q_2}{C_2} = \frac{Q_1}{C_1} = V$$

1

$$-\frac{Q_1}{C_1} + V = 0$$

$$\frac{Q_1}{C_1} = V$$

$$-\frac{Q_2}{C_2} + V = 0$$



$$\frac{Q_2}{C_2} = V$$

$$Q_1 = C_1 V$$

$$Q_2 = C_2 V$$

$$Q_1 : Q_2 = C_1 : C_2$$

# more C more Q

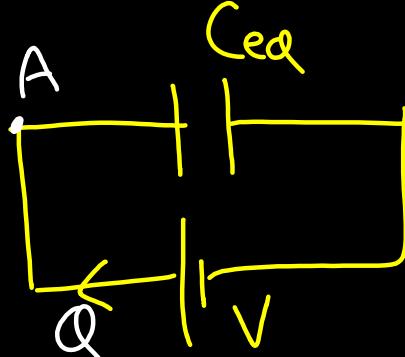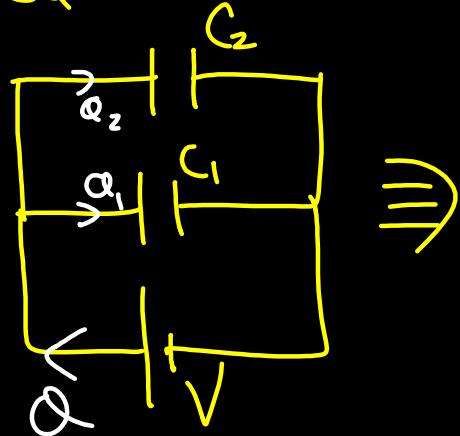$C_{eq}$ 


$$-\frac{Q}{C_{eq}} + V = 0$$

$$Q = C_{eq} V$$

$$Q = Q_1 + Q_2$$

$$C_{eq}V = C_1V + C_2V$$

$$C_{eq} = C_1 + C_2$$

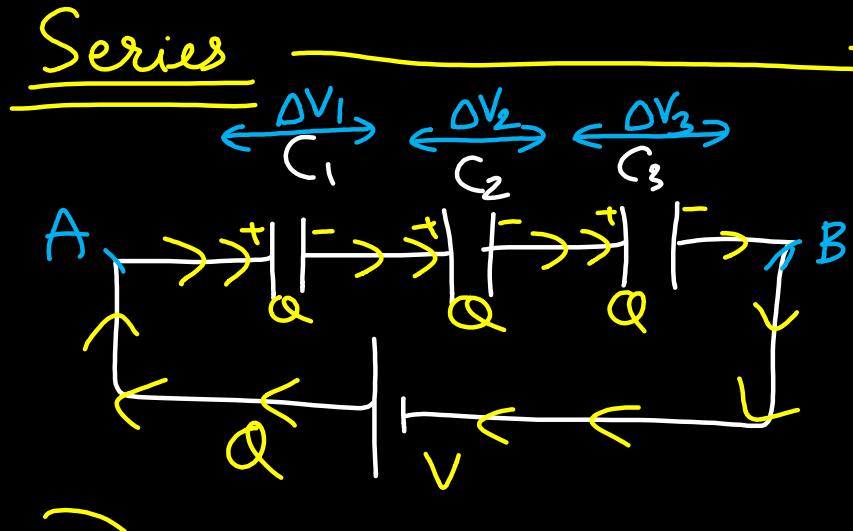

loop

$$-\frac{Q}{C_1} - \frac{Q}{C_2} - \frac{Q}{C_3} + V = 0$$

$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

charge flow same in Capacitors.

$$\boxed{\Delta V_1 + \Delta V_2 + \Delta V_3 = V}$$


$$\Delta V_1 = \frac{Q}{C_1}$$

$$\Delta V_2 = \frac{Q}{C_2}$$

$$\Delta V_3 = \frac{Q}{C_3}$$

$$\Delta V_1 : \Delta V_2 : \Delta V_3$$
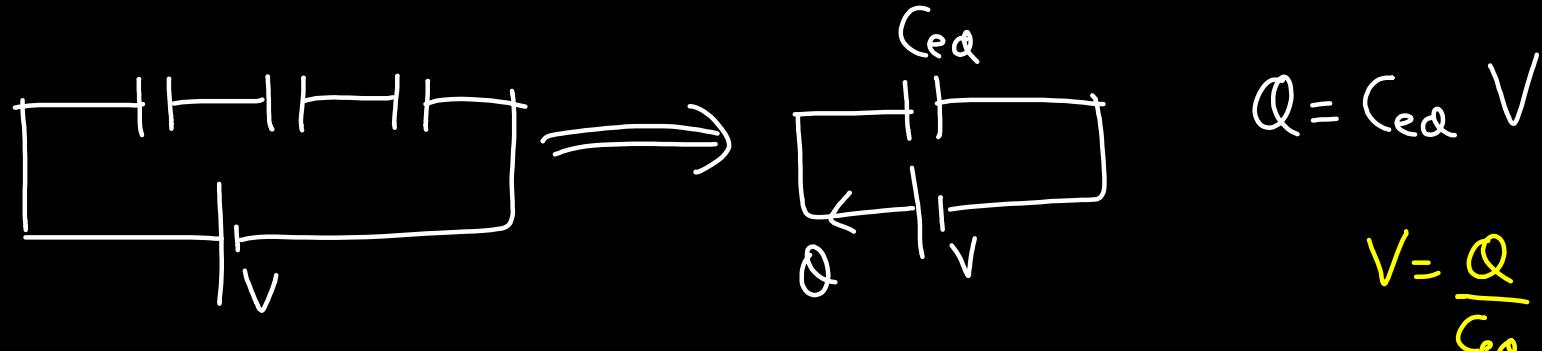
$$= \frac{1}{C_1} : \frac{1}{C_2} : \frac{1}{C_3}$$




$$V = \frac{Q}{C_1} + \frac{Q}{C_2} + \frac{Q}{C_3}$$

$$\frac{Q}{C_{eq}} =$$


$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}$$

$$\parallel C_{eq} = C_1 + C_2$$

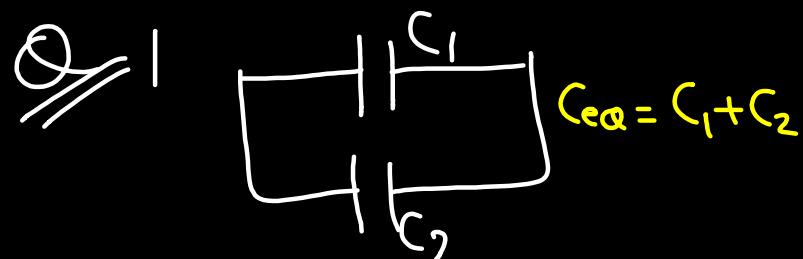
series  $\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$



$\parallel$

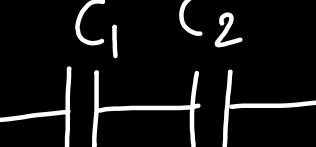

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2}$$

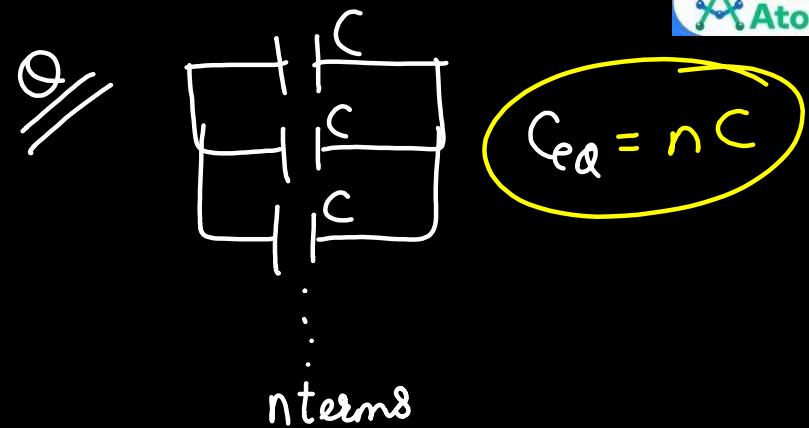

$\parallel$



n terms

$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{C} + \dots$$

$$\frac{1}{C_{eq}} = \frac{n}{C}$$

$$C_{eq} = \frac{C}{n}$$




$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{4C} + \frac{1}{8C} + \dots$$

$$= \frac{1}{C} \left( 1 + \frac{1}{2} + \frac{1}{4} + \frac{1}{8} + \dots \right)$$

$$= \frac{1}{C} \cdot \frac{a}{1-r}$$

$$\frac{1}{C_{eq}} = \frac{1}{C} \cdot \frac{(1)}{(1 - r_2)} = \frac{2}{C}$$


$$C_{eq} = C / 2$$

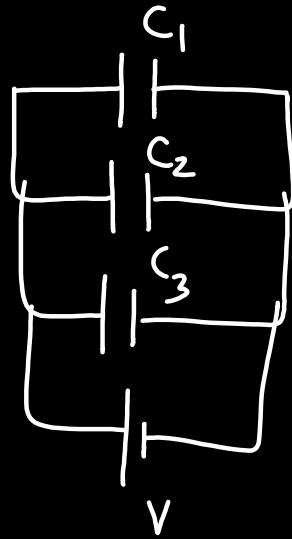


$$U = \frac{1}{2} C_1 V^2$$

$$U = \frac{1}{2} C_2 V^2$$


$$U = \frac{1}{2} C_3 V^2$$

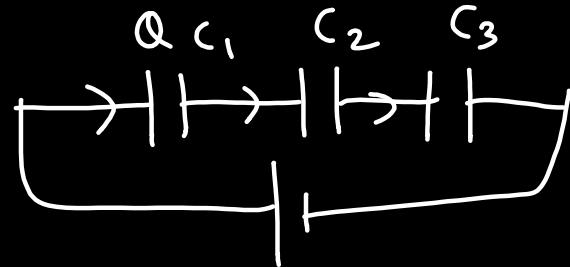
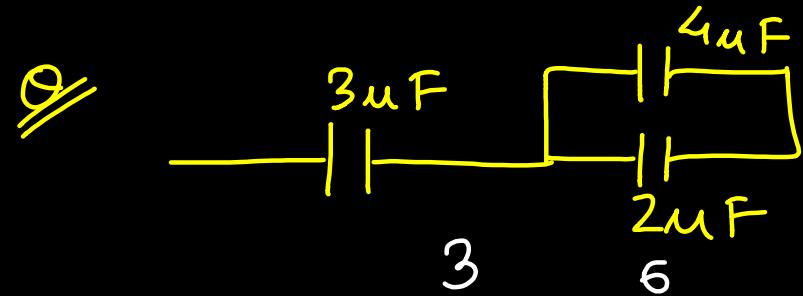
$$U = \frac{Q^2}{2C_1} + \frac{Q^2}{2C_2} + \frac{Q^2}{2C_3}$$



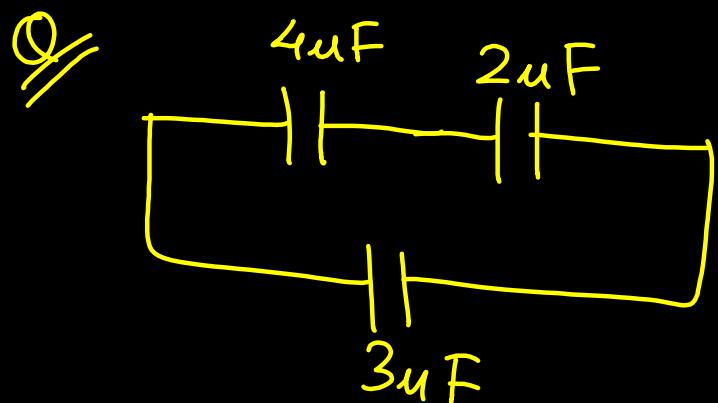
$$C_{eq} = \frac{3 \times 6}{3+6} = \frac{18}{9} = 2 \mu F$$





$$\frac{4 \times 2 \times 1}{4+2+1}$$

$$\frac{1}{3} + 3 = \frac{13}{3} \mu F$$

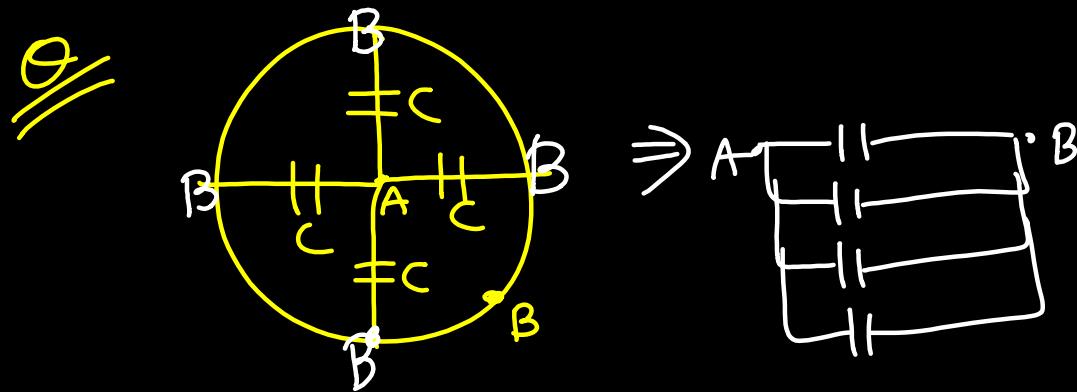


Equipotential Point Method

$\Rightarrow 4C$



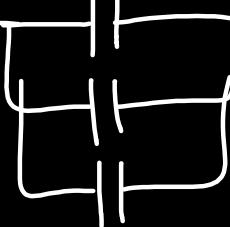
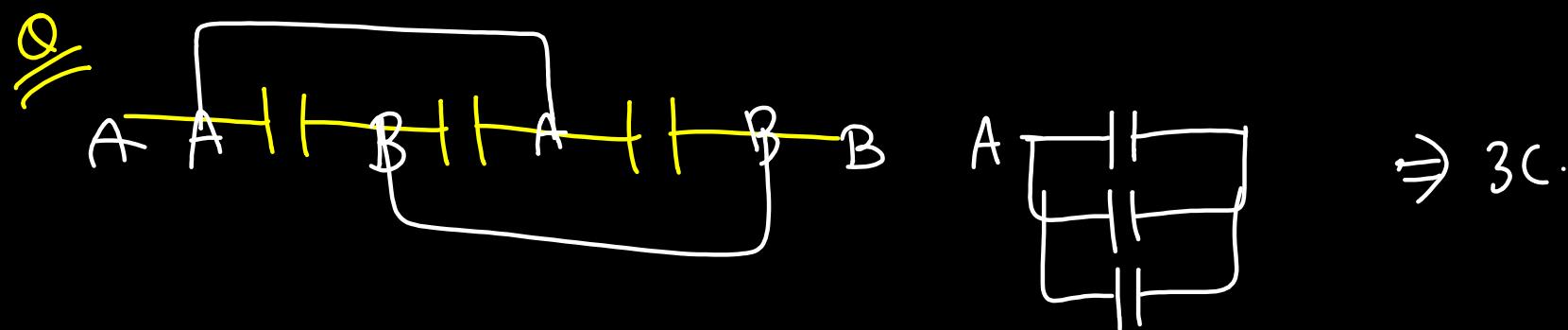


$\Rightarrow 3C$

## Wheat Stone Bridge

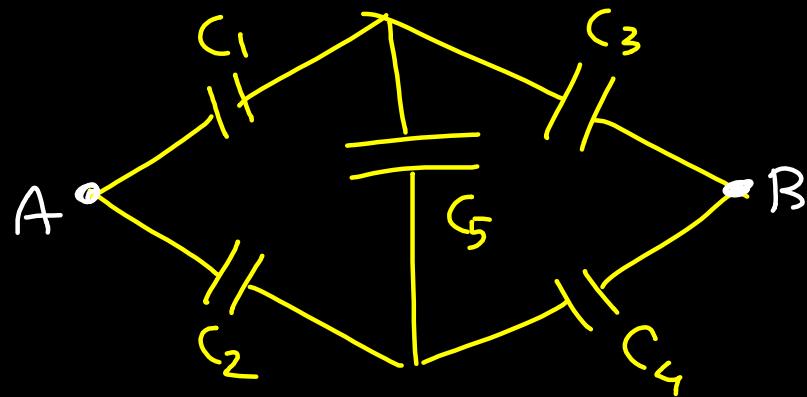

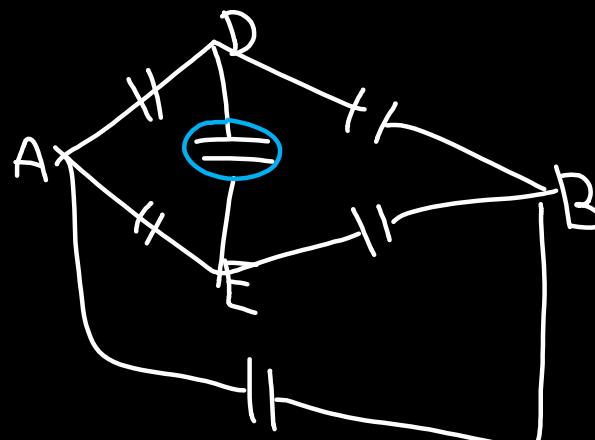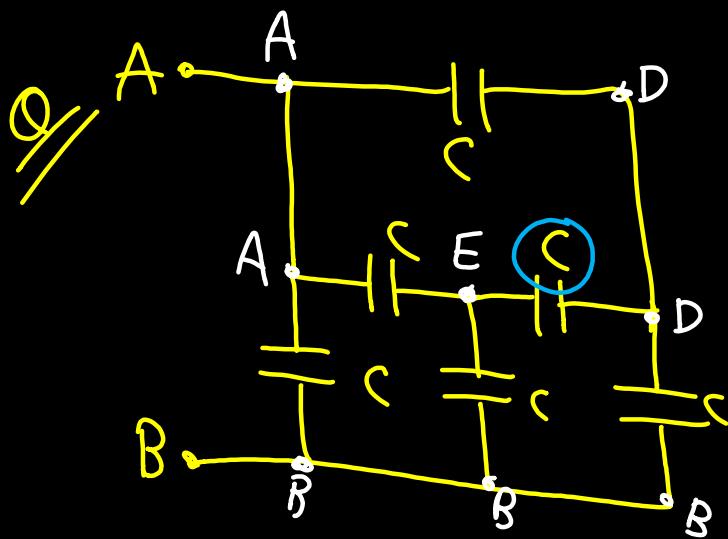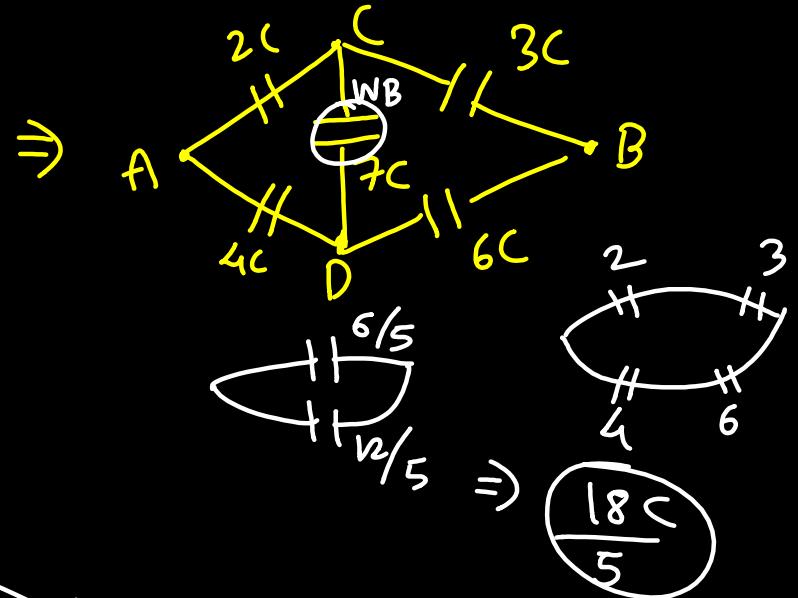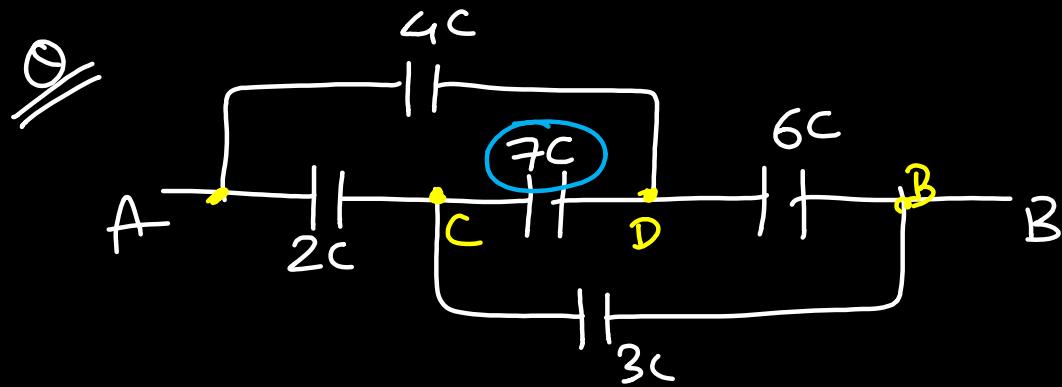
If  $\frac{C_1}{C_2} = \frac{C_3}{C_4}$  than charge on  $C_5 = 0$   
 (we can remove it)



$$\frac{C}{2} + \frac{C}{2} + C$$


$(2C)$

~~Q~~

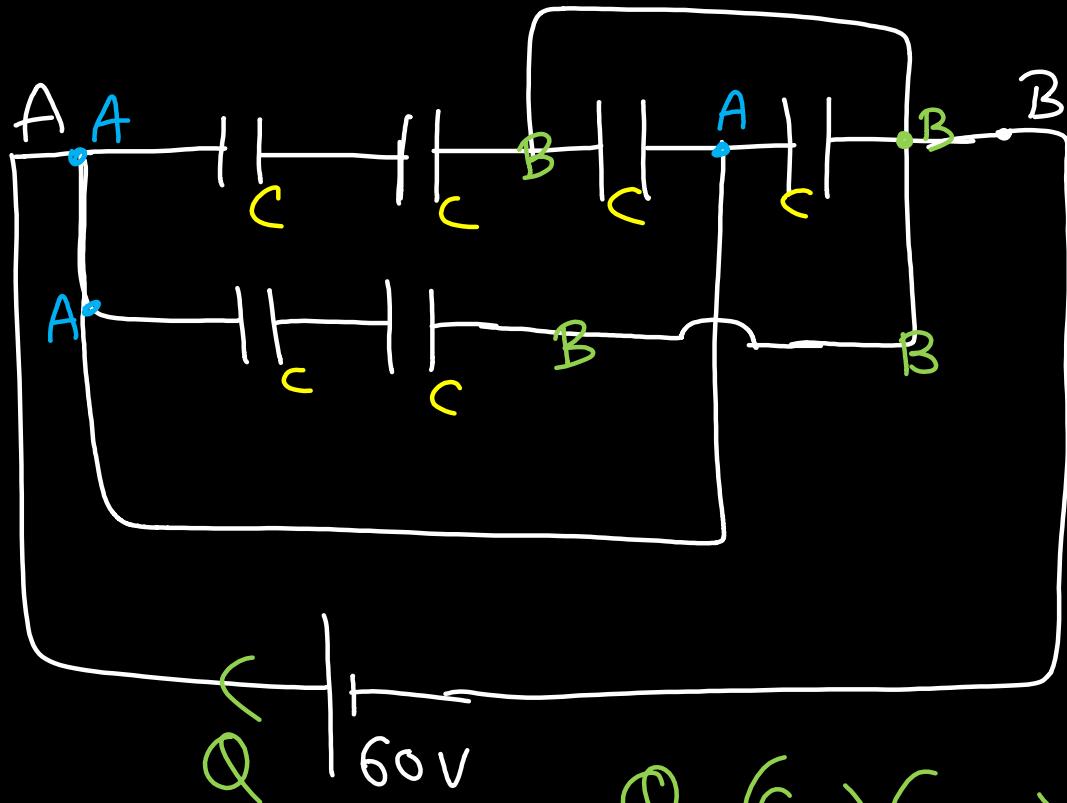


$$Q = (C_{eq})(V)$$

Find net charge  
from battery ??.

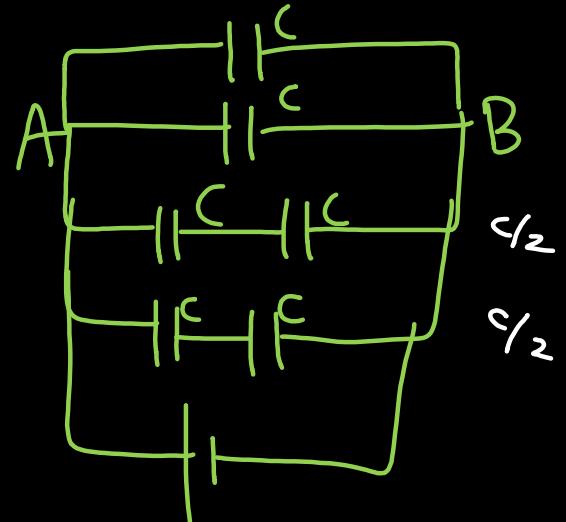

$$Q = (3C)(60) = \underline{180C}$$

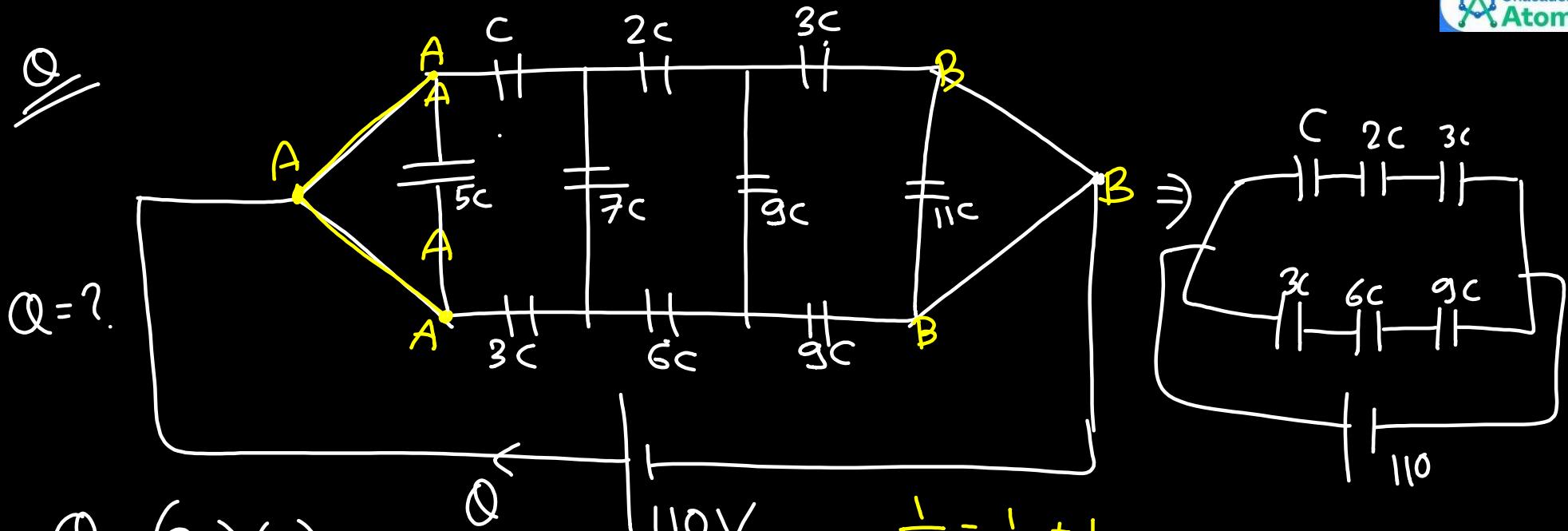

$$Q = (C_{eq})(V)$$


$$= \frac{24C}{11} \times 110$$

$$\boxed{Q = 240C}$$

$$C_{eq} = \frac{24C}{11}$$


$$\frac{1}{C_{eq}} = \frac{1}{C} + \frac{1}{2C} + \frac{1}{3C} = \frac{11}{6C} \quad C_{eq} = \frac{6C}{11}$$
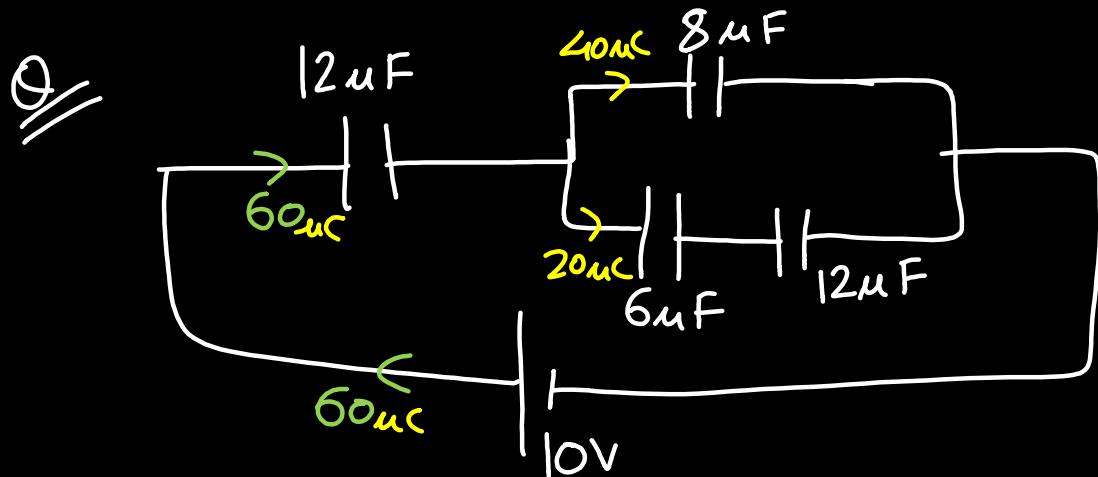
$$\frac{1}{C_{eq}} = \frac{1}{3C} \left( \frac{1}{C} + \frac{1}{2C} + \frac{1}{3C} \right) = \frac{1}{3} \frac{11}{6C} = C_{eq} \frac{18C}{11}$$



$$\frac{8 \times 12}{18} = 4$$

$\Rightarrow$

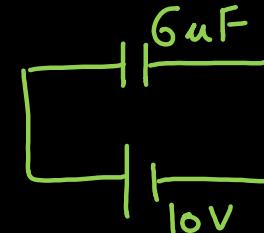


$$Q = C \cdot V$$

$$= 6 \mu F \cdot 10$$


$$Q = 60 \mu C$$

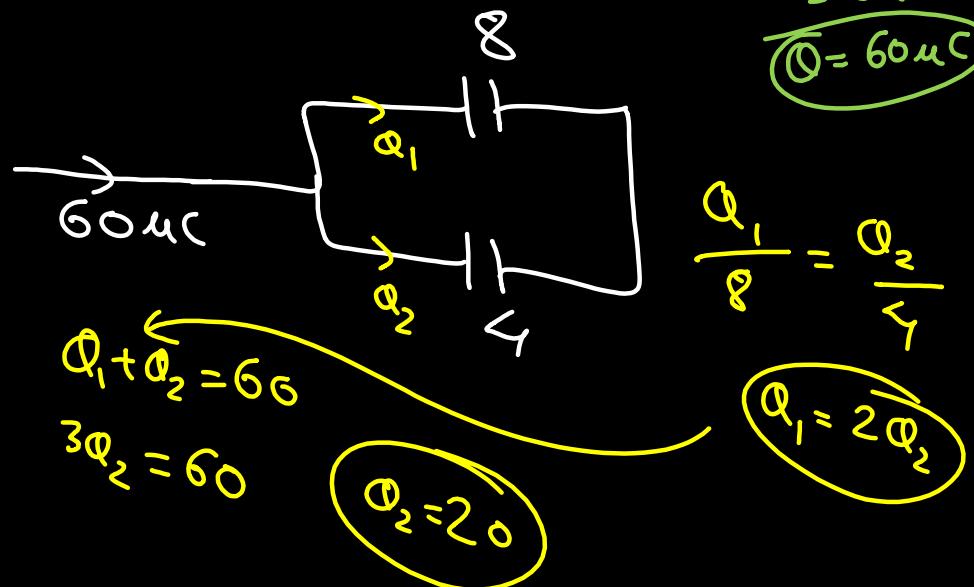- Find
- (1) charge on each C
  - (2) U stored in each C
  - (3) total charge from battery.




$$U = \frac{Q^2}{2C}$$

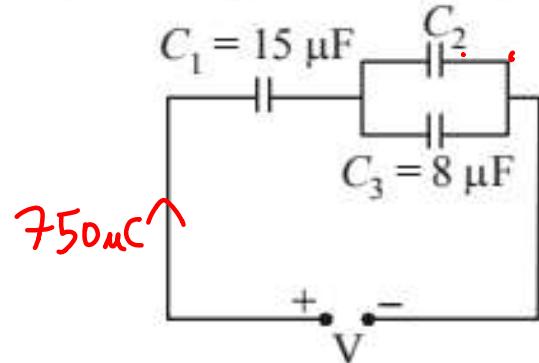In the circuit shown in the figure, the total charge is  $750 \mu\text{C}$  and the voltage across capacitor  $C_2$  is  $20 \text{ V}$ . Then the charge on capacitor  $C_2$  is : [Sep. 03, 2020 (I)]



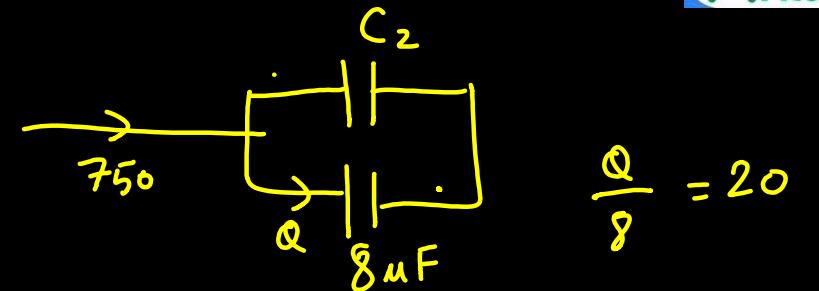- (a)  $450 \mu\text{C}$
- (b)  $590 \mu\text{C}$
- (c)  $160 \mu\text{C}$
- (d)  $650 \mu\text{C}$





$$\frac{Q}{C} = 20$$

$$Q = 160 \mu\text{C}$$

$$750 - 160 \\ = 590$$


In the given circuit, the charge on  $4 \mu\text{F}$  capacitor will be :

[12 April 2019 III]

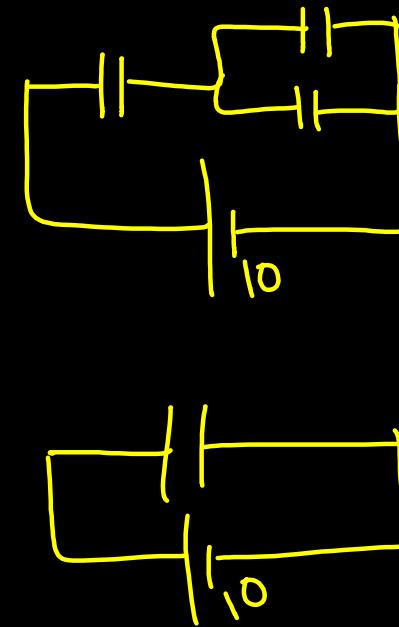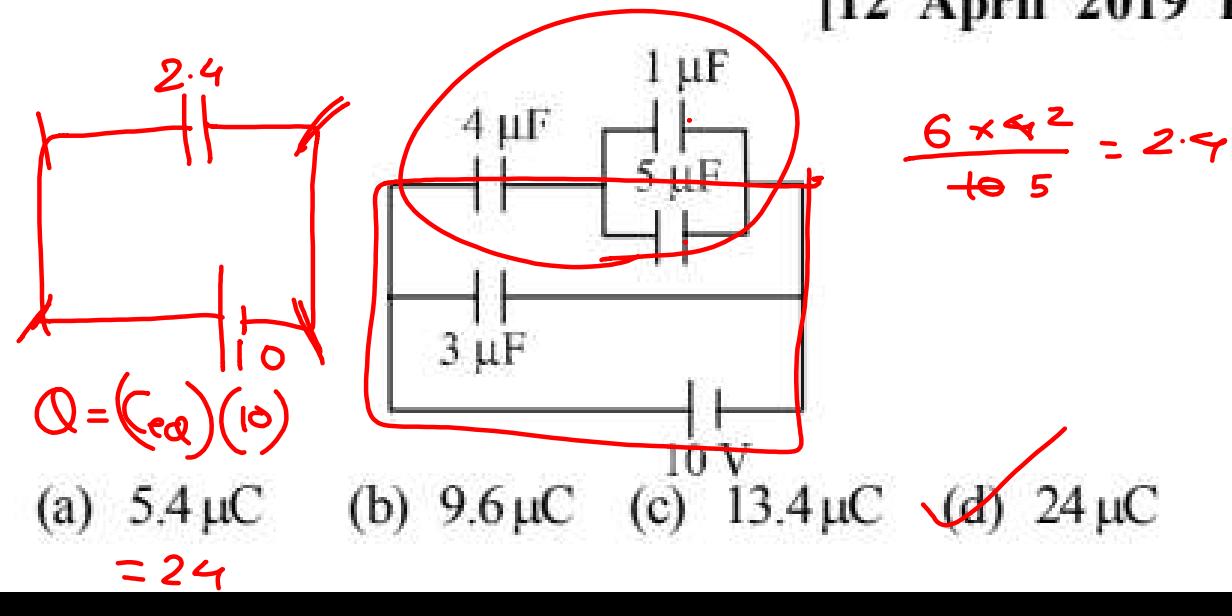


In the circuit shown, find C if the effective capacitance of the whole circuit is to be  $0.5 \mu\text{F}$ . All values in the circuit are in  $\mu\text{F}$ .

[12 Jan. 2019 II]

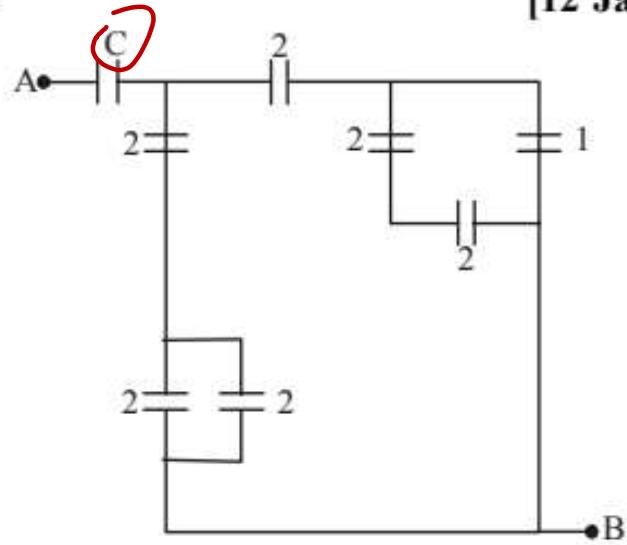


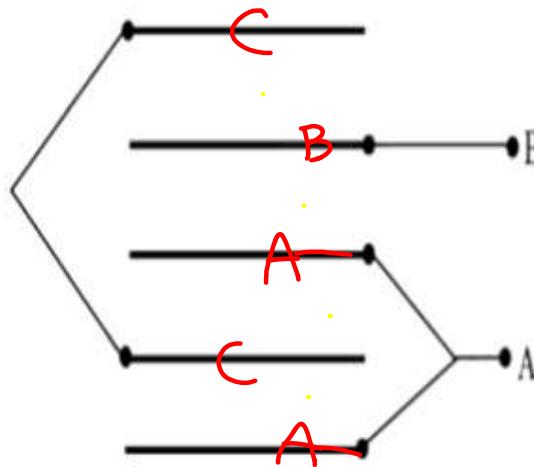- (a)  $\frac{7}{11} \mu\text{F}$    (b)  $\frac{6}{5} \mu\text{F}$    (c)  $4 \mu\text{F}$    (d)  $\frac{7}{10} \mu\text{F}$




Five identical plates of equal area  $A$  are placed parallel to each other and at equal distance  $d$  from each other as shown in fig. The effective capacity of the system between the terminals A and B is



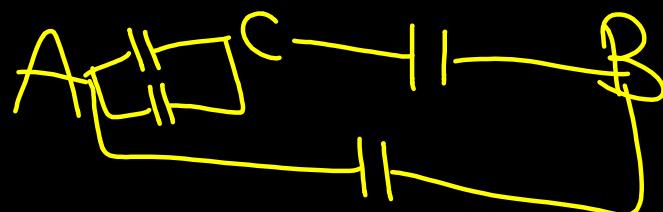- (A)  $\frac{3 \epsilon_0 A}{d}$
- (B)  $\frac{5 \epsilon_0 A}{4 d}$
- ~~(C)  $\frac{5 \epsilon_0 A}{3 d}$~~
- (D)  $\frac{4 \epsilon_0 A}{5 d}$


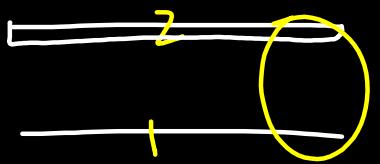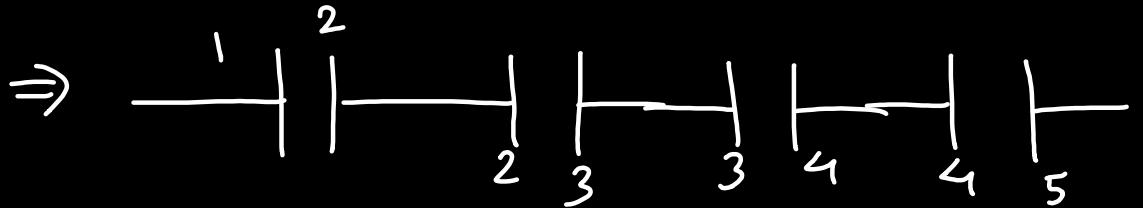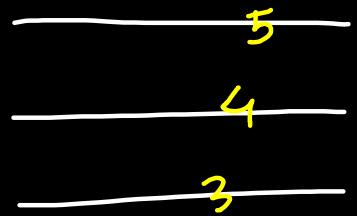
$$\Rightarrow \frac{5C}{3} = \frac{5 A \epsilon_0}{3 d}$$




$$C = \frac{A\epsilon_0}{d}$$

The total charge on the system of capacitance  $C_1 = 1\mu F$ ,  $C_2 = 2\mu F$ ,  $C_3 = 4\mu F$  and  $C_4 = 3\mu F$  connected in parallel is


(Assume a battery of 20V is connected to the combination)

- (A)  $200\mu C$       (B)  $200C$   
 (C)  $10\mu C$       (D)  $10C$

JEE MAINS 2022

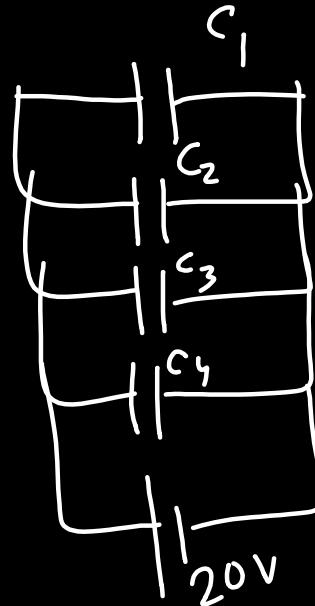

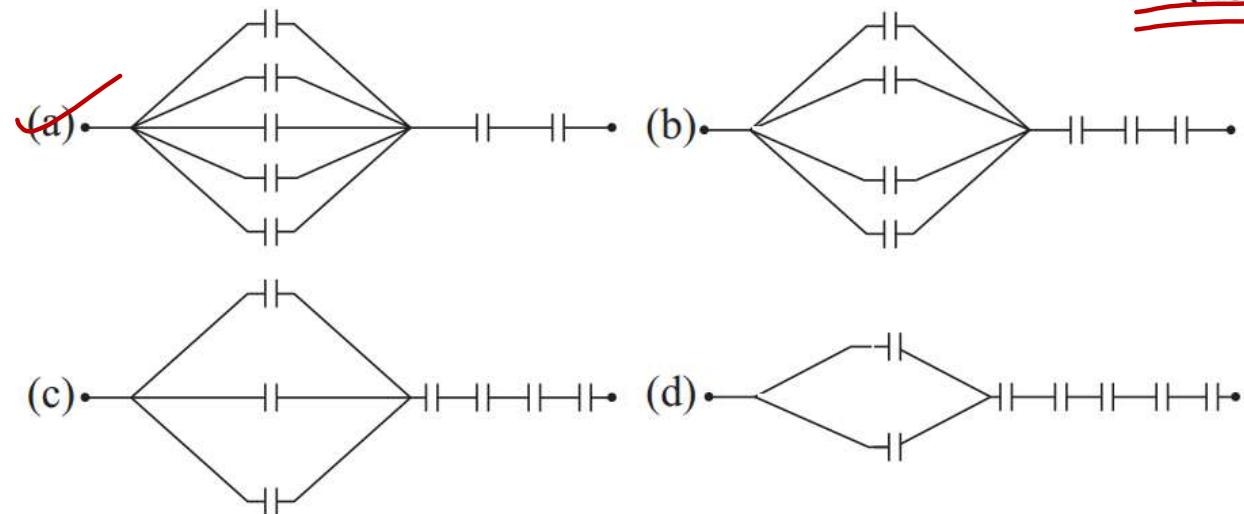Seven capacitors each of capacitance  $2\mu F$  are connected in a configuration to obtain an effective capacitance  $\frac{10}{11}\mu F$ . Which of the following combination will achieve the desired result ? (1990)



$$5C \quad C \parallel C$$


$$\frac{1}{5C} + \frac{1}{C} + \frac{1}{C} = \frac{1}{C_{eq}}$$

$$\frac{1 + 5 + 5}{5} = \frac{1}{C_{eq}}$$


$$C_{eq} = \frac{5}{11}(2)$$

In the given circuit, a charge of  $+80 \mu\text{C}$  is given to the upper plate of the  $4 \mu\text{F}$  capacitor. Then in the steady state, the charge on the upper plate of the  $3 \mu\text{F}$  capacitor is (2012)

~~H.W.~~

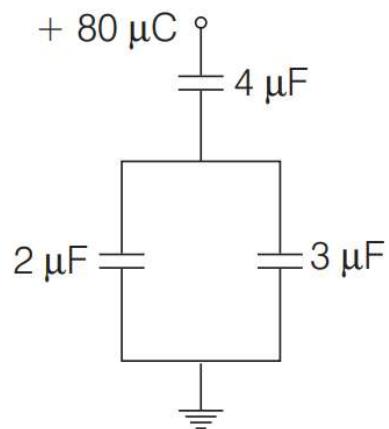


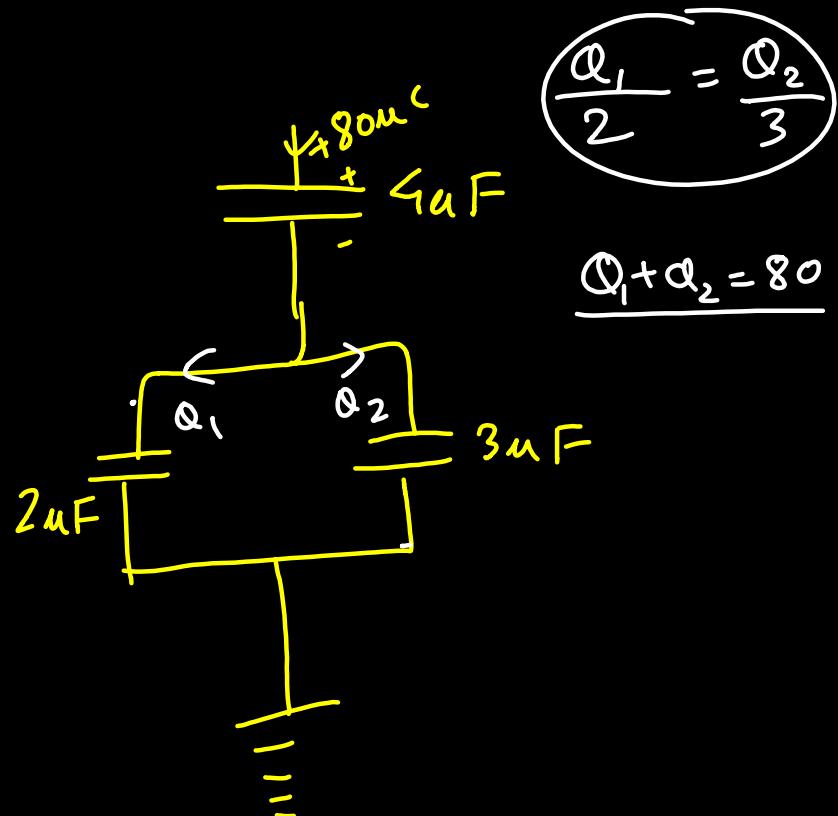- (a)  $+32 \mu\text{C}$
- (b)  $+40 \mu\text{C}$
- (c)  $+48 \mu\text{C}$
- (d)  $+80 \mu\text{C}$



In the circuit shown in the figure, there are two parallel plate capacitors each of capacitance  $C$ . The switch  $S_1$  is pressed first to fully charge the capacitor  $C_1$  and then released. The switch  $S_2$  is then pressed to charge the capacitor  $C_2$ . After some time,  $S_2$  is released and then  $S_3$  is pressed. After some time


(2013 Adv.)

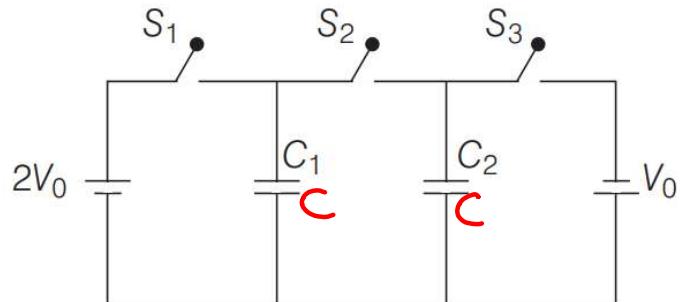

More  
than  
one  
correct

- (a) the charge on the upper plate of  $C_1$  is  $2CV_0$  ~~X~~
- (b) the charge on the upper plate of  $C_1$  is  $CV_0$  ✓
- (c) the charge on the upper plate of  $C_2$  is  $0$  ~~X~~
- (d) the charge on the upper plate of  $C_2$  is  $-CV_0$  ✓


1st

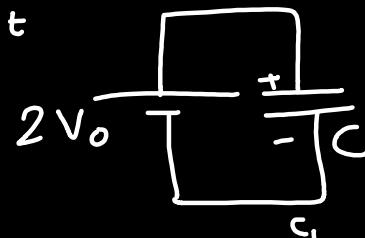



$$Q = (C)(\Delta V)$$

$$= C \cdot 2V_0$$


$$\frac{+}{-} Q = 2CV_0$$

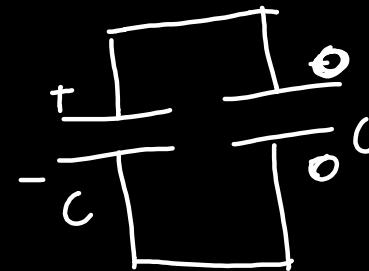

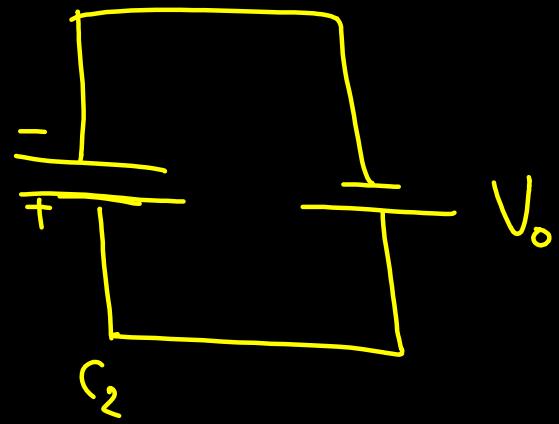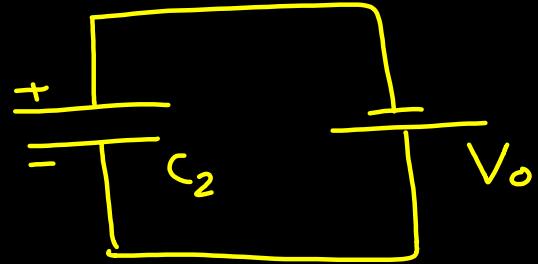
$$\Rightarrow \frac{+}{-} CV_0 \quad \frac{+}{-} CV_0$$



$$Q = (C_2)(V_o)$$

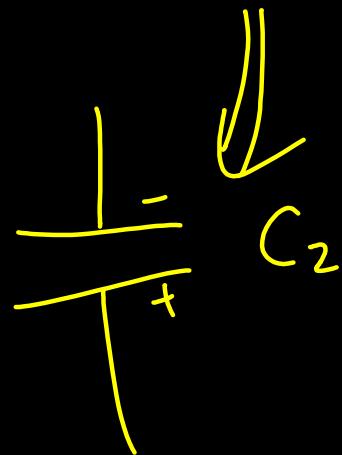

Three identical capacitors  $C_1, C_2$  and  $C_3$  have a capacitance of  $1.0\mu F$  each and they are uncharged initially. They are connected in a circuit as shown in the figure and  $C_1$  is then filled completely with a dielectric material of relative permittivity  $\epsilon_r$ . The cell electromotive force (emf)  $V_0 = 8V$ . First the switch  $S_1$  is closed while the switch  $S_2$  is kept open. When the capacitor  $C_3$  is fully charged,  $S_1$  is opened and  $S_2$  is closed simultaneously. When all the capacitors reach equilibrium, the charge on  $C_3$  is found to be  $5\mu C$ . The value of  $\epsilon_r = \dots$

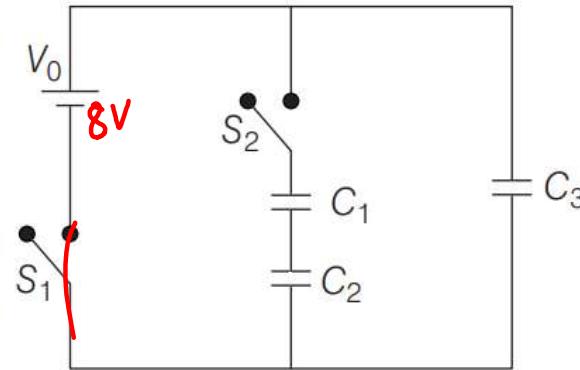


(2018 Adv.)

$$C_1 = C_2 = C_3 = 1\mu F$$



$$C = \frac{A\epsilon_0}{d}$$

$$C' = \frac{A\epsilon_0 \epsilon_r}{d}$$

$$C' = \epsilon_r C$$

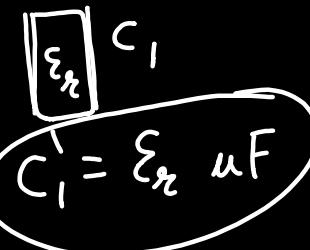

$$C' = \epsilon_r C$$

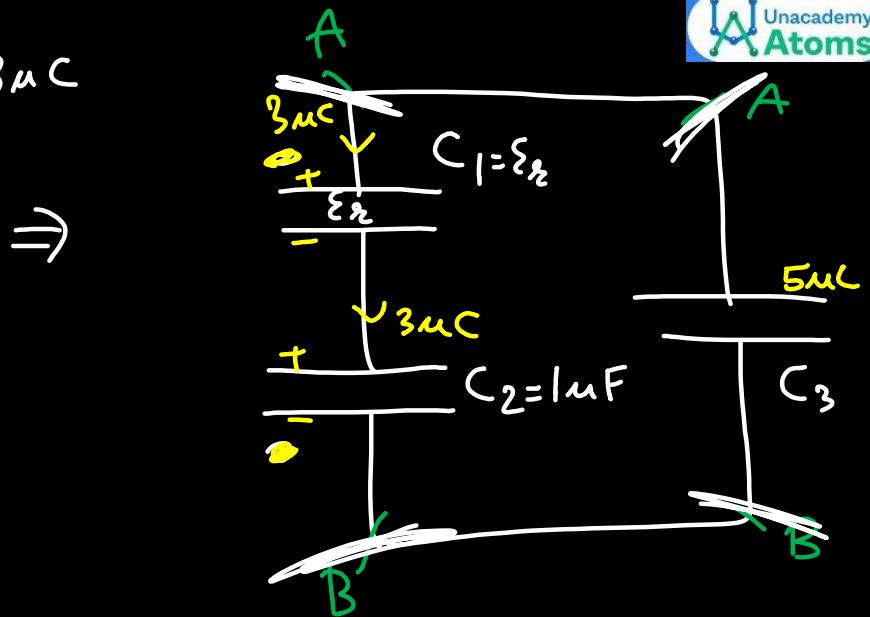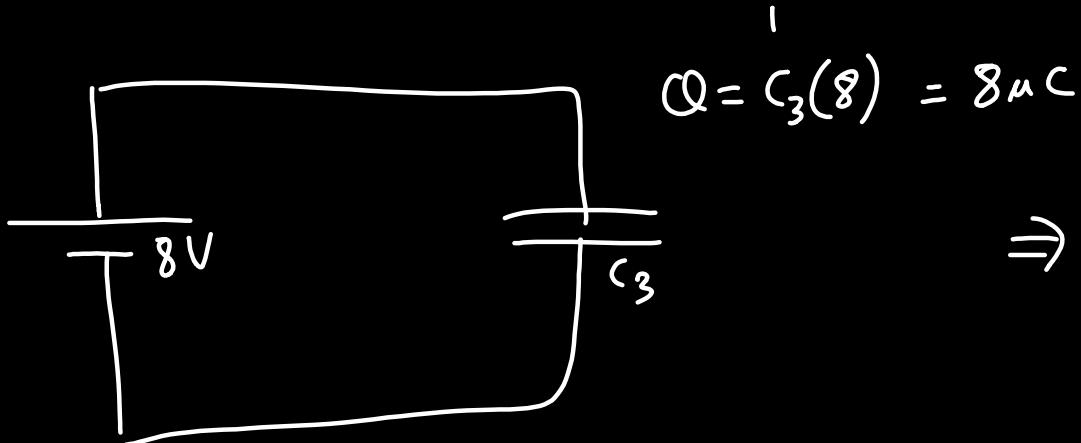

$$\frac{3}{\epsilon_r} = 2$$


$$\frac{3}{2} = \epsilon_r$$

$$1.5 = \epsilon_r$$

$$\frac{3\mu C}{\epsilon_r} + \frac{3\mu C}{1\mu F} = \frac{5\mu C}{1\mu F}$$

$$\frac{3}{\epsilon_r} + 3 = 5$$



Two capacitors  $A$  and  $B$  with capacities  $3\mu\text{F}$  and  $2\mu\text{F}$  are charged to a potential difference of  $100\text{ V}$  and  $180\text{ V}$  respectively. The plates of the capacitors are connected as shown in the figure with one wire of each capacitor free. The upper plate of  $A$  is positive and that of  $B$  is negative. An uncharged  $2\mu\text{F}$  capacitor  $C$  with lead wires falls on the free ends to complete the circuit. Calculate (1997)

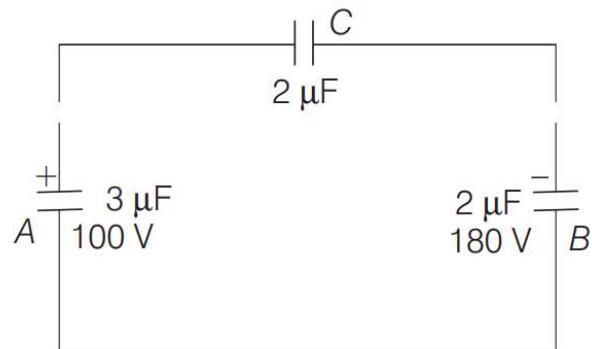

- (a) the final charge on the three capacitors and
- (b) the amount of electrostatic energy stored in the system before and after completion of the circuit.

## Folding Symmetry

$\cong$

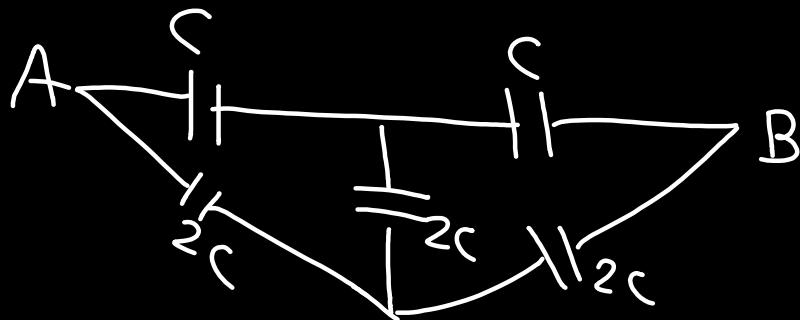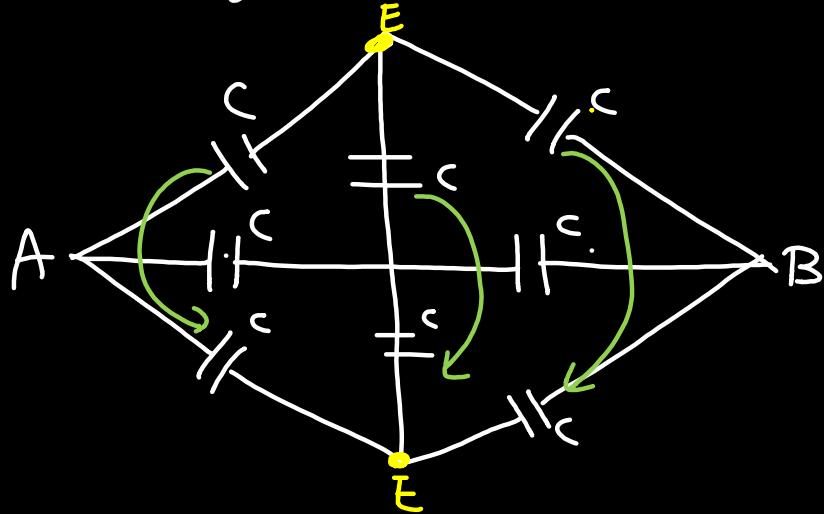

Find  $C_{eq} = ?$  b/w AB



# AB itself is line of symmetry.

→ can be folded about AB  
 → Mirror images Points  
 are equipotential.



$$\frac{C}{2} = \frac{3c}{2}$$

## Connection Removal

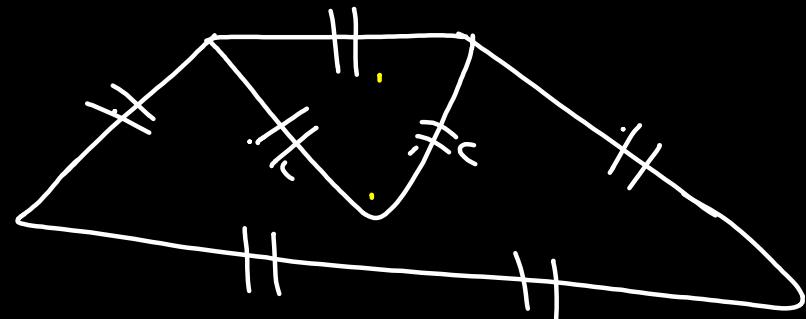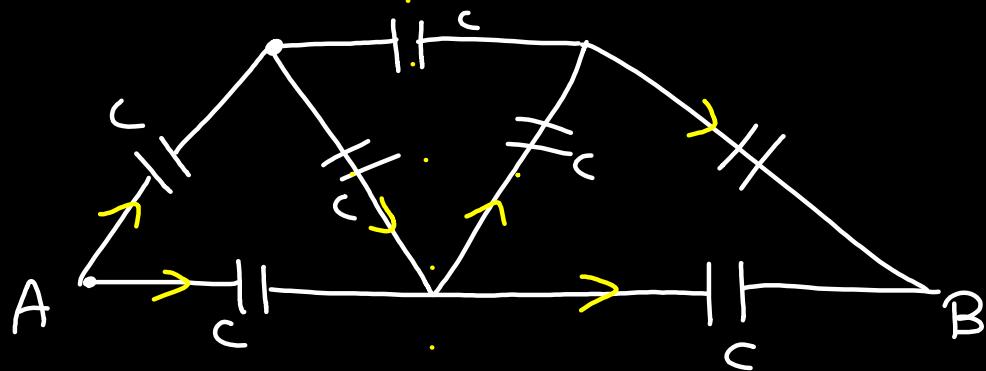


# line  $L'$  w.r.t AB is line of symmetry.

→ all points lying on this  $L'$  w.r.t line is equipotential

mirror image C  ~~$\frac{3c}{8}$~~


Same charge
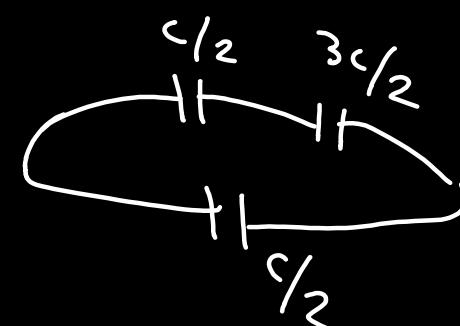
$$\frac{c/2}{c/2} \frac{3c/2}{c/2} = \frac{3c}{8}$$




$$\frac{3c}{8} + \frac{c}{2} = \frac{7c}{8}$$

∞ ladder

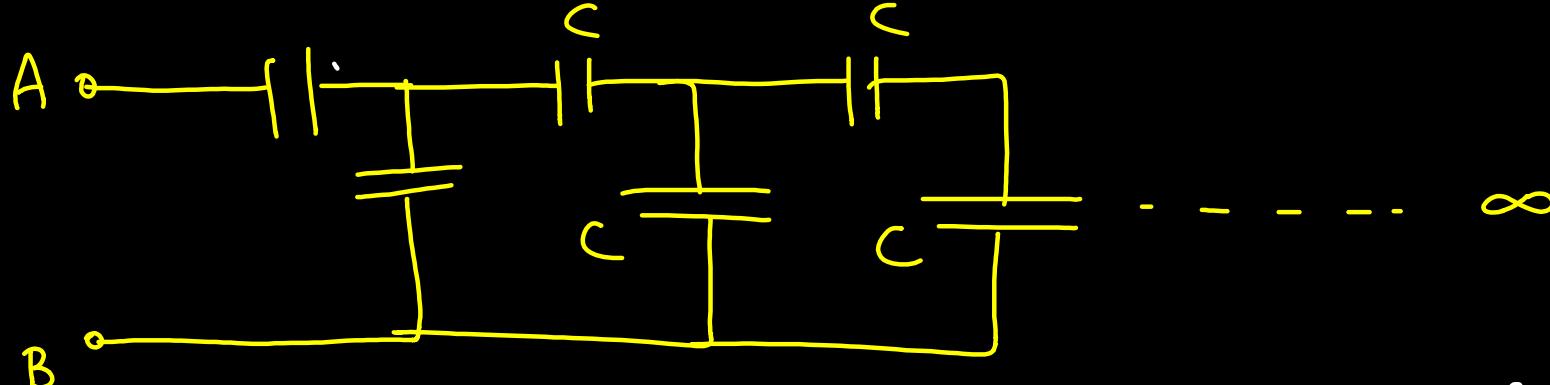

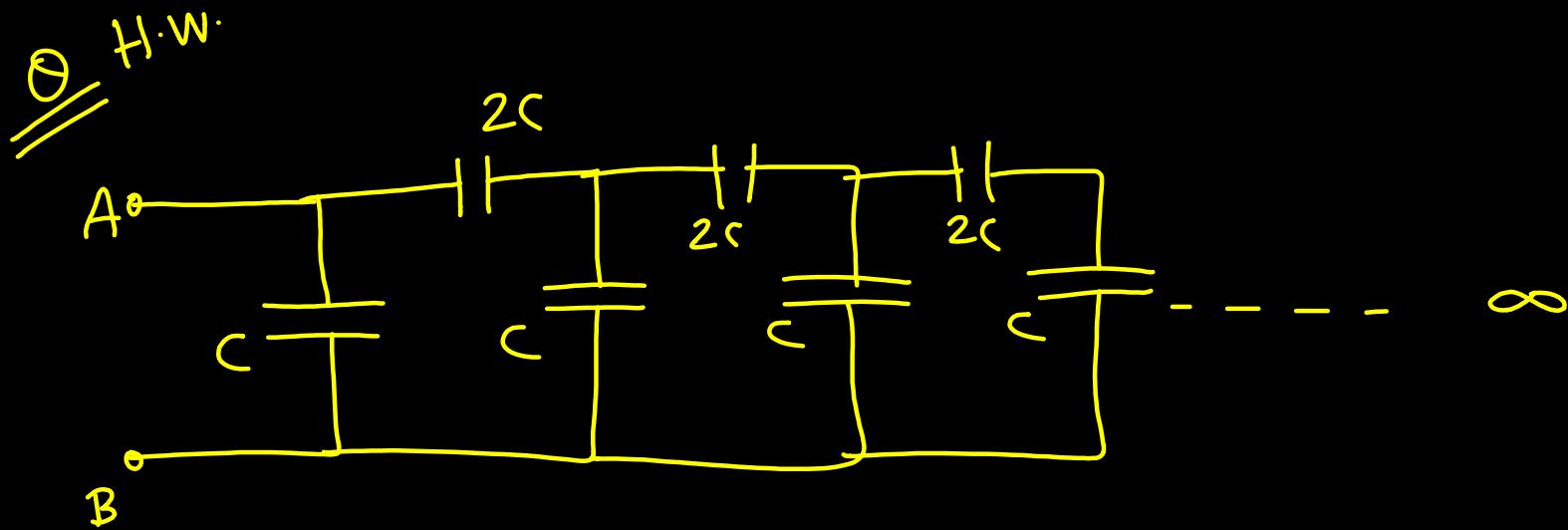
$$\begin{aligned}
 & A \xrightarrow{\text{---}} X = A \xrightarrow{\text{---}} \frac{C}{1+C} X = \frac{C}{1+C} (X+C) \\
 & X = \frac{(X+C)(C)}{X+C+C} \\
 & \Rightarrow X^2 + 2XC = XC + C^2 \\
 & X^2 + XC - C^2 = 0 \\
 & X = \frac{-C + \sqrt{5C^2}}{2} \\
 & X = \left(\frac{\sqrt{5}-1}{2}\right)C
 \end{aligned}$$




Check if Ans  
 $X = 2C$

## Cube Standard Result

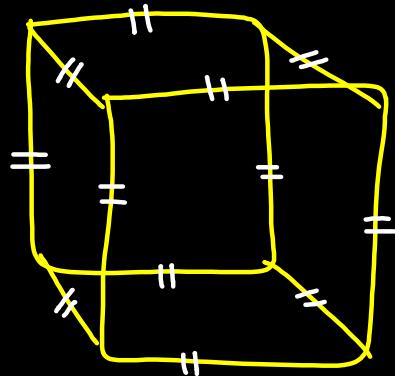


Find eq capacitance

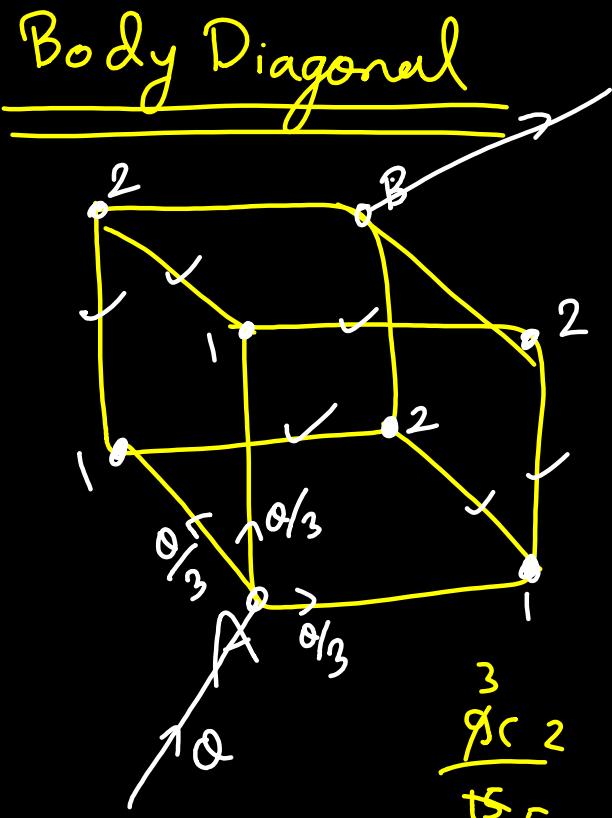
- ① about Body diagonal
- ② " Face "
- ③ about edge





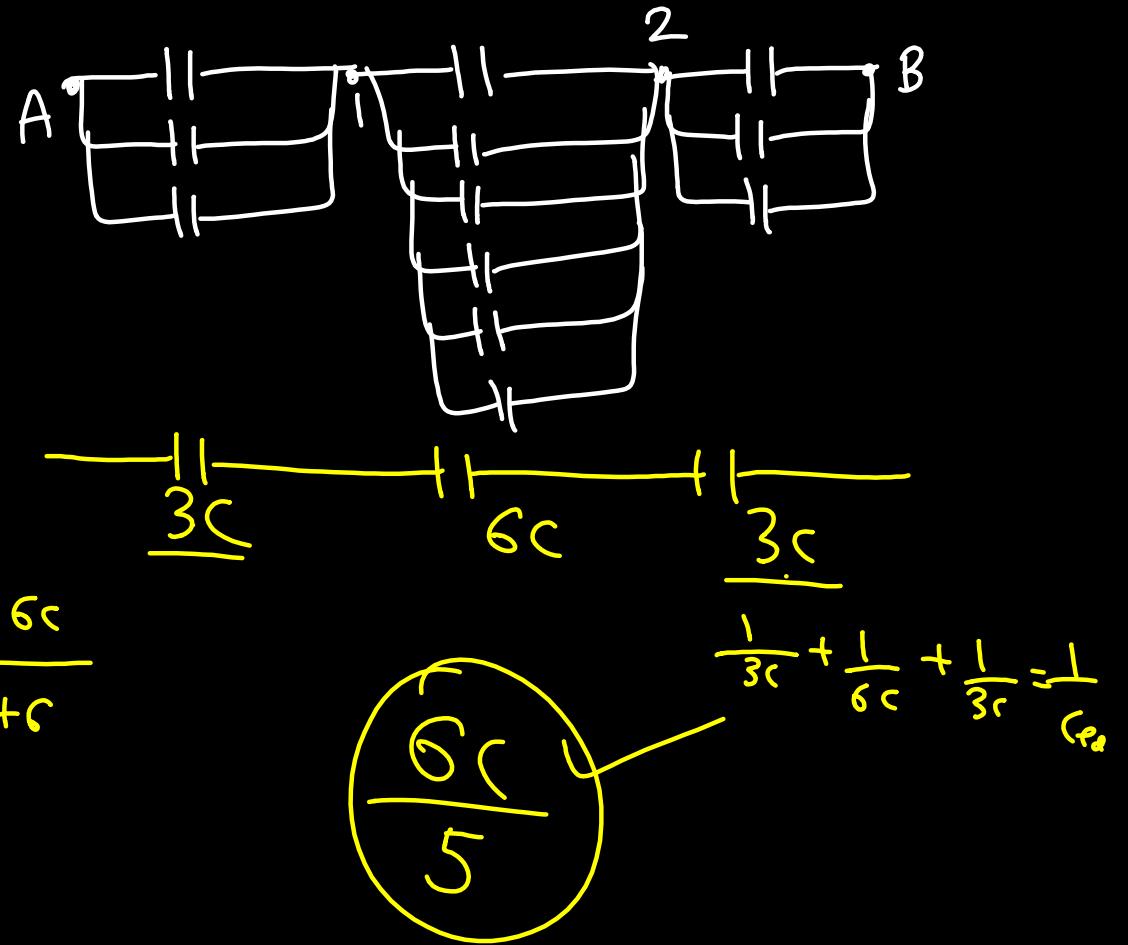
$$\frac{3}{\cancel{9}c} = \frac{\frac{3c}{2} \times 6c}{\frac{3c}{2} + 6}$$




Face Diagonal

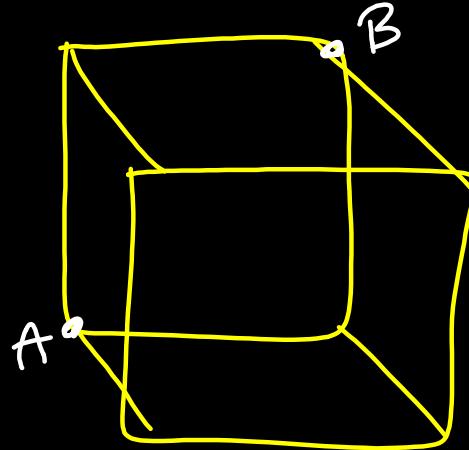




Fold

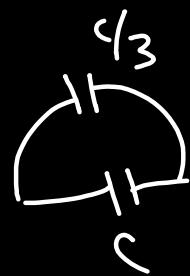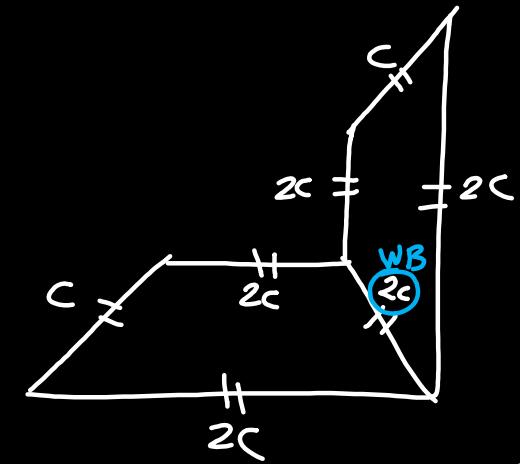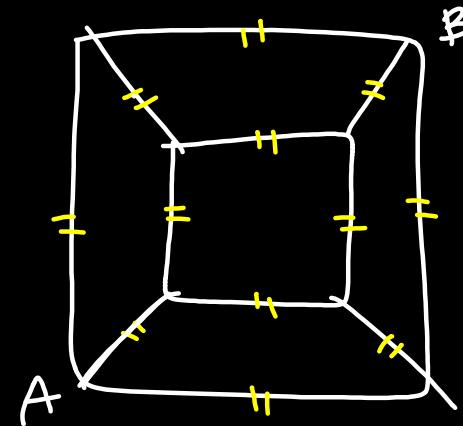

$$= \frac{\pi c^2}{3}$$

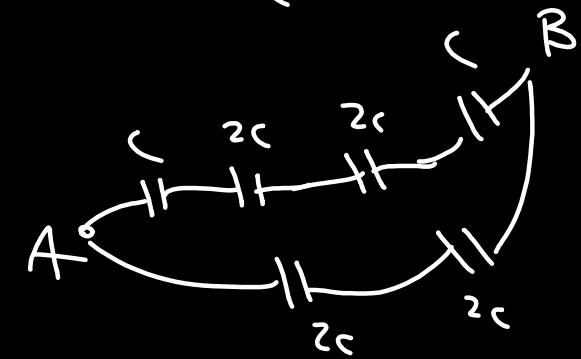

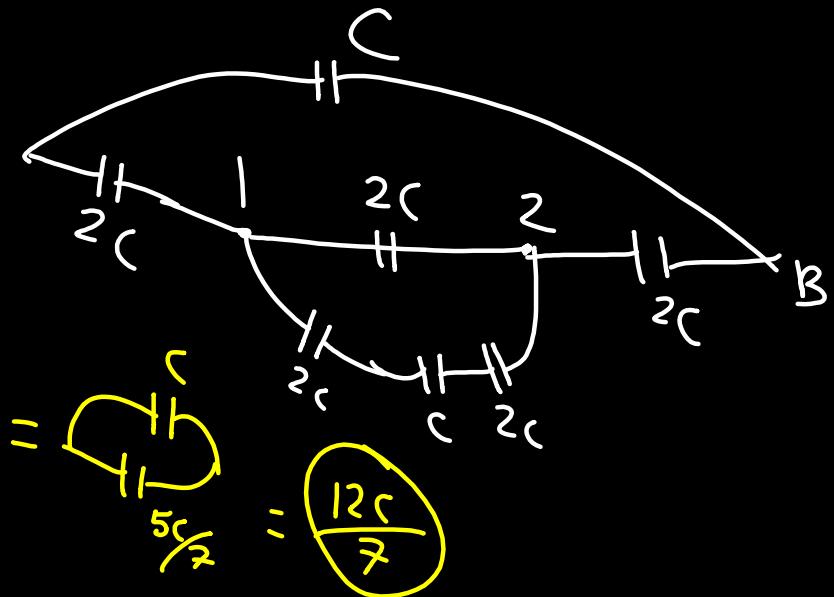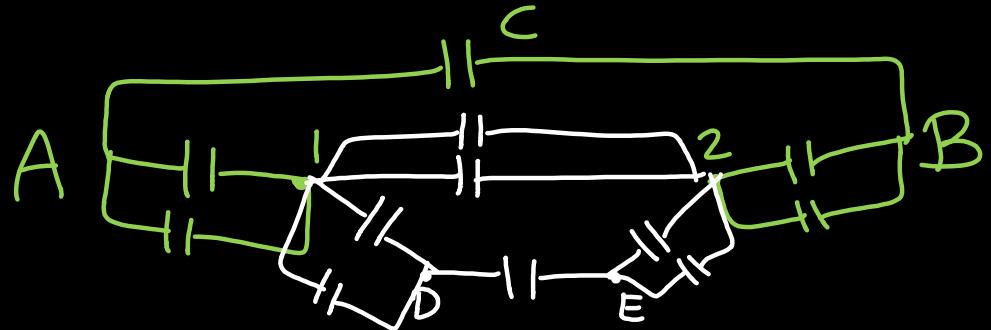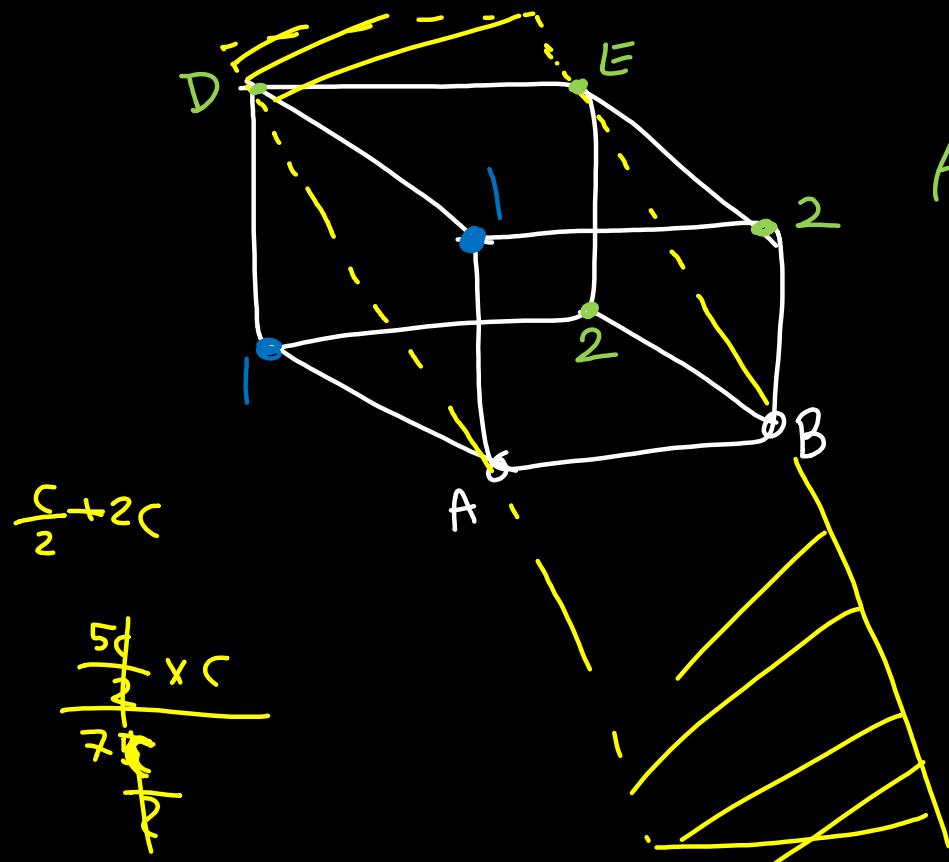Edge (plane of symmetry)  $\Rightarrow$  (mirror image same potential)



## EFFECT OF DIELECTRIC

- The insulators in which microscopic local displacement of charges takes place in presence of electric field are known as dielectrics.
- Dielectrics are non conductors up to certain value of field depending on its nature. If the field exceeds this limiting value called dielectric strength they lose their insulating property and begin to conduct.
- Dielectric strength is defined as the maximum value of electric field that a dielectric can tolerate without breakdown. Unit is volt/meter. Dimensions  $M^1 L^1 T^{-3} A^{-1}$

### Polar dielectrics

- In absence of external field the centers of positive and negative charge do not coincide-due to asymmetric shape of molecules.
- Each molecule has permanent dipole moment.
- The dipole are randomly oriented so average dipole moment per unit volume of polar dielectric in absence of external field is nearly zero.
- In presence of external field dipoles tends to align in direction of field.  
Ex. Water, Alcohol,  $CO_2$ ,  $HCl$ ,  $NH_3$

## Non polar dielectrics

- In absence of external field the center of positive and negative charge coincides in these atoms or molecules because they are symmetric.
- The dipole moment is zero in normal state.
- In presence of external field they acquire induced dipole moment.  
Ex. Nitrogen, Oxygen, Benzene, Methane

## Polarisation

The alignment of dipole moments of permanent or induced dipoles in the direction applied electric field is called polarization .


Polarization vector  $\vec{P}$  - This is a vector quantity which describes the extent to which molecules of dielectric become polarized by an electric field or oriented in direction of field.

$\vec{P} = \text{the dipole moment per unit volume of dielectric} = n\vec{p}$

where  $n$  is number of atoms per unit volume of dielectric and  $\vec{p}$  is dipole moment of an atom or molecule.

$\vec{P} = n\vec{p} = \frac{q_i d}{A_d} = \left(\frac{q_i}{A}\right) = \sigma_i$  = induced surface charge density.

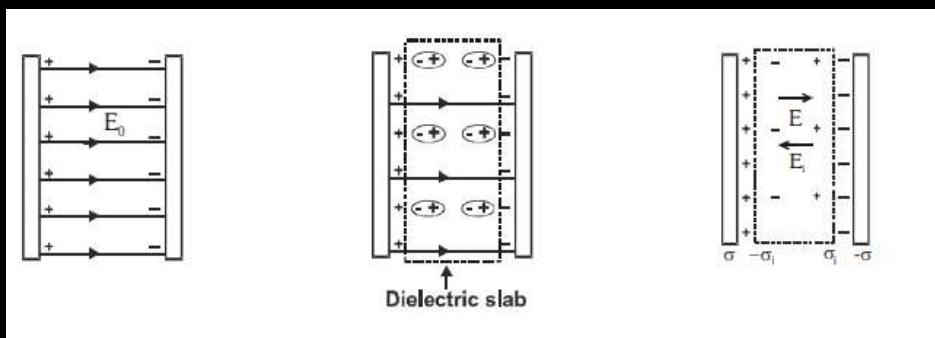Unit of  $\vec{P}$  is  $C/m^2$  Dimension is  $L^{-2} T^1 A^1$



Let  $E_0, V_0, C_0$  be electric field, potential difference and capacitance in absence of dielectric. Let  $E, V, C$  are electric field, potential difference and capacitance in presence of dielectric respectively.

$$\text{Electric field in absence of dielectric } E_0 = \frac{V_0}{d} = \frac{\sigma}{\epsilon_0} = \frac{Q}{\epsilon_0 A}$$

$$\text{Electric field in presence of dielectric } E = E_0 - E_i = \frac{\sigma - \sigma_i}{\epsilon_0} = \frac{Q - Q_i}{\epsilon_0} = \frac{V}{d}$$

$$\text{Capacitance in absence of dielectric } C_0 = \frac{Q}{V_0}$$

$$\text{Capacitance in Presence of dielectric } C = \frac{Q - Q_i}{V}$$

$$\text{The dielectric constant or relative permittivity } K \text{ or } \epsilon_r = \frac{F_0}{E} = \frac{V_0}{V} = \frac{C}{C_0} = \frac{Q}{Q - Q_i} = \frac{\sigma}{\sigma - \sigma_i} = \frac{\epsilon}{\epsilon_0}$$

$$\text{From } K = \frac{Q}{Q - Q_i} \Rightarrow Q_i = Q \left(1 - \frac{1}{K}\right) \text{ and } K = \frac{\sigma}{\sigma - \sigma_i} \Rightarrow \sigma_i = \sigma \left(1 - \frac{1}{K}\right)$$

## Capacity of Different Configurations

In case of parallel plate capacitor  $C = \frac{\epsilon_0 A}{d}$


If capacitor is partially filled with dielectric

When the dielectric is filed partially between plates, the thickness of dielectric slab is  $t(t < d)$ .

If no slab is introduced between the plates of the capacitor, then a field  $E_0$  given by  $E_0 = \frac{\sigma}{\epsilon_0}$ , exists in a space  $d$ . On inserting the slab of thickness  $t$  and a field  $E = \frac{E_0}{\epsilon_r}$  exists inside the slab of thickness  $t$  and a field  $E_0$  exists in remaining space  $(d - t)$ . If  $V$  is total potential then  $V = E_0(d - t) + Et \Rightarrow$



$$V = E_0 \left[ d - t + \left( \frac{E}{E_0} \right) t \right] \because \frac{E_0}{E} = \epsilon_r = \text{Dielectric constant}$$
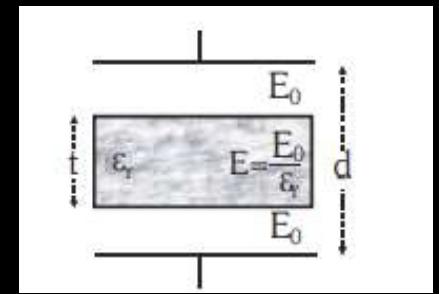
$$\Rightarrow V = \frac{\sigma}{\epsilon_0} \left[ d - t + \frac{t}{\epsilon_r} \right] = \frac{q}{A\epsilon_0} \left[ d - t + \frac{t}{\epsilon_r} \right] \Rightarrow C = \frac{q}{V} = \frac{\epsilon_0 A}{d - t \left( 1 - \frac{1}{\epsilon_r} \right)}$$



If medium is fully present between the space.  $\because t = d$  Now from equation (i)  $C_{\text{medium}} = \frac{\epsilon_0 \epsilon_r A}{d}$

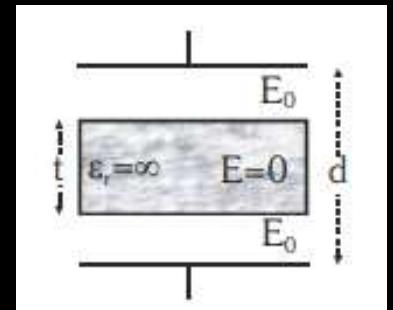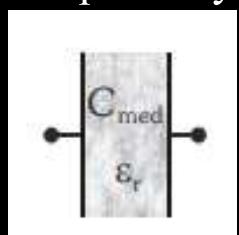If capacitor is partially filled by a conducting slab of thickness ( $t < d$ ).



### 8.3 Distance and area division by dielectric

#### Distance Division


(i) Distance is divided and area remains same.

(ii) Capacitors are in series.

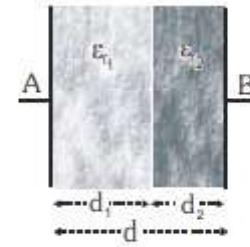(iii) Individual capacitances are  $C_1 = \frac{\epsilon_0 \epsilon_r A}{d_1}$ ,  $C_2 = \frac{\epsilon_0 \epsilon_r A}{d_2}$

These two in series  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C} = \frac{d_1}{\epsilon_0 \epsilon_{r_1} A} + \frac{d_2}{\epsilon_0 \epsilon_{r_2} A}$

$$\Rightarrow \frac{1}{C} = \frac{1}{\epsilon_0 A} \left[ \frac{d_1 \epsilon_{r_2} + d_2 \epsilon_{r_1}}{\epsilon_{r_1} \epsilon_{r_2}} \right] \Rightarrow C = \epsilon_0 A \left[ \frac{\epsilon_{r_1} \epsilon_{r_2}}{d_1 \epsilon_{r_2} + d_2 \epsilon_{r_1}} \right]$$



These two in series  $\frac{1}{C} = \frac{1}{C_1} + \frac{1}{C_2} \Rightarrow \frac{1}{C} = \frac{d_1}{\epsilon_0 \epsilon_{r1} A} + \frac{d_2}{\epsilon_0 \epsilon_{r2} A}$

$$\Rightarrow \frac{1}{C} = \frac{1}{\epsilon_0 A} \left[ \frac{d_1 \epsilon_{r2} + d_2 \epsilon_{r1}}{\epsilon_{r1} \epsilon_{r2}} \right] \Rightarrow C = \epsilon_0 A \left[ \frac{\epsilon_{r1} \epsilon_{r2}}{d_1 \epsilon_{r2} + d_2 \epsilon_{r1}} \right]$$

Special case - If  $d_1 = d_2 = \frac{d}{2} \Rightarrow C = \frac{\epsilon_0 A}{d} \left[ \frac{2 \epsilon_{r1} \epsilon_{r2}}{\epsilon_{r1} + \epsilon_{r2}} \right]$

### Area Division

- (i) Area is divided and distance remains same.
- (ii) Capacitors are in parallel.

(iii) Individual capacitances are  $C_1 = \frac{\epsilon_0 \epsilon_{r1} A_1}{d} C_2 = \frac{\epsilon_0 \epsilon_{r2} A_2}{d}$

These two in parallel so  $C = C_1 + C_2 = \frac{\epsilon_0 \epsilon_{r1} A_1}{d} + \frac{\epsilon_0 \epsilon_{r2} A_2}{d} = \frac{\epsilon_0}{d} (\epsilon_{r1} A_1 + \epsilon_{r2} A_2)$

Special case - If  $A_1 = A_2 = \frac{A}{2}$  Then  $C = \frac{\epsilon_0 A}{d} \left( \frac{\epsilon_{r1} + \epsilon_{r2}}{2} \right)$



## Variable Dielectric Constant –

If the dielectric constant is variable, then equivalent capacitance can be obtained by selecting an element as per the given condition and then integrating.

- (i) If different elements are in parallel, then  $C = \int dC$ , where  $dC$  - capacitance of selected differential element.
- (ii) If different elements are in series, then  $\frac{1}{C} = \int d\left(\frac{1}{C}\right)$  is solved to get equivalent capacitance  $C$ .


## Force on a Dielectric in a capacitor

Consider a differential displacement  $dx$  of the dielectric as shown in figure always keeping the net force on it zero so that the dielectric moves slowly without acceleration. Then,  $W_{\text{Electrostatic}} + W_F = 0$ , where  $W_F$  denotes the work done by external agent in displacement  $dx$

$$W_F = -W_{\text{Electrostatic}} \quad W_F = \Delta U$$

$$\Rightarrow -F \cdot dx = \frac{Q^2}{2} d \left[ \frac{1}{C} \right] \quad W = \frac{Q^2}{2C}$$
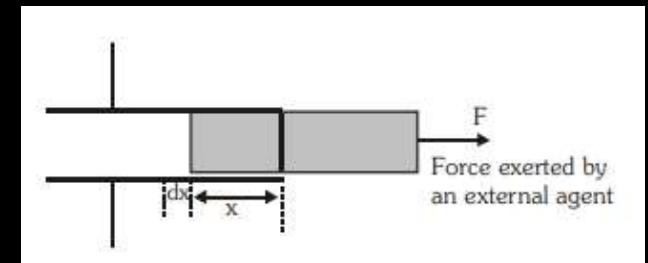
$$\Rightarrow -F \cdot dx = \frac{-Q^2}{2C^2} dC \Rightarrow F = \frac{Q^2}{2C^2} \left( \frac{dC}{dx} \right)$$



This is also true for the force between the plates of the capacitor. If the capacitor has battery connected to it, then as the p . d. V across the plates is maintained constant.  $F = \frac{1}{2} V^2 \frac{dC}{dx}$ .

## Dielectric without battery

As shown in figure, a battery with a potential difference  $|\Delta V_0|$  across its terminals is first connected to a capacitor  $C_0$ , which holds a charge  $Q_0 = C_0 |\Delta V_0|$ . We then disconnect the battery, leaving  $Q_0 = \text{constant}$ .

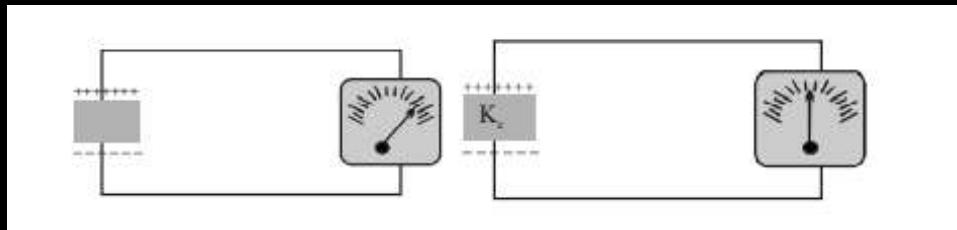


Figure : Inserting a dielectric material between the capacitor plates while keeping the charge  $Q_0$  constant


If we then insert a dielectric between the plates, while keeping the charge constant, experimentally it is found that the potential difference decreases by a factor of  $K_e$ .

$$|\Delta V_0| = \frac{|\Delta V_0|}{K_e}$$

This implies that the capacitance is changed to  $C = \frac{Q}{|\Delta V_0|} = \frac{Q}{|\Delta V_0|/K_e} = K_e \frac{Q}{|\Delta V_0|} = K_e C_0$ . Thus, we see that the capacitance has increased by a factor of  $K_e$ . The electric field within the dielectric is now

$$E = \frac{|\Delta V|}{d} = \frac{|\Delta V_0|/K_e}{d} = \frac{1}{K_e} \left( \frac{|\Delta V_0|}{d} \right) = \frac{E_0}{K_e}$$

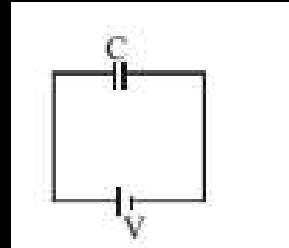We see that in the presence of a dielectric, the electric field decreases by a factor of  $K_e$ .



EFFECT ON :	BEFORE	AFTER
Capacitance	C	KC
Charge	CV	CV
PD	V	V/K
Energy	$\frac{1}{2}CV^2$	$\frac{1}{2}\frac{(CV)^2}{KC} = \frac{1}{2}\frac{CV^2}{K}$
Electric field	$E \propto d - V$ $E = \frac{V}{d}$	$E' \propto d - \frac{V}{K}$ $E' = \frac{V}{Kd}$

## Dielectric with battery

Consider a second case where a battery supplying a potential difference remains connected as the dielectric is inserted. Experimentally, it is found (first by Faraday) that the charge on the plates is increased by a factor  $K_e$

$$Q = K_e Q_0$$

Where  $Q_0$  is the charge on the plates in the absence of any dielectric


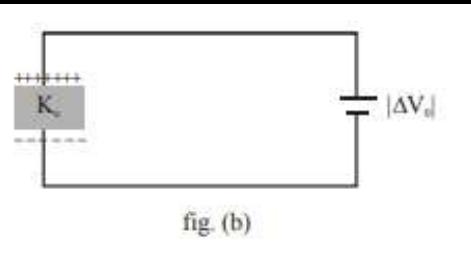
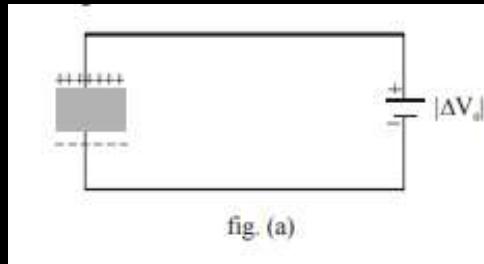


Figure: inserting a dielectric material between the capacitor plates while maintaining a constant potential difference  $|V_0|$

The capacitance becomes

$$C = \frac{Q}{|\Delta V_0|} = \frac{K_e Q_0}{|\Delta V_0|} = K_e C_0$$

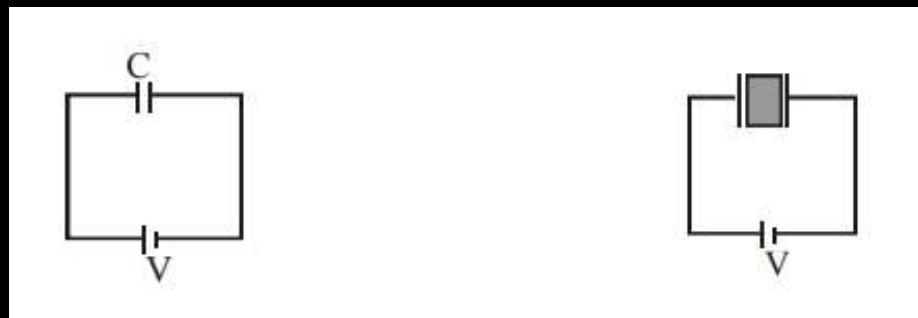
Which is the same as the first case where the charge  $Q_0$  is kept constant, but now the charge has increased.



EFFECT ON :	BEFORE	AFTER
Charge	$CV$	$KCV$
P.D.	$V$	$V$
Capacitance	$C$	$KC$
Energy	$\frac{1}{2}CV^2$	$\frac{1}{2}KCV^2$
Electric Field	$E = \frac{V}{d}$	$E = \frac{V}{d}$

Break 20 min

Resume at 8:15 min

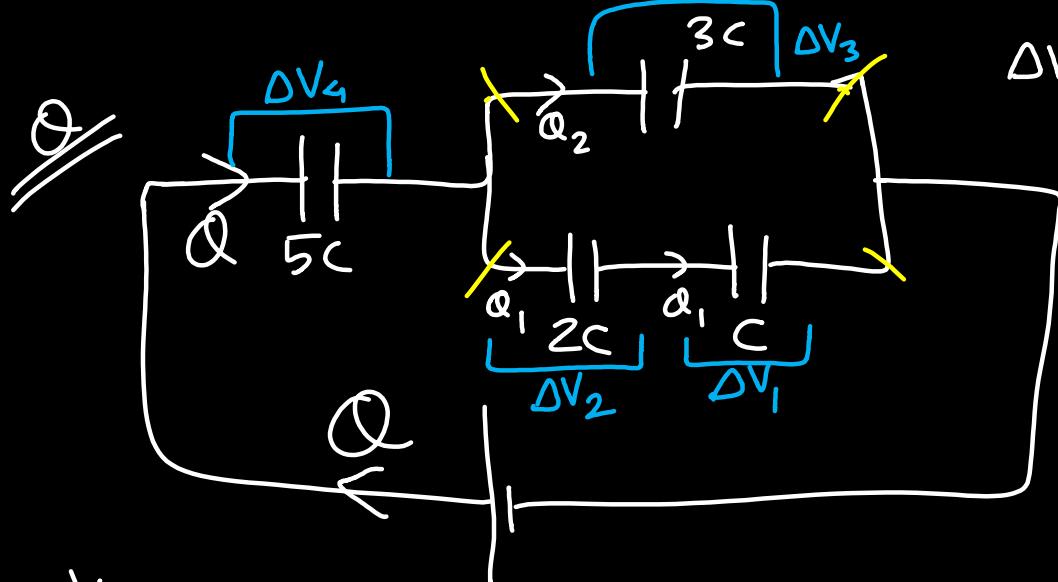

$$\Delta V = \frac{Q_1}{C} = 10$$

$$Q_1 = 10C$$

$$\Delta V_1 = 10$$

$$\begin{aligned}\Delta V_2 &= \frac{Q_1}{2C} = \frac{10C}{2C} \\ &= 5V\end{aligned}$$

$$\Delta V_1 + \Delta V_2 = \Delta V_3$$

$$10 + 5 = \Delta V_3$$

$$\Delta V_3 = \frac{Q_2}{3C} = 15$$

$$Q_2 = 45C$$

$$\Delta V_4 = \frac{Q}{5C} = \frac{65C}{5C}$$

Final

Voltage across C is 10 Volts


Find Emf of battery?

$$\text{Emf} = (\Delta V_1) + (\Delta V_3) = 26 \text{ Volts}$$

$$\begin{aligned}Q &= Q_1 + Q_2 \\ &= 10C + 45C \\ Q &= 55C\end{aligned}$$

$$\Delta V_4 = \frac{Q}{5C} = \frac{65C}{5C}$$

## Nodal Analysis

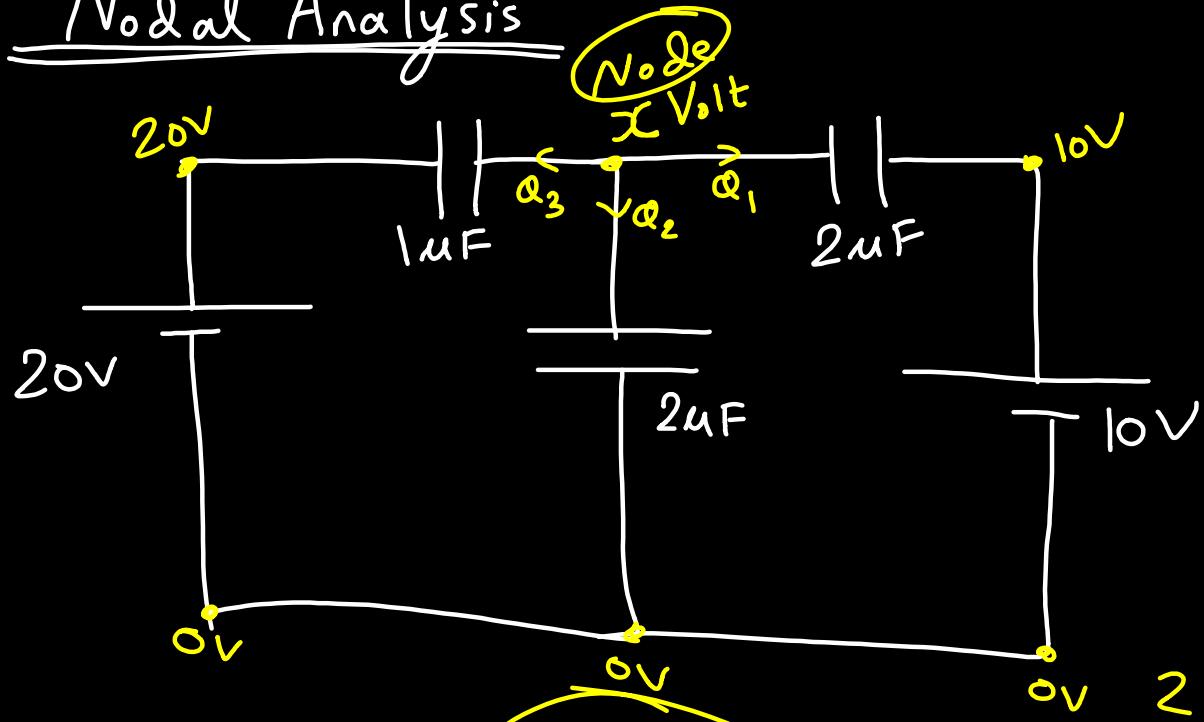

$$Q = C(V)$$

$$\begin{aligned} Q_2 &= 16 \mu\text{C} \\ |Q| &= 4 \mu\text{C} \\ |Q_3| &= 12 \mu\text{C} \end{aligned}$$

# Find charge on each capacitor ??

# Node Se Ha Jagah Charge Exit Karo


$$Q_1 + Q_2 + Q_3 = 0$$

$$2(x-10) + 2(x-0) + 1(x-20) = 0$$

$$5x = 40$$

$$x = 8$$


O H.W.

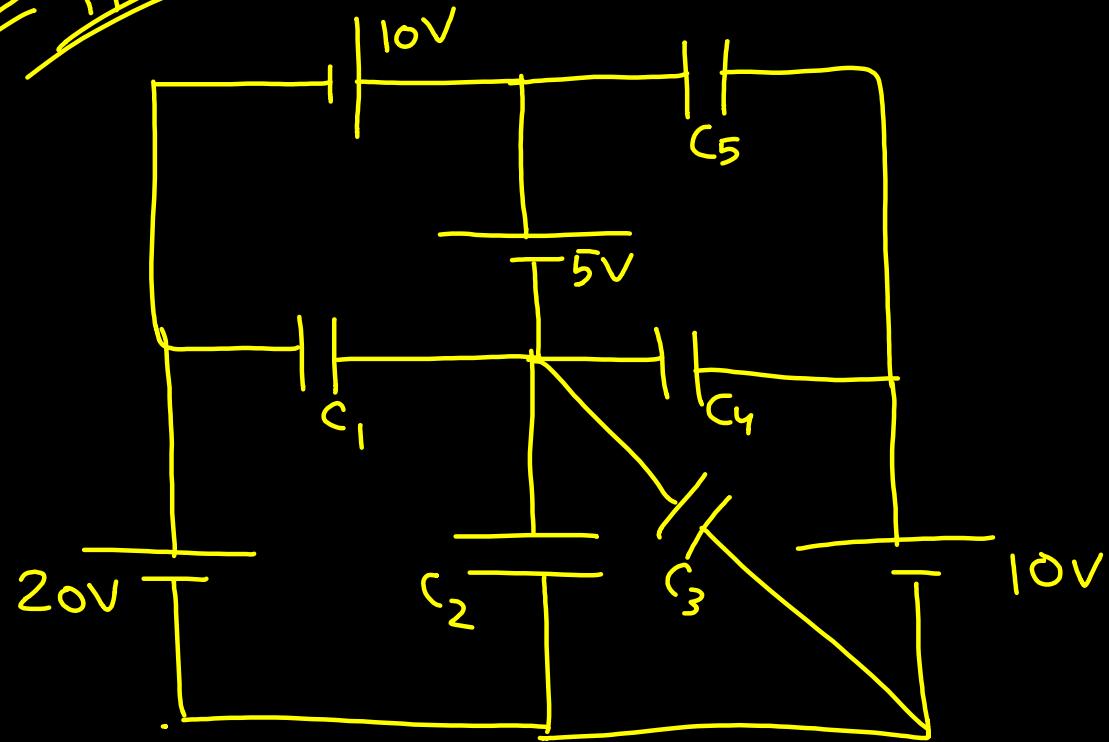

all  $C = 100 \mu F$

Find charge on each capacitor??.


## Dielectric

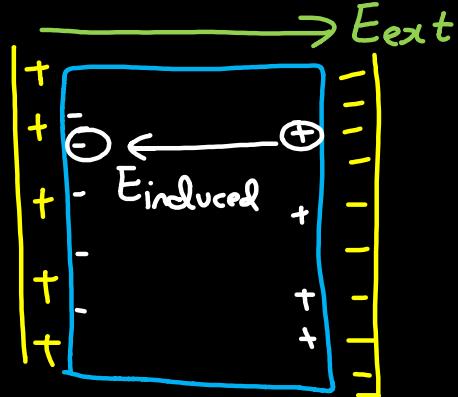

$$E_{\text{net}} = E_{\text{ext}} - E_{\text{induced}}$$

inside

## insulator

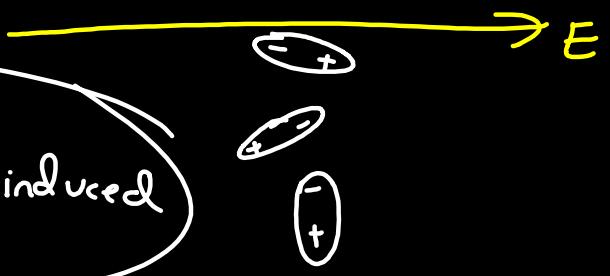

dipole wants to align along the field.



$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A\epsilon_0}$$


$$\Delta V = Ed = \frac{\sigma d}{\epsilon_0}$$

$$C = \frac{Q}{\Delta V}$$

$$C = \frac{A\epsilon_0}{d}$$

$$\begin{aligned} U &= \frac{1}{2} \epsilon_0 \epsilon^2 A d \\ &= \frac{Q^2}{2C} \\ &= \frac{1}{2} CV^2 \end{aligned}$$

full Space filled with dielectric

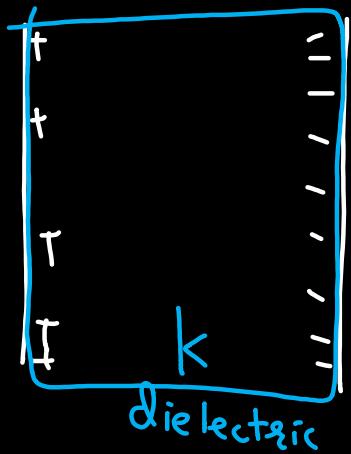

$$E_{\text{net}} = E_0 - E_{\text{induced}}$$

$$\frac{E_0}{k} = E_0 - E_{\text{induced}}$$

$$E_{\text{induced}} = E_0 - \frac{E_0}{k}$$

$$E_{\text{induced}} = E_0 \left(1 - \frac{1}{k}\right)$$

$$C_{\text{new}} = \frac{A\epsilon_0 k}{d} = kC \rightarrow k \text{ times.}$$

$$E_{\text{new}} = \frac{\sigma}{\epsilon_0 \epsilon_k} = \frac{Q}{A\epsilon_0 \epsilon_k} = \frac{Q}{A\epsilon_0 k} \quad [Q \text{ fixed}]$$

$$E_{\text{net}} = \frac{E_{\text{vacuum}}}{\text{inside}} \quad k$$

$$E = \frac{\sigma}{\epsilon_0}$$


$$E_{\text{ind}} = \frac{\sigma_{\text{ind}}}{\epsilon_0}$$

$$E_{\text{ind}} = E_0 \left( 1 - \frac{1}{k} \right)$$

$$\sigma_{\text{ind}} = \sigma \left( 1 - \frac{1}{k} \right)$$


OR

$$U = \frac{1}{2} C v^2$$

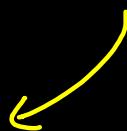

$v$  constant  
preferred

$$U = \frac{Q^2}{2C}$$

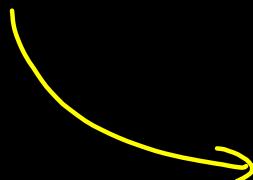


$Q$  constant  
Preferred.

$\frac{Q}{C}$

$C$  is charged battery <sup>disconnected</sup> <sub>not</sub>. Dielectric is inserted

Change in following Quantities.

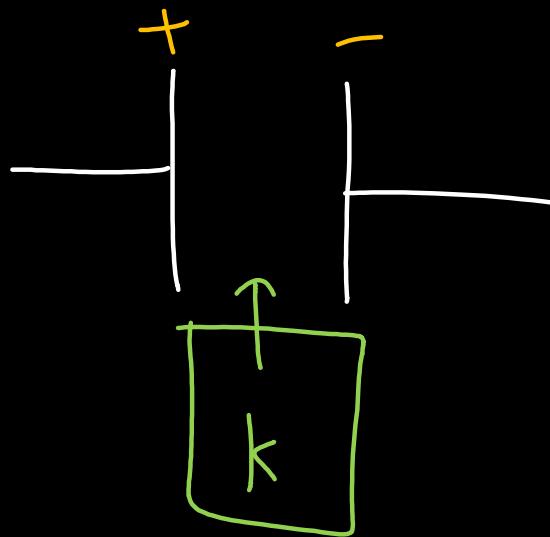

$$C \rightarrow kC \rightarrow K \text{ times}$$


$$E \rightarrow \frac{\sigma}{\epsilon_0} \frac{Q}{A\epsilon_0 \epsilon_k} \rightarrow \frac{1}{K} \text{ times.}$$

$$\Delta V \rightarrow Ed \rightarrow \frac{1}{K} \text{ times.}$$

$$U \rightarrow \frac{Q^2}{2C} \rightarrow \frac{1}{K} \text{ times.}$$

$$Q \rightarrow \text{constant}$$

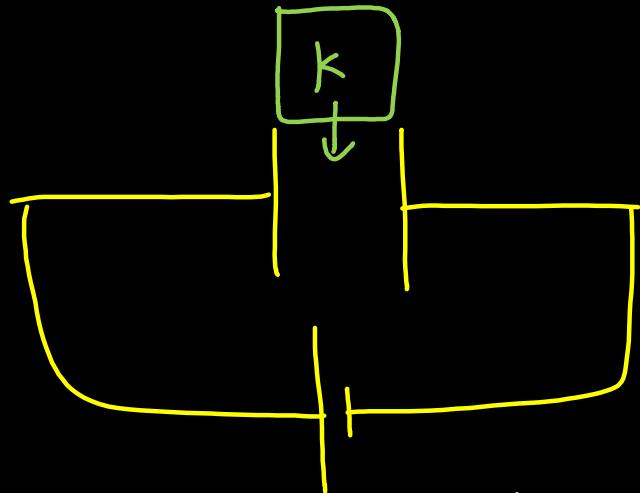$\otimes$   $C$  is connected with battery <sup>Kept</sup> Repeat



$C \rightarrow$   $\rightarrow K$  times.

$E \rightarrow \frac{\Delta V}{d} \rightarrow$  constant

$\Delta V \rightarrow$  constant constant


$U \rightarrow \frac{1}{2} CV^2 \rightarrow$   $K$  times.

$Q = C \Delta V \rightarrow Q = C \Delta V \rightarrow$   $K$  times.

$$E = \frac{\sigma}{\epsilon_0} = \frac{Q}{A \epsilon_0} = \left( \frac{\Delta V}{d} \right)$$

Find  $C_{eq}$


$$C_{eq} = C_1 + C_2$$

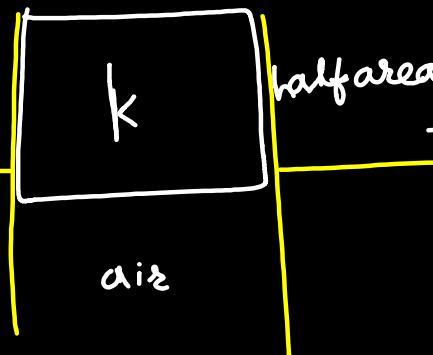


half area

$$= \frac{A\epsilon_0 k}{2d} + \frac{A\epsilon_0}{2d}$$

$$C_{eq} = \frac{A\epsilon_0(1+k)}{2d}$$

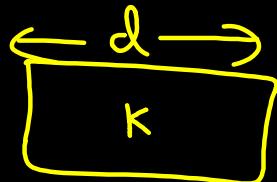
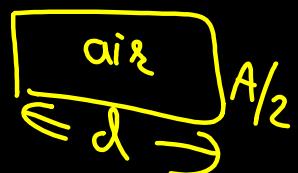
$$A/2 \quad C_1 = \frac{(A/2)(\epsilon_0)k}{d}$$




$$C_2 = \frac{(A/2)(\epsilon_0)}{d}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$= \frac{d}{2A\epsilon_0} + \frac{d}{2A\epsilon_0 k}$$

$$\frac{1}{C_{eq}} = \frac{d(k+1)}{2A\epsilon_0 k}$$
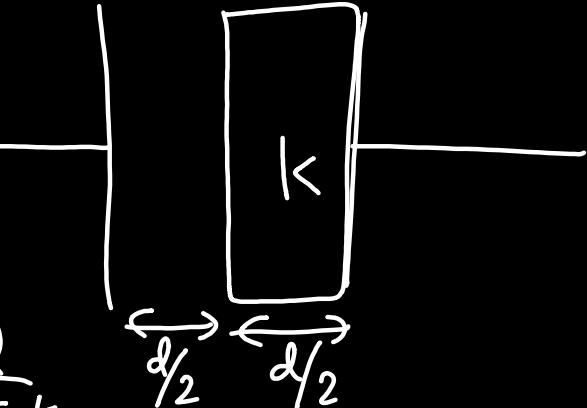
$$C_{eq} = \frac{2A\epsilon_0 k}{d(k+1)}$$




$$C_1 = \frac{A\epsilon_0}{d/2}$$


$$= \frac{2A\epsilon_0}{d}$$

$$C_2 = \frac{A\epsilon_0 k}{d/2}$$

$$C_2 = \frac{2A\epsilon_0 k}{d}$$

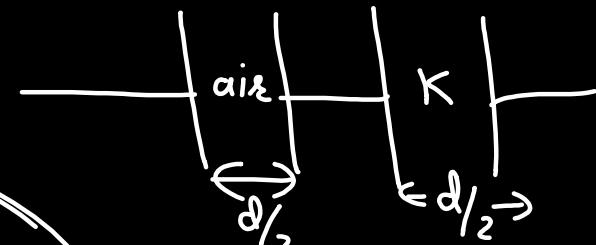

$\Theta$

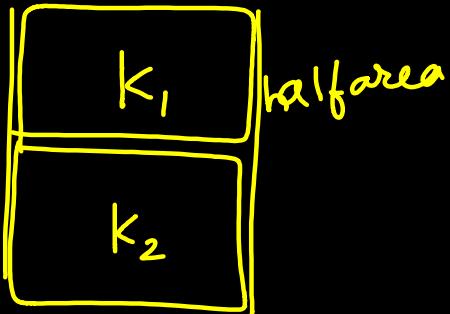

Find equivalent dielectric constant which can replace both when filled completely

$$C_{eq} = C_{ed}$$

$$\frac{A\epsilon_0}{2d}(k_1 + k_2) = \frac{A\epsilon_0}{d}k_{eq}$$

$$K_{eq}$$

$$\frac{k_1 + k_2}{2}$$


$$C_{eq} = \frac{A\epsilon_0 k_{eq}}{d}$$

$$C_1 = \frac{(A/2)(\epsilon_0)k_1}{d}$$

$$C_2 = \frac{(A/2)\epsilon_0 k_2}{d}$$

$$C_{eq} = C_1 + C_2 = \frac{A\epsilon_0(k_1 + k_2)}{2d}$$

~~Q~~

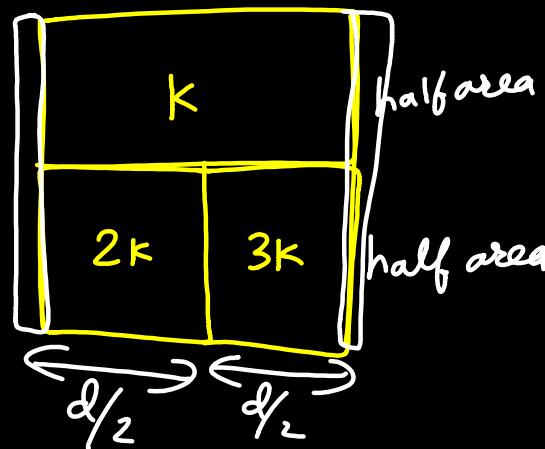

Find  $C_{\text{eff}} = ?$

=



$$C_1 = \frac{(A/2)(\epsilon_0)K}{(d)}$$


$$C_1 = \frac{A\epsilon_0 K}{2d}$$

$$C_{\text{eff}} = \left( \frac{C_2 C_3}{C_2 + C_3} \right) + C_1$$


$$C_2 = \frac{\left(\frac{A}{2}\right)(\epsilon_0)2K}{\left(\frac{d}{2}\right)} = \frac{2KA\epsilon_0}{d}$$

$$C_3 = \frac{\left(\frac{A}{2}\right)(\epsilon_0)3K}{\left(\frac{d}{2}\right)}$$


$$C_3 = \frac{3KA\epsilon_0 K}{d}$$

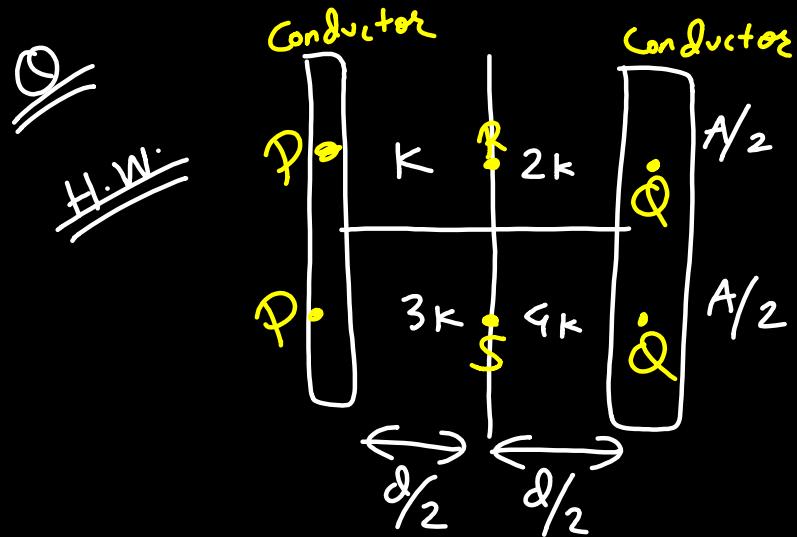
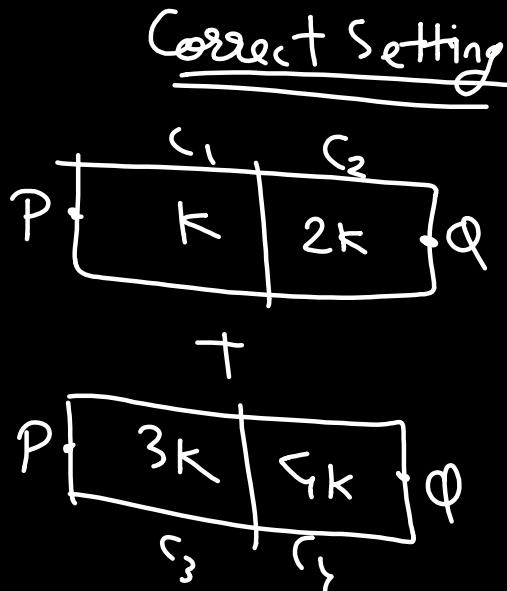
$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} + \frac{C_3 C_4}{C_3 + C_4}$$




This Setting is Wrong

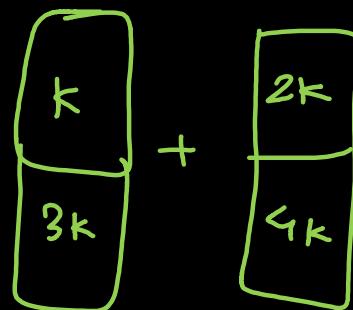

K & 3K  $\parallel$   $\text{Nahi Man}$


2K & 4K " " " "

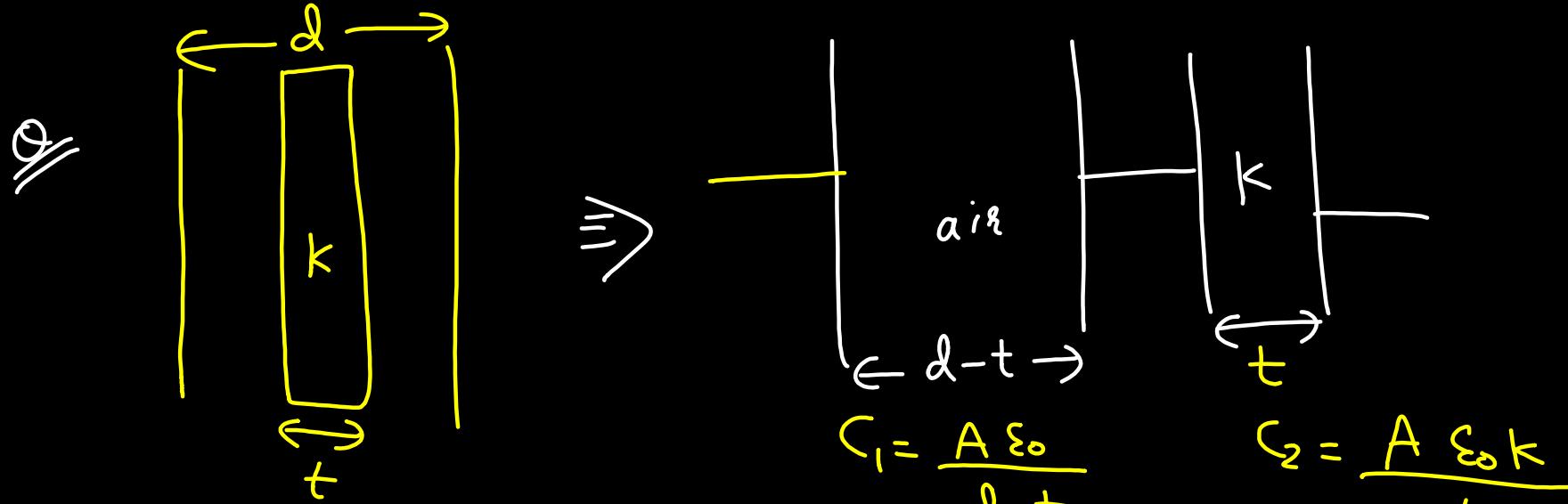

$$\begin{aligned}\frac{1}{C_{eq}} &= \frac{1}{C_1} + \frac{1}{C_2} \\ &= \frac{d-t}{A\varepsilon_0} + \frac{t}{A\varepsilon_0 k} = \frac{dk - tk + t}{A\varepsilon_0 k}\end{aligned}$$

$$\Rightarrow C_{eq} = \frac{A \varepsilon_0}{d+t\left(\frac{1}{k}-1\right)}$$

Variable  $K$

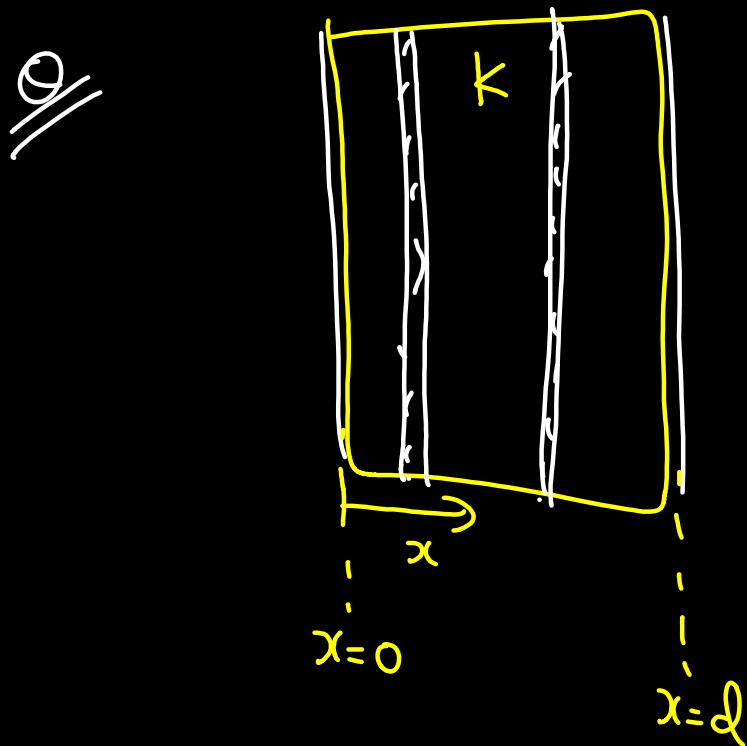

$$K = \alpha x + \beta$$



$$C = \frac{(A)(\epsilon_0)(k)}{(dx)}$$

$$C = \frac{A \epsilon_0 (\alpha x + \beta)}{dx}$$

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \dots - \infty$$


$$\frac{1}{C_{eq}} = \int \frac{1}{C}$$

$$\begin{aligned}
 \frac{1}{C_{e\alpha}} &= \int_{x=0}^{x=d} \frac{1}{C} \\
 &= \int_{x=0}^{x=d} \frac{dx}{A\epsilon_0 (\alpha x + \beta)} \\
 &= \frac{1}{A\epsilon_0} \left[ \frac{1}{\alpha} \log(\alpha x + \beta) \right]_0^d
 \end{aligned}$$

$$\frac{1}{C_{e\alpha}} = \frac{1}{\alpha A \epsilon_0} \left( \log(\alpha d + \beta) - \log \beta \right)$$


$$C_{e\alpha} = \frac{\alpha A \epsilon_0}{\log \left( \frac{\alpha d + \beta}{\beta} \right)}$$

$\textcircled{2} \quad y = l -$

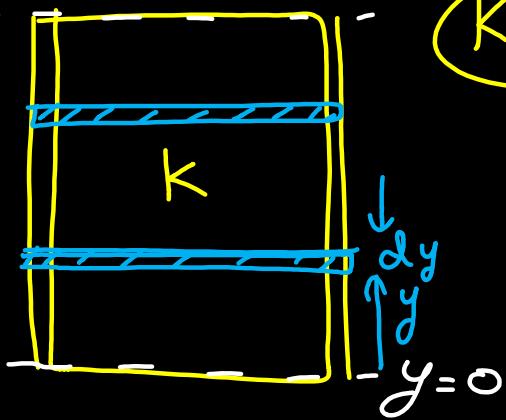

$$K = \alpha y + \beta$$

width of plate =  $w$  (into the plane)

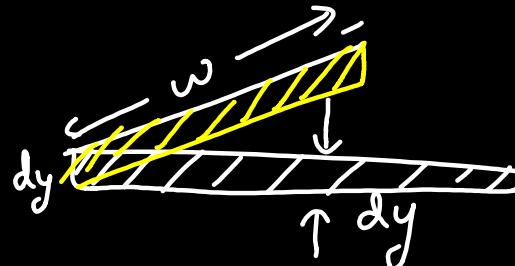


$$\text{area} = (dy) w$$

$$C = \frac{(\omega dy) (\epsilon_0) k}{(d)} = \frac{\omega(dy) \epsilon_0 (\alpha y + \beta)}{d}$$

Find  $C_{eq.}$

$$C_{ed} = C_1 + C_2 + C_3 + \dots$$

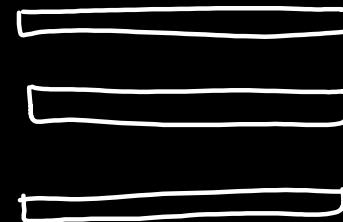


$$= \int C$$

$$= \int \frac{\omega \epsilon_0}{d} (\alpha y + \beta) dy$$

$$= \left[ \frac{\omega \epsilon_0}{d} \left( \frac{\alpha y^2}{2} + \beta y \right) \right]_0^l$$

$$C_{ed} = \frac{\omega \epsilon_0}{d} \left( \frac{\alpha l^2}{2} + \beta l \right)$$

Q

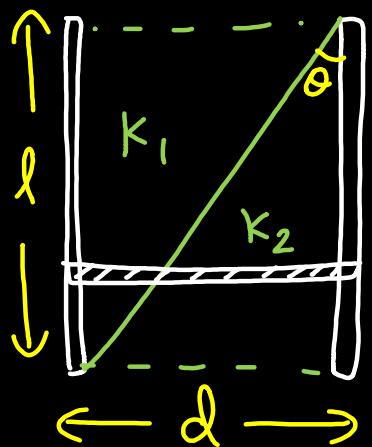

$k_1$  &  $k_2$  constant


Find  $C_{eq}$

Square plates

$$\text{area} = l^2$$

$$\text{width} = l$$



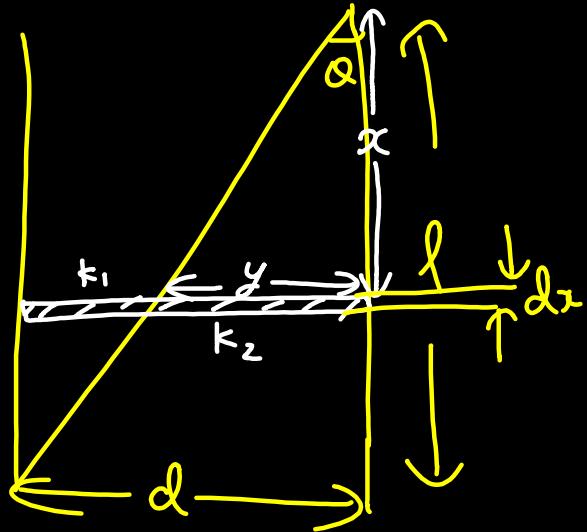

$$\tan \theta = \frac{d}{l} = \frac{y}{x}$$

$$\frac{x d}{l} = y$$



$$C_1 = \frac{(l dx) (\epsilon_0) k_1}{(d-y)}$$

$$C_2 = \frac{(l dx) (\epsilon_0) k_2}{y}$$


$$\begin{aligned} \frac{1}{C_{eq}} &= \frac{1}{C_1} + \frac{1}{C_2} \\ &= \frac{d-y}{k_1 \epsilon_0 l (dx)} + \frac{y}{\epsilon_0 k_2 l dx} \end{aligned}$$

area  
area =  $l(dx)$

$$\frac{1}{C_{eq}} = \frac{k_2(d-y) + k_1y}{k_1 k_2 \epsilon_0 l dx}$$

$$C_{eq} = \frac{k_1 k_2 \epsilon_0 l dx}{k_2 d + y(k_1 - k_2)}$$

$$y = \frac{x d}{l}$$

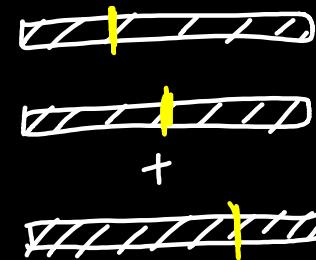


$$C_{e\alpha} = \int C_{e\alpha} = k_1 k_2 \epsilon_0 \lambda \int \frac{dx}{k_2 \lambda + \frac{x \lambda}{\ell} (k_1 - k_2)}$$

$$= \frac{k_1 k_2 \epsilon_0 \lambda}{\frac{\lambda}{\ell} (k_1 - k_2)} \left[ \log_e \left( k_2 \lambda + \frac{x \lambda}{\ell} (k_1 - k_2) \right) \right]_0^\ell$$

$\ell^2$  = area of plate

$$C_{e\alpha} = \frac{k_1 k_2 \epsilon_0 \lambda^2}{\lambda (k_1 - k_2)} \log_e \left( \frac{k_1}{k_2} \right)$$

## Force on Dielectric


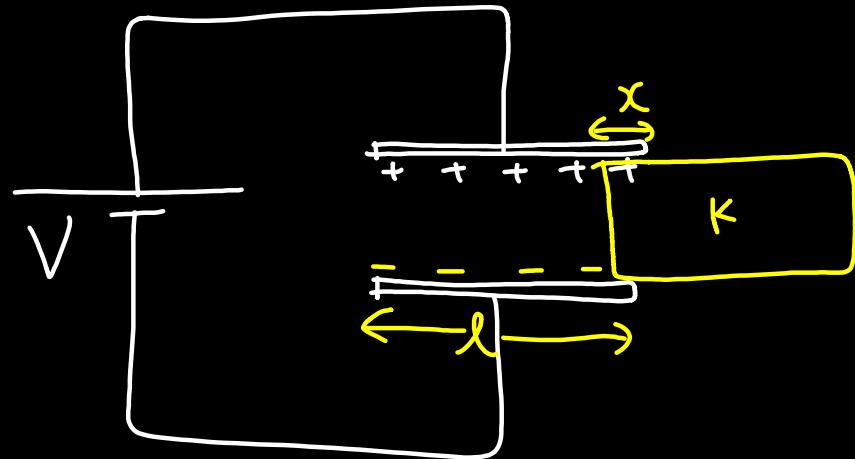



$$C_1 = \frac{(\omega)(l-x)}{\delta} \epsilon_0$$

$$C_2 = \frac{(\omega)x}{\delta} \epsilon_0 k$$

$$F = -\frac{\partial U}{\partial x}$$

width =  $\omega$

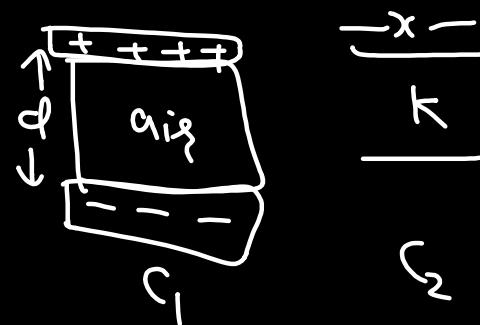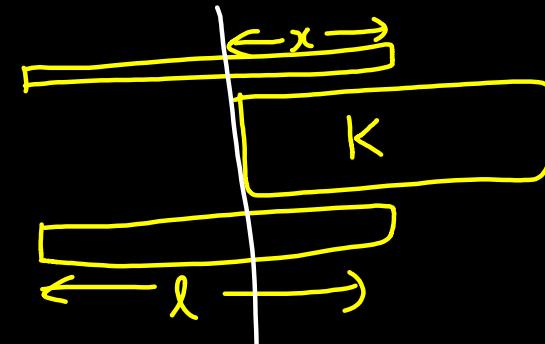

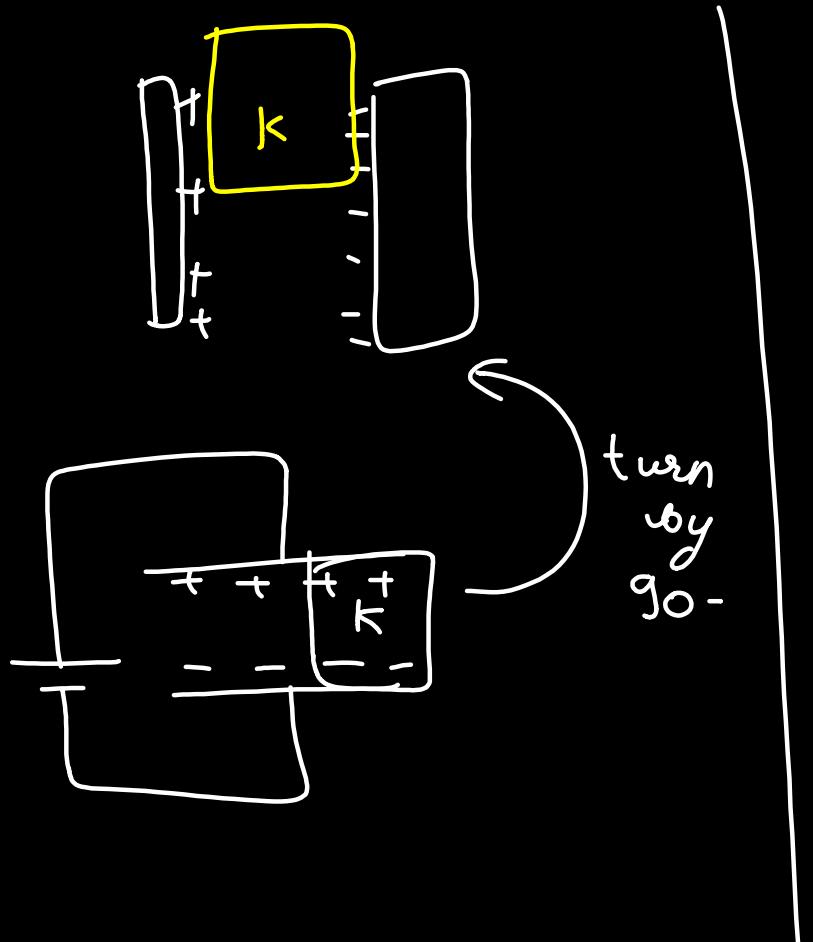

$$\begin{aligned}
 C_{eq} &= C_1 + C_2 \\
 &= \frac{\omega(l-x)\epsilon_0}{d} + \frac{\omega x\epsilon_0 k}{d}
 \end{aligned}$$

$$C_{eq} = \frac{\omega\epsilon_0}{d} [l - x + kx]$$

$$U = \frac{1}{2} C V^2$$


$$U = \frac{1}{2} \frac{\omega \epsilon_0}{d} (k - \epsilon + k\epsilon) V^2$$

$$\left| F \right| = \left| \frac{\partial U}{\partial x} \right| = \frac{1}{2} \frac{\omega \epsilon_0}{d} (0 - 1 + k) V^2$$

$$F = \frac{\omega \epsilon_0 V^2}{2d} (k - 1)$$

Constant

$$acc = \frac{F}{m}$$

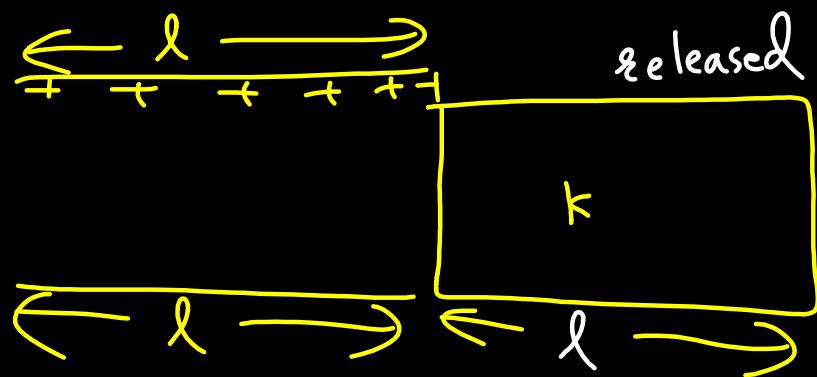

$$U = 0$$

$$a = F/m$$

$$s = l$$

$$s = vt + \frac{1}{2}at^2$$

$$\sqrt{\frac{2s}{a}} = t_0$$

$$\text{Time Period oscillation} = 4t$$